

Name:

ID#

1. (10%) A cellphone incorporates a 2.4GHz oscillator whose frequency is defined by the resonance frequency of an  $LC$  tank. If the tank capacitance is realized as the  $pn$  junction of Example 2.15, calculate the change in the oscillation frequency while the reverse voltage goes from 0 to 1.5 V. Assume the circuit operates at 2.4 GHz at a reverse voltage of 0 V, and the junction area is  $2500 \mu\text{m}^2$ .

$$f_{res} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}, C_j = 0.265 \text{ fF} / \mu\text{m}^2, C_{j,tot} = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_0}}}, V_0 = 0.73 \text{ V}$$

Ans:

$$jL\omega_{res} = -(jC\omega_{res})^{-1} \quad f_{res} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

$$\text{at } V_R = 0 \text{ V and } C_j = 0.265 \text{ fF} / \mu\text{m}^2$$

$$C_{j,tot} (V_R = 0) = (0.265 \text{ fF} / \mu\text{m}^2) \times (2500 \mu\text{m}^2) = 662.5 \text{ fF}$$

$$f_{res} = 2.4 \text{ GHz} = \frac{1}{2\pi} \frac{1}{\sqrt{L \times 662.5 \text{ fF}}}, L = 6.64 \text{ nH}$$

$$\text{if } V_R = 1.5 \text{ V} \quad C_{j,tot} = \frac{C_{j0}}{\sqrt{1 + \frac{1.5}{0.73}}} \times 2500 \mu\text{m}^2 = 379 \text{ fF}$$

$$f_{res} (V_R = 1.5) = \frac{1}{2\pi} \frac{1}{\sqrt{L \times 379 \text{ fF}}} = 3.17 \text{ GHz}$$

2. (10%). An NMOS device with  $\lambda = 0.1 \text{ V}^{-1}$  must provide a  $g_m r_o$  of 20 with  $V_{DS} = 1.5 \text{ V}$ . Determine the required value of  $W/L$  if  $I_D = 0.5 \text{ mA}$ . Assume  $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$ , and  $V_{TH} = 0.4 \text{ V}$ .

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2, \quad g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

Ans:

3b. Given NMOS with  $\lambda = 0.1 \text{ V}^{-1}$   $g_m r_o = 20$   
 $V_{DS} = 1.5 \text{ V}$   
 determine  $W/L$  if  $I_D = 0.5 \text{ mA}$ .


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 \text{ V}^{-1})(0.5 \text{ mA})} = 20 \text{ k}\Omega$$

$$\Rightarrow g_m = \frac{20}{20 \text{ k}\Omega} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$


$$\begin{aligned} \therefore \frac{W}{L} &= \left( \frac{20}{20 \text{ k}\Omega} \right)^2 \frac{1}{2 \mu_n C_{ox} I_D} \\ &= \left( \frac{1}{\text{k}\Omega} \right)^2 \frac{1}{2 \left( \frac{200 \mu\text{A}}{\text{V}^2} \right) (0.5 \text{ mA})} \approx 5. \end{aligned}$$

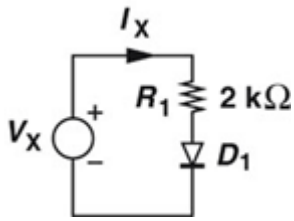3. (10%) Suppose  $D_1$  must sustain a voltage 850 mV for  $V_X = 2.0$  V.  $R_1 = 2.0$  k $\Omega$ . Calculate the required  $I_S$ .

$$V_T = 26\text{mV}, I_D = I_S \exp^{\frac{V_D}{V_T}}$$



21.

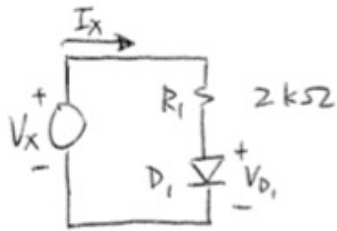


Given: @  $V_X = 2\text{V}$ ,  $V_{D_1} = 850\text{mV}$

$$\Rightarrow I_X = \frac{V_X - V_{D_1}}{R_1} = 0.58\text{ mA}$$


$$\begin{aligned} \therefore I_S &= \frac{I_X}{(e^{V_{D_1}/V_T} - 1)} \approx I_X \exp[-V_{D_1}/V_T] \\ &= (0.58\text{ mA}) \exp[-0.85/0.026] \approx 3.64 \cdot 10^{-18}\text{ A} \end{aligned}$$

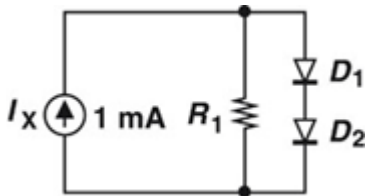4. (10%) In the following circuit, determine the value of  $R_1$  such that this resistor carries 0.5 mA.

Assume  $I_S = 5 \times 10^{-16}$  A for each diode.  $V_T = 26\text{mV}$ ,  $I_D = I_S \exp^{\frac{V_D}{V_T}}$



29.

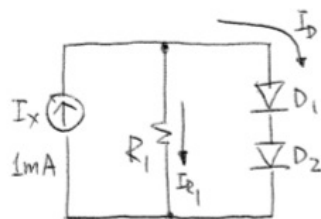

Given  $I_{R_1} = 0.5\text{ mA}$ ,  
 $I_S = 5 \cdot 10^{-16}\text{ A}$  for  
 each diode.


Find  $R_1$ .

$$\text{By KCL, } I_D = I_X - I_{R_1} = 0.5\text{ mA}$$

$$\begin{aligned} \Rightarrow V_{D_1} = V_{D_2} &= V_T \ln\left(\frac{I_D}{I_S}\right) = 0.026 \ln\left(\frac{0.5\text{ mA}}{5 \cdot 10^{-16}\text{ A}}\right) \\ &\approx 0.718\text{ V} \end{aligned}$$

$$\therefore R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{2 V_{D_1}}{I_{R_1}} = \frac{2(0.718\text{ V})}{0.5\text{ mA}} = 2.87\text{ k}\Omega$$

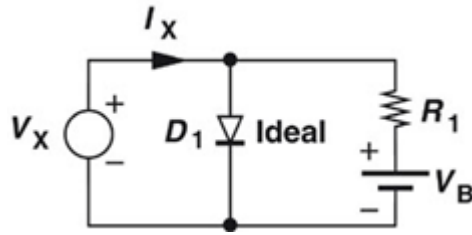
5. (10%) For the circuits shown below, choose the correct  $I_X/V_X$  characteristic for  $V_B=+1\text{V}$  and  $V_B=-1\text{V}$




Ans:

$$I_X = \begin{cases} \frac{V_X - V_B}{R_1} & V_X < 0 \\ \infty & V_X > 0 \end{cases}$$

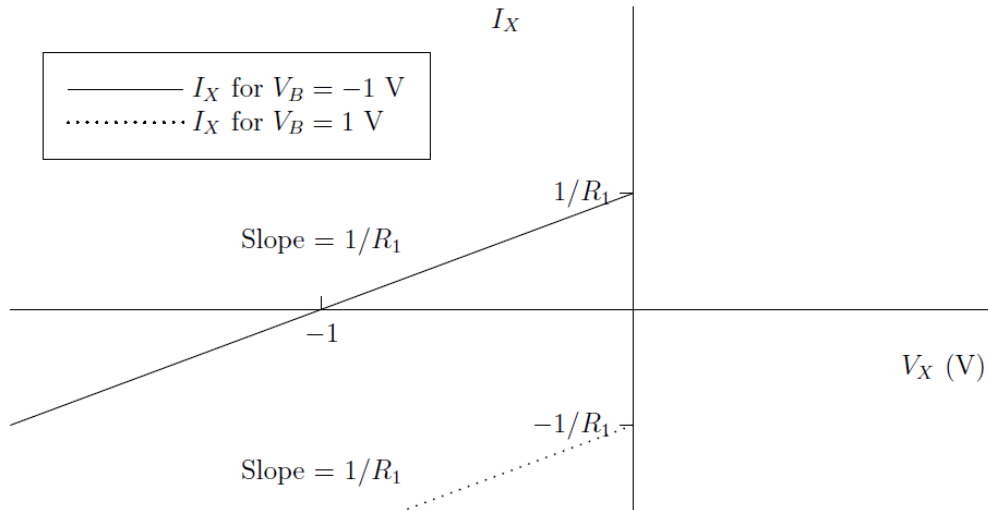
Plotting  $I_X$  vs.  $V_X$  for  $V_B = -1\text{V}$  and  $V_B = 1\text{V}$ , we get:



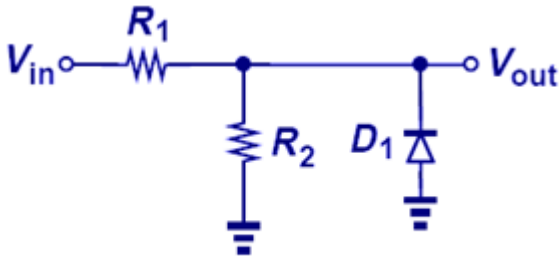6. (10%) Using the constant voltage mode, plot the input/output characteristic of the following circuit.




Ans:

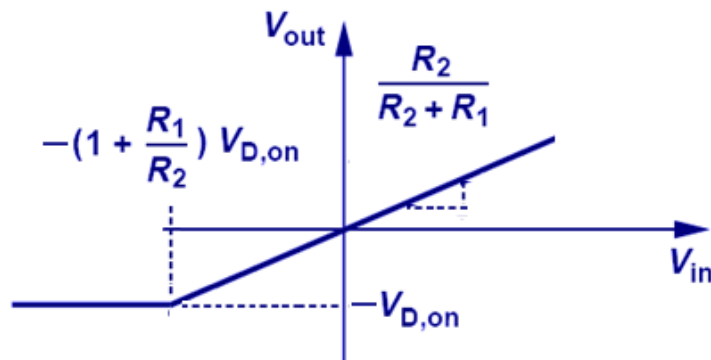

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in} = -V_{D,on} \Rightarrow V_{in} = -\left(1 + \frac{R_1}{R_2}\right) V_{D,on}$$

7. (10%) If  $W/L = 10/0.18$  and  $\lambda=0$ , determine the operating point of  $M_1$  in the following circuit.

$$\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2, \text{ and } V_{TH} = -0.4\text{V}. \quad I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2$$

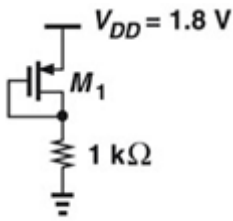


Ans:

(b) Since  $M_1$  is diode-connected, we know it is operating in saturation.

$$\begin{aligned} |V_{GS}| &= |V_{DS}| \\ V_{DD} - |V_{GS}| &= |I_D|(1 \text{ k}\Omega) = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 (1 \text{ k}\Omega) \\ |V_{GS}| = |V_{DS}| &= \boxed{0.952 \text{ V}} \\ |I_D| &= \boxed{848 \mu\text{A}} \end{aligned}$$

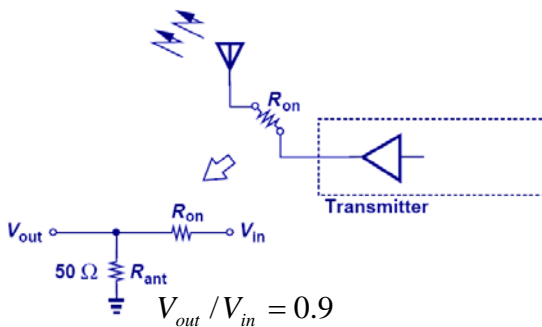8. (10%) The switch connecting the transmitter to the antenna attenuates the signal by no more than 10%. If  $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$ , and  $V_{TH} = 0.4\text{V}$ , and the  $W/L$  is 1500, determine the minimum required  $V_{GS}$  of the switch.

Assume the antenna can be model as a  $50\Omega$  resistor.  $R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$



Ans:


$$V_{out} = \frac{R_{ant}}{R_{ant} + R_{on}} = \frac{50}{50 + R_{on}} = 0.90, R_{on} = 5.6$$

$$R_{on} = \frac{1}{\mu_n C_{ox} (W/L)(V_{GS} - V_{TH})} = 5.6 = \frac{1}{200 \times 10^{-6} \times 1500 \times (V_{GS} - 0.4)}$$

$$V_{GS} = 0.995\text{V}$$

9 (10%) Determine the W/L of the above figure that place the  $M_1$  at the edge of saturation. Assume
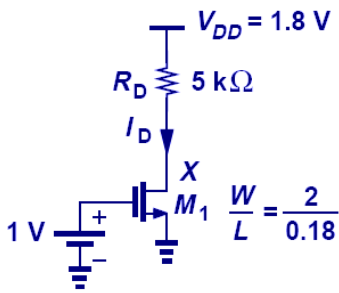
$$\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2, \text{ and } V_{TH} = 0.5\text{V}. \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$



Ans:


$V_{GS} = +1\text{V}$ , drain voltage must fall to  $V_{GS} - V_{TH} = 0.5\text{V}$  for  $M_1$  enter triode region.

$$I_D = \frac{V_{DD} - V_{DS}}{R_D} = 260 \mu\text{A} = I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$


$$260 \mu\text{A} = \frac{1}{2} \times 200 \mu\text{A}/\text{V}^2 \times \frac{W}{L} (1 - 0.5)^2$$

$$\frac{W}{L} = \frac{260}{100 \times 0.25} = \frac{1.872}{0.18}$$

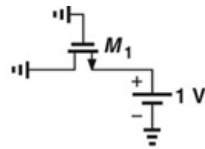
10. (10%) Please determine the region of  $M_1$  in each circuit. Assume  $V_{TH} = 0.4\text{V}$ , ( $V_{GS} < V_{TH}$ , MOS is at OFF region,  $V_{DS} > V_{GS} - V_{TH}$  MOS at saturation region,  $V_{DS} < V_{GS} - V_{TH}$ , MOS at triode region)




(a)

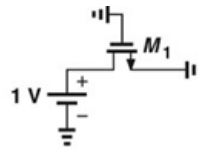

(b)

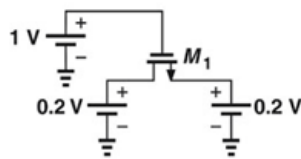

(c)

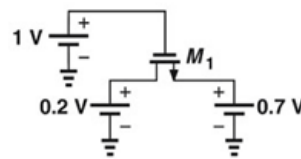

(d)

Ans:

20. (a) OFF  $\because V_{GS} = 0 \quad (V_{GS} < V_{TH})$

(b) OFF  $\because V_{GS} = 0 \quad (V_{GS} < V_{TH})$

(c) TRIODE (LINEAR)  $\because V_{GS} > V_{TH} \ \& \ V_{DS} \ll 2(V_{GS} - V_{TH})$

(d) SATURATION  $\because V_{GS} > V_{TH} \ \& \ V_{DS} > V_{GS} - V_{TH}$