

國立中山大學一百學年度第一學期資工系數位系統期末考試

學號：

姓名：

一、選擇與是非題（每題 3 分，12 分）

- () 1. What kind of flip-flop is the most popular component to compose a register? ①SR ②D ③JK ④T
- () 2. How many address lines are required in an 8M×16 RAM? ①12 ②18 ③23 ④24
- () 3. Which one is non-volatile memory? ① Registers ②SRAM ③ DRAM ④ Flash memory
- () 4. In a ripple counter, all flip-flops use the same clock signal.

二、問答題（98 分）

1. Derive the following terms for the sequential circuit shown in Fig. 1.

- (1) Input (Excitation) equations (5%)
- (2) State equations and output equation (6%)
- (3) State table (8%)
- (4) State diagram (5%)

2. The state diagram for sequence detector which detects a sequence of three or more consecutive 1's in a string of bits coming through an input line x is shown in Fig. 2(a).

- (1) Complete the state table as shown in Table 1 using natural binary encoding for state assignment (i.e., $S_0 = 00, S_1 = 01, S_2 = 10, S_3 = 11$). (4%)
- (2) Use D flip-flops and derive the simplified flip-flop input (excitation) equations and output equation using the K-map. (4%)
- (3) Draw the logic diagram of sequence detector with D flip-flops as shown in Fig. 2(b). (4%)
- (4) Use JK flip-flops and complete the state table and JK flip-flop input as shown in Table 2. (6%)
- (5) Use JK flip-flops and derive the simplified flip-flop input (excitation) equations using the K-map. (6%)
- (6) Draw the logic diagram of sequence detector with JK flip-flops as shown in Fig. 2(c). (4%)

3. Design the synchronous sequential circuit using T flip-flops with the state diagram as shown in Fig. 3(a).

- (1) Complete the state table as shown in Table 3. (8%)
- (2) Derive the simplified flip-flop input (excitation) equations. (6%)
- (3) Draw the logic diagram with T flip-flops as shown in Fig. 3(b). (5%)

4. Please answer the following problems.

- (1) Briefly explain the operations of the 4-bit universal shift register shown in Fig. 4. (6%)
- (2) Briefly explain the read and write operations of the 4×4 RAM and the memory cell as shown in Fig. 5(a) and 5(b), respectively. (8%)

5. Using an 8×2 ROM shown in Fig. 6 and a $3 \times 4 \times 2$ PLA shown in Fig. 7, implement the truth table shown in Table 4. (13%)

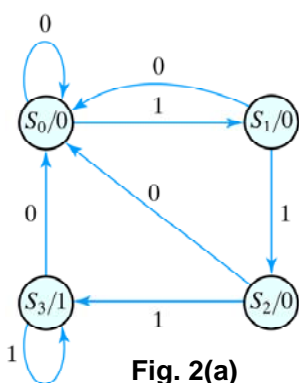


Fig. 2(a)

Table 1					
Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	1	1

Table 2								
Present State		Input	Next State		Flip-Flop Inputs			
A	B	x	A	B	J_A	K_A	J_B	K_B
0	0	0	0	0				
0	0	1	0	1				
0	1	0	0	1				
0	1	1	1	0				
1	0	0	1	0				
1	0	1	1	1				
1	1	0	1	1				
1	1	1	1	1				

國立中山大學一百學年度第一學期資工系數位系統期末考試

學號：

姓名：

Fip-flop	D	JK		T																																			
characteristic equation	$Q(t+1) = D$	$Q(t+1) = JQ' + K'Q$		$Q(t+1) = T \oplus Q$																																			
characteristic table	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>D</th> <th>Q(t+1)</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> </tr> </tbody> </table>	D	Q(t+1)	0	0	1	1	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>J</th> <th>K</th> <th>Q(t+1)</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>Q(t)</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>Q'(t)</td> </tr> </tbody> </table>	J	K	Q(t+1)	0	0	Q(t)	0	1	0	1	0	1	1	1	Q'(t)	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>T</th> <th>Q(t+1)</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>Q(t)</td> </tr> <tr> <td>1</td> <td>Q'(t)</td> </tr> </tbody> </table>	T	Q(t+1)	0	Q(t)	1	Q'(t)									
D	Q(t+1)																																						
0	0																																						
1	1																																						
J	K	Q(t+1)																																					
0	0	Q(t)																																					
0	1	0																																					
1	0	1																																					
1	1	Q'(t)																																					
T	Q(t+1)																																						
0	Q(t)																																						
1	Q'(t)																																						
excitation table	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>Q(t)</th> <th>Q(t=1)</th> <th>J</th> <th>K</th> <th>Q(t)</th> <th>Q(t=1)</th> <th>T</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>X</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>X</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>X</td> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	Q(t)	Q(t=1)	J	K	Q(t)	Q(t=1)	T	0	0	0	X	0	0	0	0	1	1	X	0	1	1	1	0	X	1	1	0	1	1	1	X	0	1	1	0			
Q(t)	Q(t=1)	J	K	Q(t)	Q(t=1)	T																																	
0	0	0	X	0	0	0																																	
0	1	1	X	0	1	1																																	
1	0	X	1	1	0	1																																	
1	1	X	0	1	1	0																																	

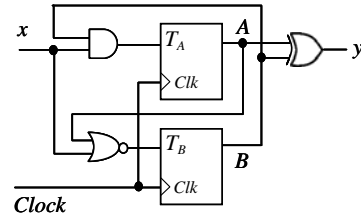


Fig. 1

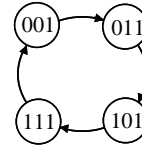


Fig. 3(a)

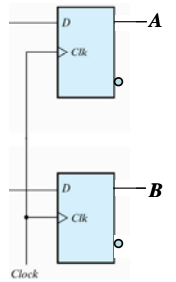


Fig. 2(b)

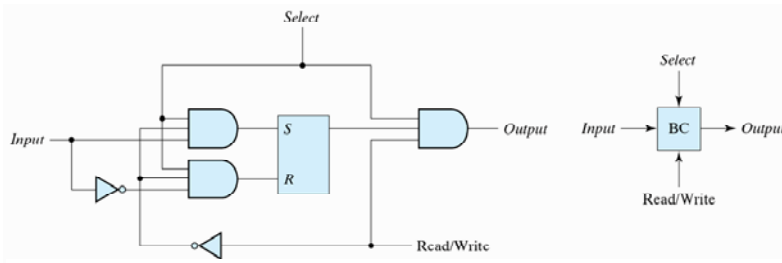


Fig. 5(b)

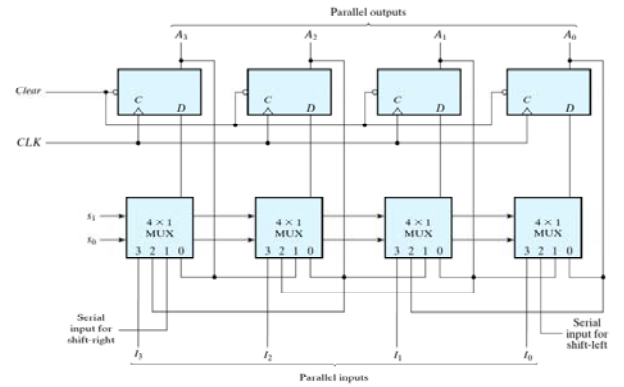


Fig. 4

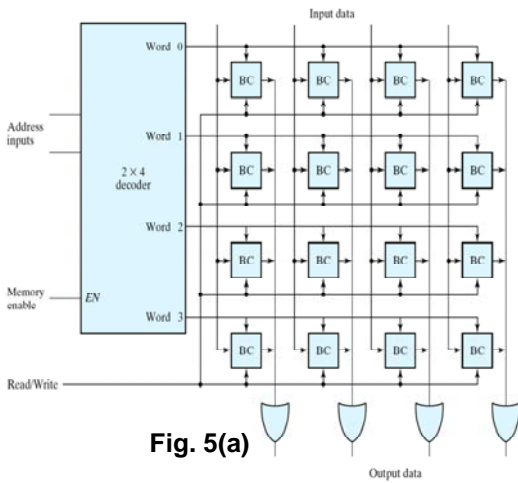


Fig. 5(a)

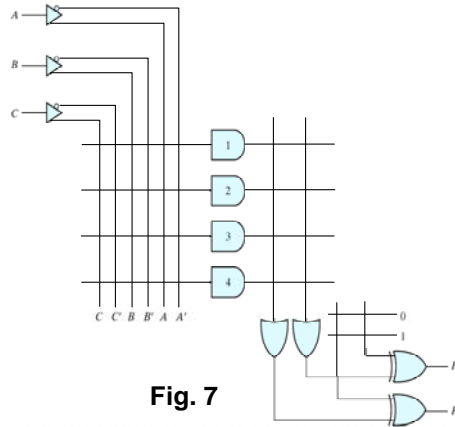


Fig. 7

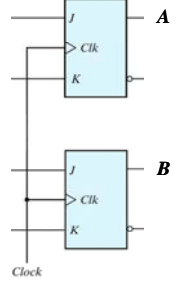


Fig. 2(c)

Table 3

Present State			Next State			Flip-Flop Inputs		
A ₂	A ₁	A ₀	A ₂	A ₁	A ₀	T _{A2}	T _{A1}	T _{A0}
0	0	0	0	0	0			
0	0	1	0	0	1			
0	1	0	1	0	0			
0	1	1	1	1	1			
1	0	0	1	0	0			
1	0	1	1	1	1			
1	1	0	0	1	0			
1	1	1	0	1	1			

Table 4

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	1	1
1	0	0	1	0
1	0	1	1	1
1	1	0	0	1
1	1	1	0	1

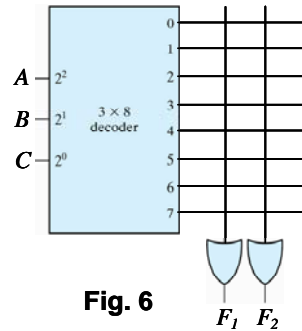


Fig. 6

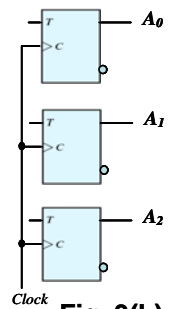


Fig. 3(b)