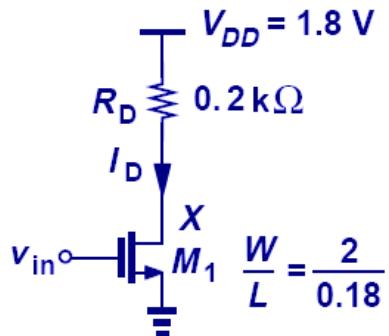


Name:

ID#

1. (8%) Calculate the small signal voltage gain of the CS stage if $I_D=1\text{mA}$, $\mu_n C_{ox}=100\text{uA/V}^2$, and $V_{TH}=0.5\text{V}$ and $\lambda=0$. Verify that M_1 is in the saturation. $g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$



Ans:

$$R_D I_D < V_{DD} - (V_{GS} - V_{TH})$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 \times 100\text{u} \times \frac{2}{0.18} \times 1\text{m}} = \frac{1}{670.82\Omega}$$


$$A_V = -g_m R_D = -\frac{1}{670.82} 0.2k = -0.298$$

$$V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = 0.5 + \sqrt{\frac{2 \times 1\text{m}}{100\text{u} \times \frac{2}{0.18}}} = 1.84\text{V}$$


$$V_{DD} - R_D I_D = 1.8 - 0.2k \times 1\text{mA} = 1.6\text{V} \quad V_{GS} - V_{TH} = 1.84 - 0.5 = 1.34$$

the device is saturation and has a margin of 0.26V with respect to the triode region

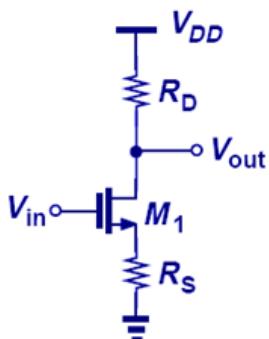2. (6%) Draw the small signal model of the following source degeneration circuit. And find the small signal gain of the following circuit.




Ans:

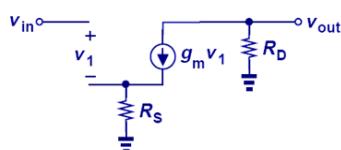

$$v_{in} = v_1 + g_m v_1 R_S \Rightarrow v_1 = \frac{v_{in}}{1 + g_m R_S} \quad v_{out} = -g_m v_1 R_D \quad \frac{v_{out}}{v_{in}} = -\frac{g_m R_D}{1 + g_m R_S} = -\frac{\frac{R_D}{g_m}}{\frac{1}{g_m} + R_S}$$

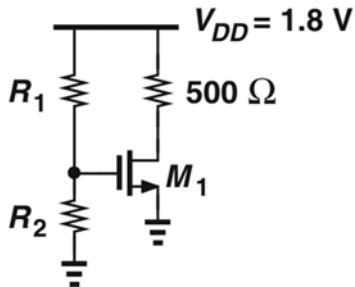3. (12%) For $I_D=1\text{mA}$ and $\text{W/L}=20/0.18$, compute R_1 and R_2 such that input impedance at least $20\text{k}\Omega$.

$$\mu_n C_{ox} = 200 \text{uA/V}^2, \text{ and } V_{TH} = 0.5\text{V} \text{ and } \lambda = 0. \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$



Ans:

$$\textcircled{2} \quad T_0 \text{ get } I_{DS} = 1 \text{ mA}$$

$$\frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 = 1 \times 10^{-3} \text{ A.}$$

$$\frac{1}{2} (200 \times 10^{-6}) \left(\frac{20}{0.18}\right) (V_{GS} - V_{TH})^2 = 10^{-3}$$

$$(V_{GS} - V_{TH})^2 = 0.09$$

$$V_{GS} - V_{TH} = 0.3,$$

$$\text{i.e. } V_{GS} = 0.7,$$

Since $V_{GS} = \frac{R_2}{R_1 + R_2} \times 1.8$

$$0.7 = \frac{R_2}{R_1 + R_2} \times 1.8$$

$$0.7 R_1 = . R_2,$$

$$\therefore \frac{R_1}{R_2} = \frac{11}{7}. \quad \text{---} \textcircled{1}$$


To get input impedance $\geq 20k\Omega$.

$$R_1 // R_2 \geq 20k\Omega. \quad \text{---} \textcircled{2}$$

By inspection, setting $R_1 = 55k\Omega$ and $R_2 = 35k\Omega$

will satisfy both $\textcircled{1}$ and $\textcircled{2}$.

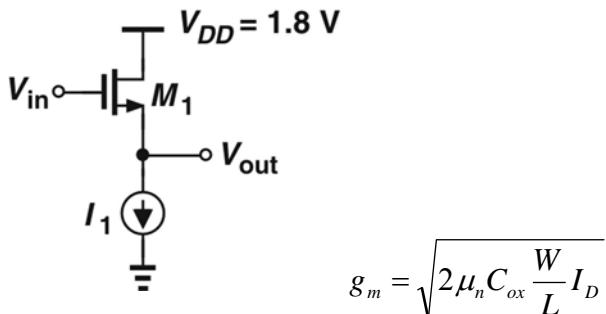4. (8%) The circuit exhibits an output impedance of less than 50Ω with a power budget of 2mW . Determine the W/L. Assume $\lambda=0$, $\mu_n C_{ox}=200\mu\text{A/V}^2$, and the output impedance seen at M_1 is only $1/g_m$.



Ans:

(53) To get $R_{out} = 50\Omega$,

$$\frac{1}{g_m} = 50\Omega$$

$$\therefore g_m = 20 \text{ mS.}$$


$$\begin{aligned} \text{Power } (P) &= 1.8 \times I_{ds} \\ &\approx 2 \times 10^{-3} \text{ W.} \end{aligned}$$

$$\therefore I_{ds} = 1.11 \text{ mA.}$$

$$\therefore g_m = \sqrt{2 \times (200 \times 10^{-6}) / \left(\frac{W}{L}\right) / (1.11 \text{ mA})}$$

$$\therefore \frac{W}{L} = 900 \quad //$$

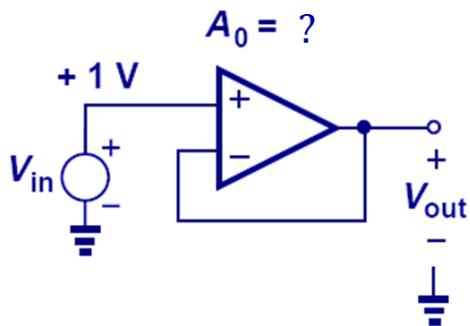5. (6%) A unity-gain buffer shown below. $V_{in+}=1\text{V}$. What value of A_0 is necessary so that the output voltage is equal to 0.9999?



Ans:


$$V_{out} = A_0(V_{in} - V_{out}) \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + A_0} = 0.9999$$

$$\Rightarrow 0.9999 + 0.9999A_0 = A_0$$

$$\Rightarrow 0.0001A_0 = 0.9999$$

$$\Rightarrow A_0 = 9999 \approx 10000$$

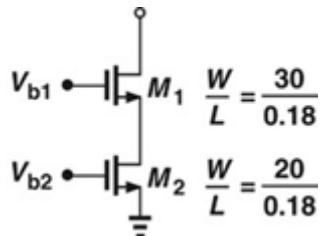6. (12%) An cascade current source as shown below must be designed for a biasing current of 0.5mA. Assume $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, and $V_{TH} = 0.4\text{V}$. (a) (8%) Neglect channel length modulation, compute the required value of V_{b2} . What is the minimum tolerable of V_{b1} if M2 must remain saturation? (b) (4%) Assume $\lambda = 0.1\text{V}^{-1}$. Calculate the output impedance of the circuit.



Ans:

14.

$$(a) \quad I_{D2} = I_{BIAS} = \frac{1}{2} UnCox \left(\frac{W}{L}\right)_2 (V_{b2} - V_{T_H})^2$$

$$\Rightarrow V_{b2} = \sqrt{\frac{2 I_{BIAS}}{UnCox \left(\frac{W}{L}\right)_2}} + V_{T_H}$$

$$= \sqrt{\frac{2(0.5 \text{ mA})}{(100 \frac{\mu\text{A}}{V^2})(\frac{20}{0.18})}} + 0.4 \text{ V} \approx 0.7 \text{ V}$$

M₂ operates in saturation as long as
 $V_{GS2} - V_{TH} \leq V_{DS2} \Rightarrow V_{DS2} \geq 0.3 \text{ V}.$

Observe that $V_{GS1} = V_{b1} - V_{DS2}$

$$I_{D1} = I_{BIAS} = \frac{1}{2} UnCox \left(\frac{W}{L}\right)_1 (V_{b1} - V_{DS2} - V_{T_H})^2$$

$$\Rightarrow V_{b1} \geq \sqrt{\frac{2 I_{BIAS}}{UnCox \left(\frac{W}{L}\right)_1}} + 0.4 \text{ V} + 0.3 \text{ V}$$

$$= \sqrt{\frac{2(0.5 \text{ mA})}{(100 \frac{\mu\text{A}}{V^2})(\frac{30}{0.18})}} + 0.7 \text{ V} \approx 0.95 \text{ V}.$$

∴ Minimum $V_{b1} = 0.95 \text{ V}.$

$$(b) \quad R_{out} = (1 + g_{m1} r_{o2}) r_{o1} + r_{o2}$$


$$= \left(1 + \sqrt{2 UnCox \left(\frac{W}{L}\right)_1 I_{BIAS}} \cdot \frac{1}{2 I_{BIAS}}\right) \cdot \frac{1}{2 I_{BIAS}} + \frac{1}{2 I_{BIAS}}$$

$$= \left[1 + \sqrt{2(100 \frac{\mu\text{A}}{V^2})(\frac{30}{0.18})(0.5 \text{ mA})} \cdot \frac{1}{(0.1)(0.5 \text{ mA})}\right] \cdot \frac{1}{(0.1)(0.5 \text{ mA})}$$

$$+ \frac{1}{(0.1)(0.5 \text{ mA})}$$

$$\approx 1.67 \text{ M}\Omega$$

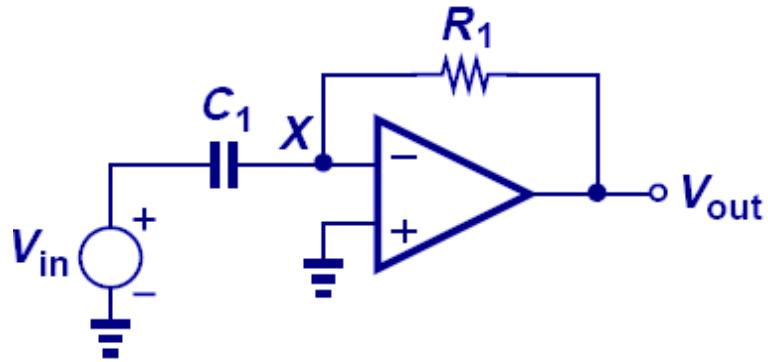7. (6%) A differentiator is shown below. Please find the transfer function.




Ans:

$$\frac{V_{in} - V_X}{\frac{1}{C_1 s}} = \frac{V_X - V_{out}}{R_1} \quad V_X = \frac{V_{out}}{-A_0}$$

$$\frac{V_{out}}{V_{in}} = \frac{-R_1 C_1 s}{1 + \frac{1}{A_0} + \frac{R_1 C_1 s}{A_0}}$$

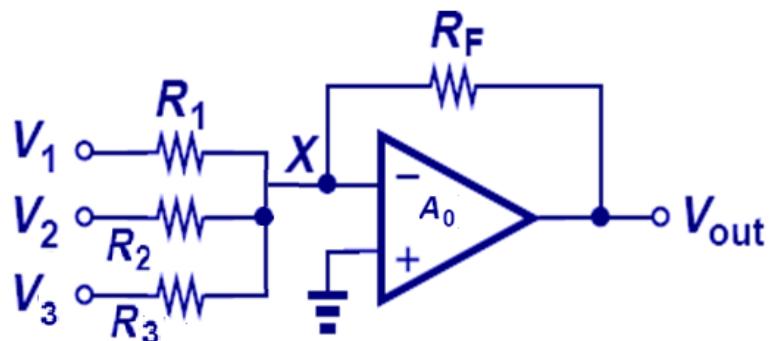8. (6%) Find the output voltage of the following circuit in terms of V_1 , V_2 , V_3 , R_1 , R_2 , R_3 and R_F .



Ans:

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{-V_{out}}{R_F}$$

$$V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

9. (6%) An inverting amplifier must provide an input impedance of approximately $10k\Omega$ and a nominal

gain of 4. If the op amp exhibits an open-loop gain of 1000 and output impedance of $1\text{k}\Omega$, determine the

$$\text{gain error. } \varepsilon = 1 - \frac{A_0 - \frac{R_{out}}{R_1}}{1 + \frac{R_{out}}{R_2} + A_0 + \frac{R_1}{R_2}}$$

Ans:

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{R_1}{R_2} = 4 \Rightarrow R_{in} \approx R_2 = 10\text{K}\Omega$$

$$R_1 = 4R_2 = 40\text{K}\Omega$$

$$\varepsilon = 1 - \frac{A_0 - \frac{R_{out}}{R_1}}{1 + \frac{R_{out}}{R_2} + A_0 + \frac{R_1}{R_2}} = 0.51\%$$

10. (4%) The integrator of Fig. 8.51 must provide a pole at no higher than 2 Hz. If the values of R_1 and C_1 are limited to $5\text{k}\Omega$ and 50nF , respectively, determine the required gain of the op amp.

$$S_p = \frac{-1}{2\pi(A_0 + 1)RC}$$

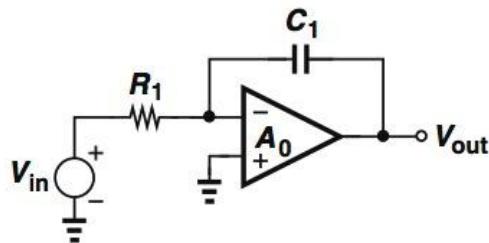



Figure 8.51

Ans:

$$S_p = \frac{-1}{2\pi(A_0 + 1)RC} \leq -2\text{Hz} \Rightarrow 2\pi(A_0 + 1)(5\text{K})(50\text{nF}) \geq 2 \Rightarrow A_0 \geq 1273$$

11. (8%) Determine the output impedance of following two circuits. Assume all transistors operate at


saturation and $g_m r_o \gg 1$.

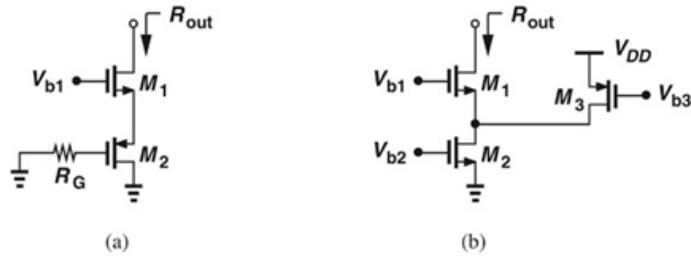

Ans:

19. (a) R_x is the input impedance of a common-gate configuration:

 "Looking into" the source of M_2 ,

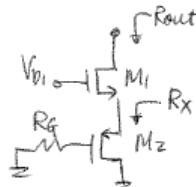

$$R_x = \frac{1}{g_{m2}} \parallel r_{o2}$$

$$\therefore R_{out} = g_{m1} r_o, R_x = g_{m1} r_o, \left(\frac{1}{g_{m2}} \parallel r_{o2} \right)$$


(b) From observation,

$$\rightarrow R_3 = r_{o3} (\because V_{SG} = 0$$

in AC)


$$\rightarrow R_2 = r_{o2} (\because V_{SG} = 0$$

in AC)

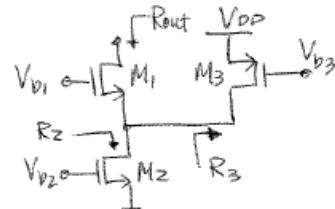

$$\therefore R_{out} = g_{m1} r_o, (R_2 \parallel R_3) = g_{m1} r_o, (r_{o2} \parallel r_{o3})$$

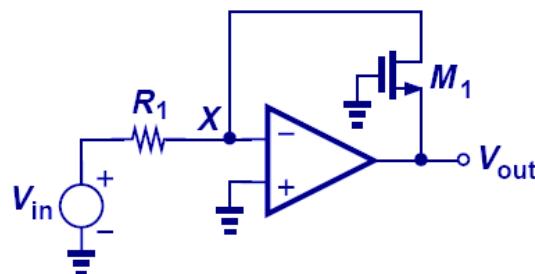12. (6%) Please find the output voltage of the following square root amplifier.




Ans:

$$\frac{V_{in}}{R_1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$V_{out} = - \sqrt{\frac{2V_{in}}{\mu_n C_{ox} \frac{W}{L} R_1}} - V_{TH}$$

$$(V_{GS} = -V_{out})$$

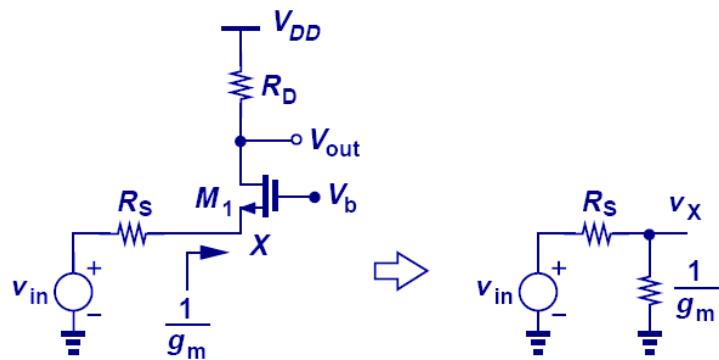13. (6%) Please find the voltage gain of the following Common gate stage with source resistance.




Ans:


$$v_X = \frac{1}{\frac{g_m}{1+R_S} v_{in}} = \frac{1}{1+g_m R_S} v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_X} \frac{v_X}{v_{in}} = \frac{g_m R_D}{1+g_m R_S} = \frac{R_D}{\frac{1}{g_m} + R_S}$$

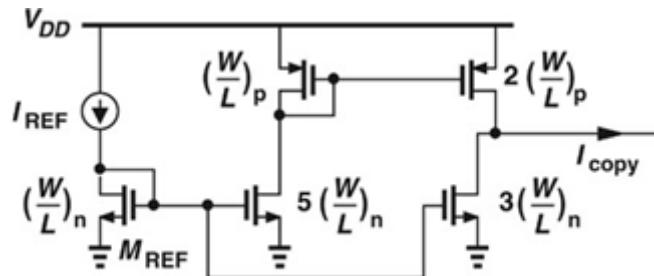14. (6%) Calculate I_{copy} of the following circuit. Assume all of the transistors operate in saturation.



Ans:

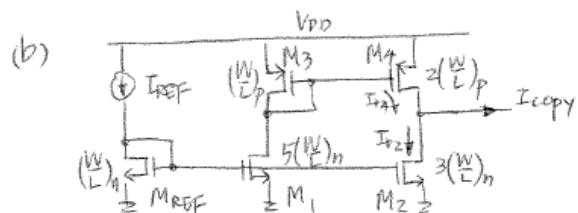

$$V_{GS,REF} = V_{GS,1} \therefore I_{D1} = 5 I_{REF}$$

$$V_{GS,3} = V_{GS,4} \therefore I_{D4} = 2 I_{D3} = 2 I_{D1} = 10 I_{REF}$$

$$V_{GS,REF} = V_{GS,2} \therefore I_{D2} = 3 I_{REF}$$

$$\therefore I_{copy} = I_{D4} - I_{D2} = 7 I_{REF}$$