

國立中山大學 101 學年度第一學期資工系數位系統期末考試

學號：

姓名：

一、選擇與是非題（每題 3 分，12 分）

- () 1. How many address lines are required in a $64M \times 16$ RAM? ①16 ②26 ③30 ④64
- () 2. The master-slave D flip-flop shown in Fig. 1(a) is a positive-edge-triggered flip-flop.
- () 3. The outputs of a Moore state machine are functions of both the present state and inputs.
- () 4. Programmable ROM has a programmable AND array and a fixed OR array.

二、問答題（94 分）

1. Please answer the following problems.

- (1) Fig. 1(a) shows a master-slave D flip-flop. Complete the timing diagram shown in Fig. 1(b). (6%)
- (2) Briefly explain the operations of the 4-bit up/down binary counter shown in Fig. 2. (6%)

2. The state diagram for sequence detector which detects a sequence of two or more consecutive 1's in a string of bits coming through an input line x is shown in Fig. 3(a).

- (1) Complete the state table as shown in Table 1 using natural binary encoding for state assignment (i.e., $S_0 = 00$, $S_1 = 01$, $S_2 = 10$). (5%)
- (2) Use D flip-flops and derive the simplified flip-flop input (excitation) equations and output equation using the K-map. (4%)
- (3) Draw the logic diagram of sequence detector with D flip-flops as shown in Fig. 3(b). (4%)
- (4) Use JK flip-flops and complete the state table and JK flip-flop input as shown in Table 2. (6%)
- (5) Use JK flip-flops and derive the simplified flip-flop input (excitation) equations using the K-map. (6%)
- (6) Draw the logic diagram of sequence detector with JK flip-flops as shown in Fig. 3(c). (4%)

3. Design a serial adder using a JK flip-flop as shown in Fig. 4.

- (1) Complete the state table as shown in Table 3. (8%)
- (2) Derive the simplified flip-flop input (excitation) equations. (6%)
- (3) Draw the logic diagram with a JK flip-flop as shown in Fig. 4. (5%)

4. Design the synchronous sequential circuit using T flip-flops with the state diagram as shown in Fig. 5(a).

- (1) Complete the state table as shown in Table 4. (8%)
- (2) Derive the simplified flip-flop input (excitation) equations. (6%)
- (3) Draw the logic diagram with T flip-flops as shown in Fig. 5(b). (5%)

5. Using an 8×2 ROM shown in Fig. 6 and a $3 \times 4 \times 2$ PLA shown in Fig. 7, implement the truth table shown in Table 5. (15%)

 


Table 1

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Table 2

Present State		Input	Next State		Flip-Flop Inputs			
A	B	x	A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	1	0	0	0	0
0	1	1	0	1	0	0	0	1
1	0	0	1	0	0	0	1	0
1	0	1	1	0	0	0	1	0
1	1	0	1	1	0	0	0	0
1	1	1	1	1	1	0	0	1

國立中山大學 101 學年度第一學期資工系數位系統期末考試

學號：

姓名：

Flip-flop	D	JK	T																																																								
characteristic equation	$Q(t+1) = D$	$Q(t+1) = JQ' + K'Q$	$Q(t+1) = T \oplus Q$																																																								
characteristic table	<table border="1"> <thead> <tr> <th>D</th> <th>Q(t+1)</th> <th>J</th> <th>K</th> <th>Q(t+1)</th> <th>T</th> <th>Q(t+1)</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>Q(t)</td> <td>0</td> <td>Q(t)</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> <td>Q'(t)</td> </tr> <tr> <td></td> <td></td> <td>1</td> <td>0</td> <td>1</td> <td></td> <td></td> </tr> <tr> <td></td> <td></td> <td>1</td> <td>1</td> <td>Q'(t)</td> <td></td> <td></td> </tr> </tbody> </table>	D	Q(t+1)	J	K	Q(t+1)	T	Q(t+1)	0	0	0	0	Q(t)	0	Q(t)	1	1	0	1	0	1	Q'(t)			1	0	1					1	1	Q'(t)			<table border="1"> <thead> <tr> <th>J</th> <th>K</th> <th>Q(t+1)</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>Q(t)</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>Q'(t)</td> </tr> </tbody> </table>	J	K	Q(t+1)	0	0	Q(t)	0	1	0	1	0	1	1	1	Q'(t)	<table border="1"> <thead> <tr> <th>T</th> <th>Q(t+1)</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>Q(t)</td> </tr> <tr> <td>1</td> <td>Q'(t)</td> </tr> </tbody> </table>	T	Q(t+1)	0	Q(t)	1	Q'(t)
D	Q(t+1)	J	K	Q(t+1)	T	Q(t+1)																																																					
0	0	0	0	Q(t)	0	Q(t)																																																					
1	1	0	1	0	1	Q'(t)																																																					
		1	0	1																																																							
		1	1	Q'(t)																																																							
J	K	Q(t+1)																																																									
0	0	Q(t)																																																									
0	1	0																																																									
1	0	1																																																									
1	1	Q'(t)																																																									
T	Q(t+1)																																																										
0	Q(t)																																																										
1	Q'(t)																																																										
excitation table	<table border="1"> <thead> <tr> <th>Q(t)</th> <th>Q(t = 1)</th> <th>J</th> <th>K</th> <th>Q(t)</th> <th>Q(t = 1)</th> <th>T</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>X</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>X</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>X</td> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	Q(t)	Q(t = 1)	J	K	Q(t)	Q(t = 1)	T	0	0	0	X	0	0	0	0	1	1	X	0	1	1	1	0	X	1	1	0	1	1	1	X	0	1	1	0																							
Q(t)	Q(t = 1)	J	K	Q(t)	Q(t = 1)	T																																																					
0	0	0	X	0	0	0																																																					
0	1	1	X	0	1	1																																																					
1	0	X	1	1	0	1																																																					
1	1	X	0	1	1	0																																																					

 


Fig. 1(a)

Fig. 1(b)

 
 


Fig. 2

 


Fig. 3(b)

 


Fig. 3(c)

 


Fig. 4

 


Fig. 5(a)

Table 4

Present State			Next State			Flip-Flop Inputs		
A ₂	A ₁	A ₀	A ₂	A ₁	A ₀	T _{A2}	T _{A1}	T _{A0}

Table 3

Present State	Inputs	Next State	Output	Flip-Flop Inputs
Q	x y	Q	s	J _Q K _Q
0	0 0	0	0	
0	0 1	0	1	
0	1 0	1	0	
0	1 1	1	1	
1	0 0	0	0	
1	0 1	0	1	
1	1 0	1	0	
1	1 1	1	1	

 


Fig. 7

 


Fig. 6

A	B	C	F ₁	F ₂
0	0	0	1	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

Table 5

 


Fig. 5(b)