

Name:

ID#

1. (10%) A cellphone incorporates a 2.4GHz oscillator whose frequency is defined by the resonance frequency of an LC tank. If the tank capacitance is realized as the pn junction of Example 2.15, calculate the change in the oscillation frequency while the reverse voltage goes from 0 to 1.5 V. Assume the circuit operates at 2.4 GHz at a reverse voltage of 0 V, and the junction area is $2500 \mu\text{m}^2$.

$$f_{res} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}, C_j = 0.265 \text{ fF} / \mu\text{m}^2, C_{j,tot} = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_0}}}, V_0 = 0.73 \text{ V}$$

Ans:

$$jL\omega_{res} = -(jC\omega_{res})^{-1} \quad f_{res} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

$$\text{at } V_R = 0 \text{ V and } C_j = 0.265 \text{ fF} / \mu\text{m}^2$$

$$C_{j,tot} (V_R = 0) = (0.265 \text{ fF} / \mu\text{m}^2) \times (2500 \mu\text{m}^2) = 662.5 \text{ fF}$$

$$f_{res} = 2.4 \text{ GHz} = \frac{1}{2\pi} \frac{1}{\sqrt{L \times 662.5 \text{ fF}}}, L = 6.64 \text{ nH}$$

$$\text{if } V_R = 1.5 \text{ V} \quad C_{j,tot} = \frac{C_{j0}}{\sqrt{1 + \frac{1.5}{0.73}}} \times 2500 \mu\text{m}^2 = 379 \text{ fF}$$

$$f_{res} (V_R = 1.5) = \frac{1}{2\pi} \frac{1}{\sqrt{L \times 379 \text{ fF}}} = 3.17 \text{ GHz}$$

2. (10%). An NMOS device with $\lambda = 0.1 \text{ V}^{-1}$ must provide a $g_m r_o$ of 20 with $V_{DS} = 1.5 \text{ V}$. Determine the required value of W/L if $I_D = 0.5 \text{ mA}$. Assume $\mu_n C_{ox} = 200 \mu\text{A} / \text{V}^2$, and $V_{TH} = 0.4 \text{ V}$. $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$,

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \quad r_o = \frac{1}{\lambda I_D}$$

Ans:

3b. Given NMOS with $\lambda = 0.1 \text{ V}^{-1}$ $g_m r_o = 20$
 $V_{DS} = 1.5 \text{ V}$
determine W/L if $I_D = 0.5 \text{ mA}$.


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 \text{ V}^{-1})(0.5 \text{ mA})} = 20 \text{ k}\Omega$$

$$\Rightarrow g_m = \frac{20}{20 \text{ k}\Omega} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$


$$\therefore \frac{W}{L} = \left(\frac{20}{20 \text{ k}\Omega}\right)^2 \frac{1}{2\mu_n C_{ox} I_D} \\ = \left(\frac{1}{1 \text{ k}\Omega}\right)^2 \frac{1}{2(200 \mu\text{A} / \text{V}^2)(0.5 \text{ mA})} \approx 5.$$

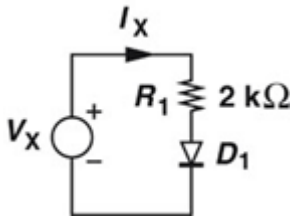3. (10%) Suppose D_1 must sustain a voltage 850 mV for $V_X = 2.0$ V. $R_1 = 2.0$ k Ω . Calculate the required I_S .

$$V_T = 26\text{mV}, I_D = I_S \exp^{\frac{V_D}{V_T}}$$



21.

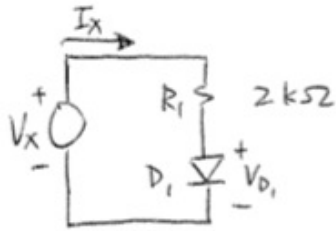


Given: @ $V_X = 2$ V, $V_{D_1} = 850$ mV

$$\Rightarrow I_X = \frac{V_X - V_{D_1}}{R_1} = 0.58 \text{ mA}$$


$$\begin{aligned} \therefore I_S &= \frac{I_X}{(e^{V_{D_1}/V_T} - 1)} \approx I_X \exp[-V_{D_1}/V_T] \\ &= (0.58 \text{ mA}) \exp[-0.85/0.026] \approx 3.64 \cdot 10^{-18} \text{ A} \end{aligned}$$

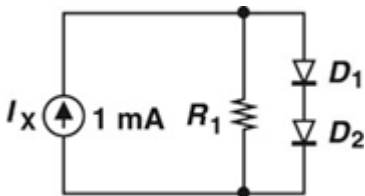4. (10%) In the following circuit, determine the value of R_1 such that this resistor carries 0.5 mA.

Assume $I_S = 5 \times 10^{-16}$ A for each diode. $V_T = 26$ mV, $I_D = I_S \exp^{\frac{V_D}{V_T}}$



29.

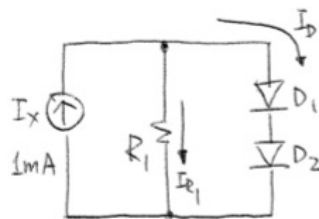

Given $I_{R_1} = 0.5$ mA,
 $I_S = 5 \cdot 10^{-16}$ A for
each diode.


Find R_1 .

$$\text{By KCL, } I_D = I_X - I_{R_1} = 0.5 \text{ mA}$$

$$\begin{aligned} \Rightarrow V_{D_1} = V_{D_2} &= V_T \ln\left(\frac{I_D}{I_S}\right) = 0.026 \ln\left(\frac{0.5 \text{ mA}}{5 \cdot 10^{-16} \text{ A}}\right) \\ &\approx 0.718 \text{ V} \end{aligned}$$

$$\therefore R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{2 V_{D_1}}{I_{R_1}} = \frac{2(0.718 \text{ V})}{0.5 \text{ mA}} = 2.87 \text{ k}\Omega$$

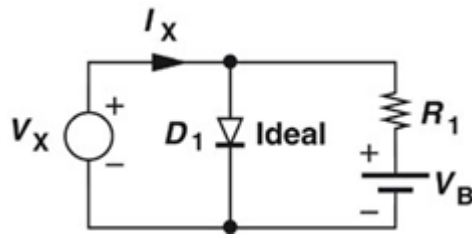
5. (10%) For the circuits shown below, choose the correct I_X/V_X characteristic for $V_B=+1V$ and $V_B=-1V$




Ans:

$$I_X = \begin{cases} \frac{V_X - V_B}{R_1} & V_X < 0 \\ \infty & V_X > 0 \end{cases}$$

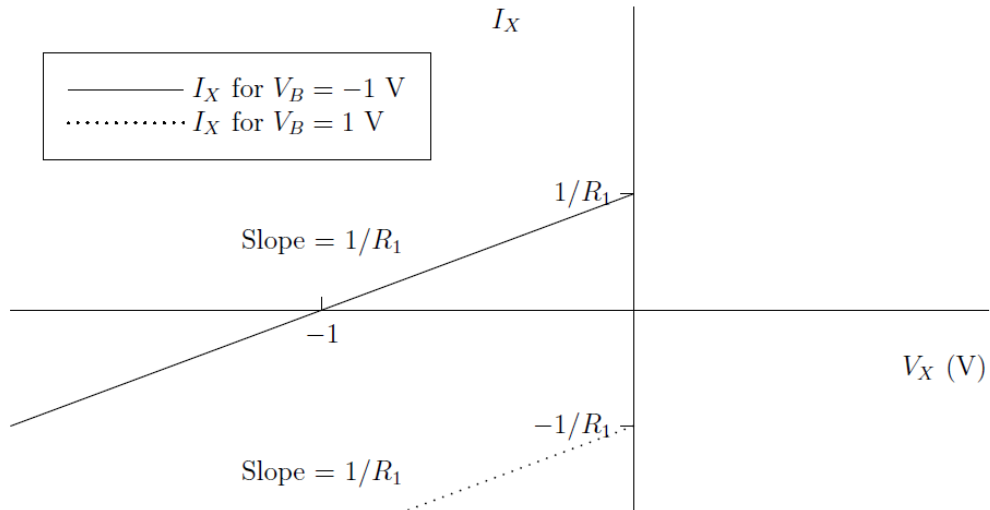
Plotting I_X vs. V_X for $V_B = -1V$ and $V_B = 1V$, we get:



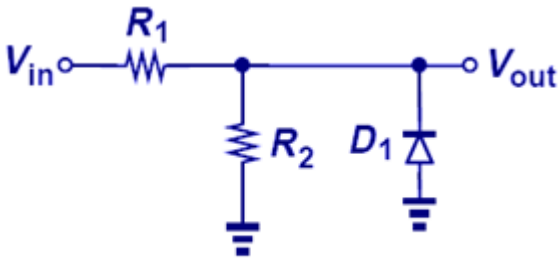6. (10%) Using the constant voltage mode, plot the input/output characteristic of the following circuit.




Ans:

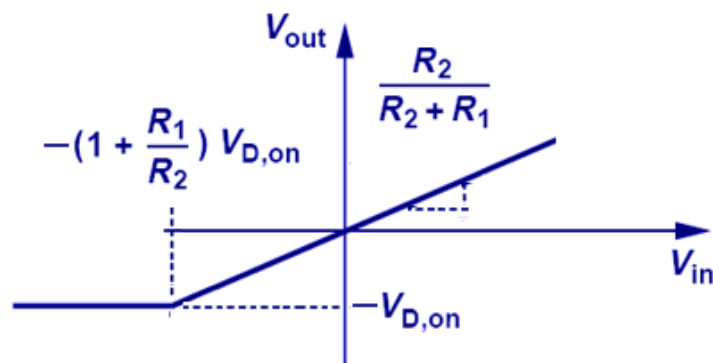

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in} = -V_{D,on} \Rightarrow V_{in} = -\left(1 + \frac{R_1}{R_2}\right) V_{D,on}$$

7. (10%) If $W/L = 10/0.18$ and $\lambda=0$, determine the operating point of M_1 in the following circuit.

$$\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2, \text{ and } V_{TH} = -0.4\text{V}. \quad I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2$$

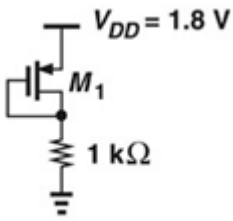

Ans:

(b) Since M_1 is diode-connected, we know it is operating in saturation.

$$|V_{GS}| = |V_{DS}|$$


$$V_{DD} - |V_{GS}| = |I_D|(1 \text{ k}\Omega) = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 (1 \text{ k}\Omega)$$

$$|V_{GS}| = |V_{DS}| = \boxed{0.952 \text{ V}}$$

$$|I_D| = \boxed{848 \mu\text{A}}$$

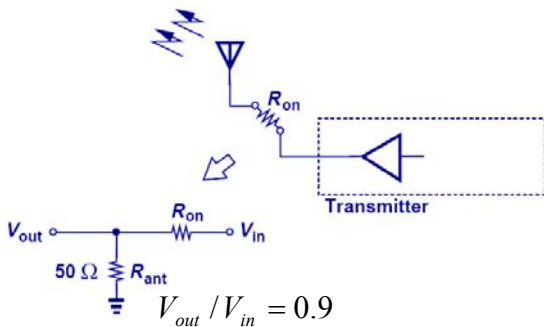8. (10%) The switch connecting the transmitter to the antenna attenuates the signal by no more than 10%. If $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, and $V_{TH} = 0.4\text{V}$, and the W/L is 1500, determine the minimum required V_{GS} of the switch.

Assume the antenna can be model as a 50Ω resistor. $R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$




Ans:

$$V_{out} = \frac{R_{ant}}{R_{ant} + R_{on}} = \frac{50}{50 + R_{on}} = 0.90, R_{on} = 5.6$$

$$R_{on} = \frac{1}{\mu_n C_{ox} (W/L)(V_{GS} - V_{TH})} = 5.6 = \frac{1}{200 \times 10^{-6} \times 1500 \times (V_{GS} - 0.4)}$$

$$V_{GS} = 0.995\text{V}$$

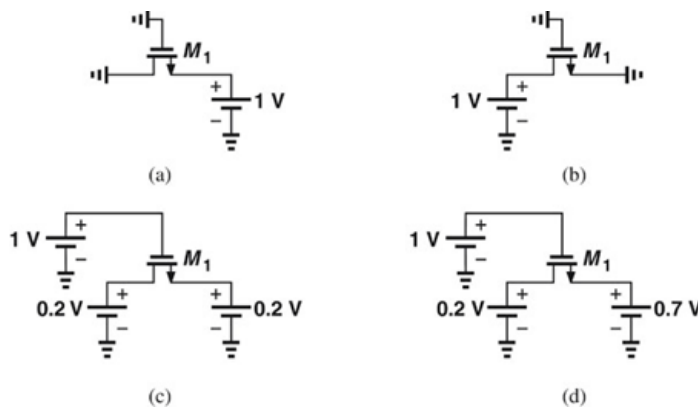9. (10%) Please determine the region of M1 in each circuit. Assume $V_{TH}=0.4V$, ($V_{GS} < V_{TH}$, MOS is at OFF region, $V_{DS} > V_{GS} - V_{TH}$ MOS at saturation region, $V_{DS} < V_{GS} - V_{TH}$, MOS at triode region)




Ans:


20. (a) OFF $\because V_{GS} = 0$ ($V_{GS} < V_{TH}$)
 (b) OFF $\because V_{GS} = 0$ ($V_{GS} < V_{TH}$)
 (c) TRIODE (LINEAR) $\because V_{GS} > V_{TH}$ &
 $V_{DS} < 2(V_{GS} - V_{TH})$
 (d) SATURATION $\because V_{GS} > V_{TH}$ & $V_{DS} > V_{GS} - V_{TH}$

10. (10%)

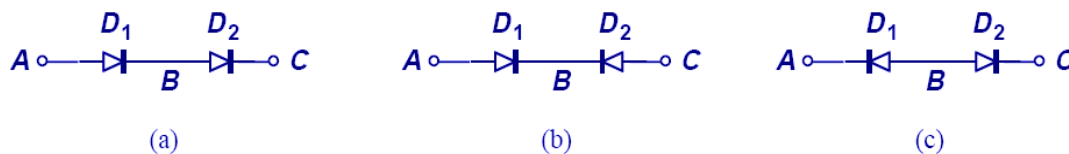- (a) Which semiconductor is the pure silicon, high resistance? (a) Intrinsic (b) Extrinsic
- (b) What type of semiconductor does emphasize the abundance of free holes ? (a) n-type (b) p-type
- (a) Which one of the following figure can conduct current from A to C?



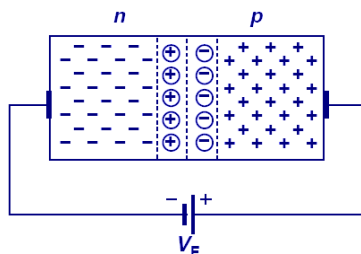- (a) What is the bias condition of the following figure ? (a) forward bias (b) reverse bias



- (b) Which is the node of anode of diode in the following figure ? (a) A (b) B

