

Name:

ID#

1. (10%) A cellphone incorporates a 2.4GHz oscillator whose frequency is defined by the resonance frequency of an LC tank. If the tank capacitance is realized as the pn junction of Example 2.15, calculate the change in the oscillation frequency while the reverse voltage goes from 0 to 1.5 V. Assume the circuit operates at 2.4 GHz at a reverse voltage of 0 V, and the junction area is 2500 μm².

$$f_{res} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}, C_j = 0.265 \text{ fF} / \mu\text{m}^2, C_{j,tot} = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_0}}}, V_0 = 0.73\text{V}$$

Ans:


2. (10%). An NMOS device with λ=0.1V⁻¹ must provide a g_mr_o of 20 with V_{DS}=1.5V. Determine the required value of W/L if I_D=0.5mA. Assume μ_nC_{ox}=200uA/V², and V_{TH}=0.4V. $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$,

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \quad r_o = \frac{1}{\lambda I_D}$$

Ans:

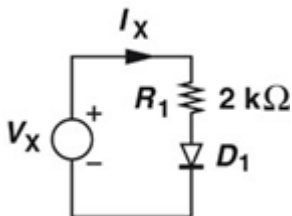
3. (10%) Suppose D₁ must sustain a voltage 850 mV for V_X = 2.0 V. R₁ = 2.0 kΩ. Calculate the required I_S.

$$V_T = 26\text{mV}, I_D = I_S \exp^{\frac{V_D}{V_T}}$$



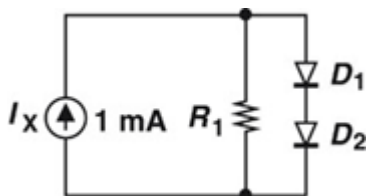
4. (10%) In the following circuit, determine the value of R₁ such that this resistor carries 0.5 mA.

$$\text{Assume } I_S = 5 \times 10^{-16} \text{ A for each diode. } V_T = 26\text{mV}, I_D = I_S \exp^{\frac{V_D}{V_T}}$$




5. (10%) Please plot the input/output characteristic of the circuit assuming a constant voltage model (V_{D,on}).

Ans:

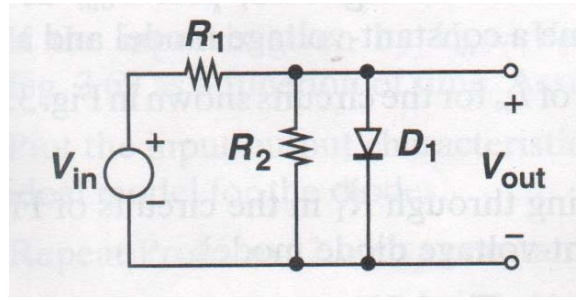

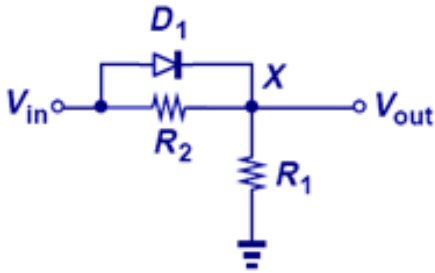
6. (10%) Using the constant voltage mode, plot the input/output characteristic of the following circuit.



Ans:

7. (10%) If $W/L = 10/0.18$ and $\lambda=0$, determine the operating point of M_1 in the following circuit.


$$\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2, \text{ and } V_{TH} = -0.4\text{V}. \quad I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2$$

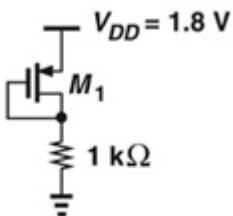

Ans:

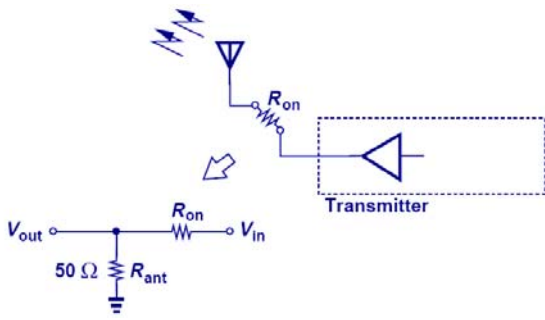
8. (5%) The switch connecting the transmitter to the antenna attenuates the signal by no more than 10%. If $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, and $V_{TH} = 0.4\text{V}$, and the W/L is 1500, determine the minimum required V_{GS} of the switch.

Assume the antenna can be model as a 50Ω resistor.
$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$



Ans:

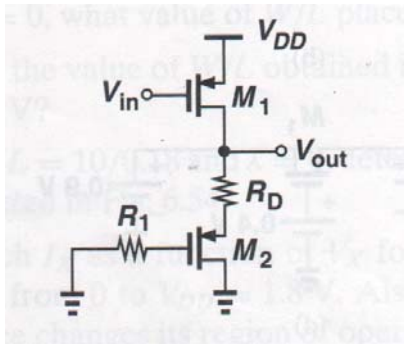9.
 10. (5%) Construct the small signal model of circuit, if all transistor operate in saturation and $\lambda \neq 0$.



Ans:

11. (10%) This circuit employs two identical diodes with $I_S = 5 \times 10^{-16}$ A. Calculate the voltage across R_1 for $I_X = 2$ mA. Assume $R_1 = 2.0$ k Ω .

