

Name: ID#

1. (10%) A cellphone incorporates a 2.4GHz oscillator whose frequency is defined by the resonance frequency of an *LC* tank. If the tank capacitance is realized as the *pn* junction of Example 2.15, calculate the change in the oscillation frequency while the reverse voltage goes from 0 to 1.5 V. Assume the circuit operates at 2.4 GHz at a reverse voltage of 0 V, and the junction area is 2500 μm^2 .

$$f_{res} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} , C_j = 0.265 \text{ fF}/\mu\text{m}^2 , C_{j,tot} = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_0}}} , V_0 = 0.73 \text{ V}$$

Ans:

$$jL\omega_{res} = -(jC\omega_{res})^{-1} \quad f_{res} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

at $V_R = 0 \text{ V}$ and $C_j = 0.265 \text{ fF}/\mu\text{m}^2$

$$C_{j,tot} = (V_R = 0) = (0.265 \text{ fF}/\mu\text{m}^2) \times (2500 \mu\text{m}^2) = 662.5 \text{ fF}$$

$$f_{res} = 2.4 \text{ GHz} = \frac{1}{2\pi} \frac{1}{\sqrt{L \times 662.5 \text{ fF}}} , L = 6.64 \text{ nH}$$

$$\text{if } V_R = 1.5 \text{ V} \quad C_{j,tot} = \frac{C_{j0}}{\sqrt{1 + \frac{1.5}{0.73}}} \times 2500 \mu\text{m}^2 = 379 \text{ fF}$$

$$f_{res}(V_R = 1.5) = \frac{1}{2\pi} \frac{1}{\sqrt{L \times 379 \text{ fF}}} = 3.17 \text{ GHz}$$

2. (10%). An NMOS device with $\lambda=0.1 \text{ V}^{-1}$ must provide a $g_m r_o$ of 20 with $V_{DS}=1.5 \text{ V}$. Determine the required value of W/L if $I_D=0.5 \text{ mA}$. Assume $\mu_n C_{ox}=200 \mu\text{A/V}^2$, and $V_{TH}=0.4 \text{ V}$. $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$,

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \quad r_o = \frac{1}{\lambda I_D}$$

Ans:

Given NMOS with $\lambda = 0.1 \text{ V}^{-1}$ $g_m r_o = 20$
 $V_{DS} = 1.5 \text{ V}$

determine W/L if $I_D = 0.5 \text{ mA}$.


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 \text{ V}^{-1})(0.5 \text{ mA})} = 20 \text{ k}\Omega$$

$$\Rightarrow g_m = \frac{20}{20 \text{ k}\Omega} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\begin{aligned} \therefore \frac{W}{L} &= \left(\frac{20}{20 \text{ k}\Omega}\right)^2 \frac{1}{2 \mu_n C_{ox} I_D} \\ &= \left(\frac{1}{1 \text{ k}\Omega}\right)^2 \frac{1}{2 \left(200 \frac{\mu\text{A}}{\text{V}^2}\right) \left(0.5 \text{ mA}\right)} \approx 5. \end{aligned}$$

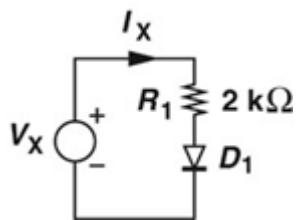3. (10%) Suppose D_1 must sustain a voltage 850 mV for $V_x = 2.0$ V. $R_1 = 2.0$ k Ω . Calculate the required I_s .

$$V_T = 26\text{mV}, \quad I_D = I_s \exp^{\frac{V_D}{V_T}}$$



Given: @ $V_x = 2\text{V}$, $V_{D_1} = 850\text{mV}$


$\Rightarrow I_x = \frac{V_x - V_{D_1}}{R_1} = 0.58\text{mA}$

$$\therefore I_s = \frac{I_x}{(e^{V_{D_1}/V_T} - 1)} \approx I_x \exp[-V_{D_1}/V_T]$$

$$= (0.58\text{ mA}) \exp[-0.85/0.026] \approx 3.64 \cdot 10^{-18}\text{A}$$

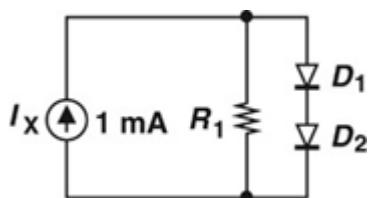4. (10%) In the following circuit, determine the value of R_1 such that this resistor carries 0.5 mA.

Assume $I_s = 5 \times 10^{-16}\text{A}$ for each diode. $V_T = 26\text{mV}$, $I_D = I_s \exp^{\frac{V_D}{V_T}}$



Given $I_{R_1} = 0.5\text{mA}$,
 $I_s = 5 \cdot 10^{-16}\text{A}$ for
each diode.

Find R_1 .

$$\text{By KCL, } I_D = I_x - I_{R_1} = 0.5\text{mA}$$


$$\Rightarrow V_{D_1} = V_{D_2} = V_T \ln\left(\frac{I_D}{I_s}\right) = 0.026 \ln\left(\frac{0.5\text{mA}}{5 \cdot 10^{-16}\text{A}}\right)$$

$$\approx 0.718\text{ V}$$

$$\therefore R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{2V_{D_1}}{I_{R_1}} = \frac{2(0.718\text{V})}{0.5\text{mA}} = 2.87\text{ k}\Omega$$


5. (10%) Please plot the input/output characteristic of the circuit assuming a constant voltage model ($V_{D,on}$).

Ans:

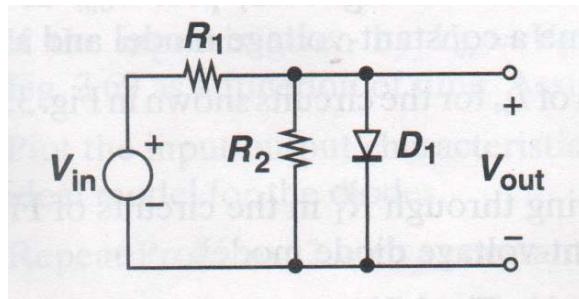


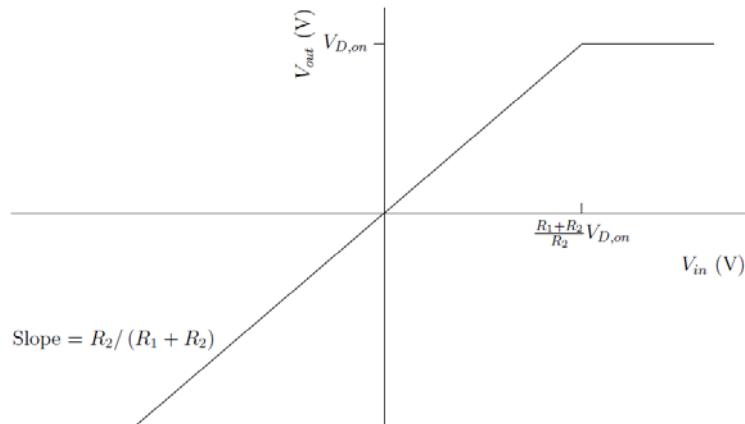3.23 (a)




$$V_{out} = \begin{cases} \frac{R_2}{R_1+R_2} V_{in} & V_{in} < \frac{R_1+R_2}{R_2} V_{D,on} \\ V_{D,on} & V_{in} > \frac{R_1+R_2}{R_2} V_{D,on} \end{cases}$$



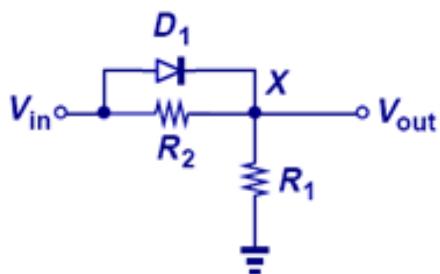6. (10%) Using the constant voltage mode, plot the input/output characteristic of the following circuit.



Ans:

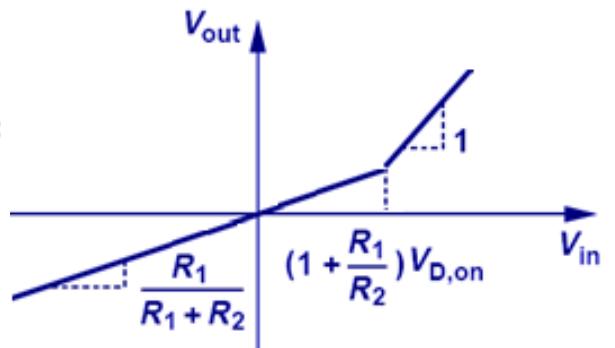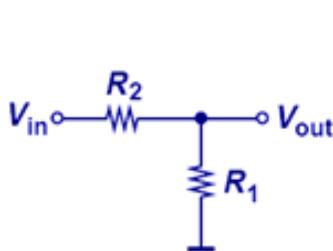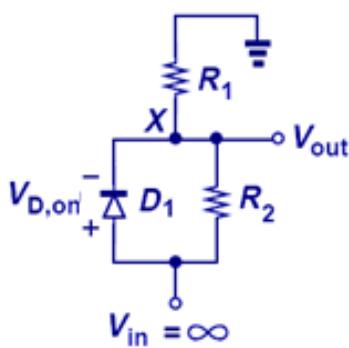


$$V_{in} = V_{D, on} + V_{out} \quad I_{R2} = \frac{V_{D, on}}{R_2} \quad I_{R1} = \frac{V_{X} - 0}{R_1} = \frac{(V_{in} - V_{D, on})}{R_1}$$

$$\frac{V_{D, on}}{R_2} = \frac{(V_{in} + V_{D, on})}{R_1}$$

$$V_{in} = (1 + \frac{R_1}{R_2}) V_{D, on} \quad V_{out} = \frac{R_1}{R_1 + R_2} V_{in}$$

7. (10%) If $W/L = 10/0.18$ and $\lambda=0$, determine the operating point of M_1 in the following circuit. $\mu_p C_{ox} = 100 \mu\text{A/V}^2$, and $V_{TH} = -0.4\text{V}$. $I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2$

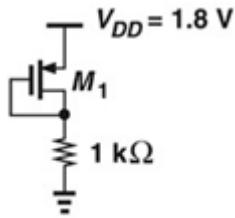


Ans:

(b) Since M_1 is diode-connected, we know it is operating in saturation.

$$\begin{aligned} |V_{GS}| &= |V_{DS}| \\ V_{DD} - |V_{GS}| &= |I_D|(1 \text{ k}\Omega) = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 (1 \text{ k}\Omega) \\ |V_{GS}| &= |V_{DS}| = 0.952 \text{ V} \\ |I_D| &= 848 \mu\text{A} \end{aligned}$$

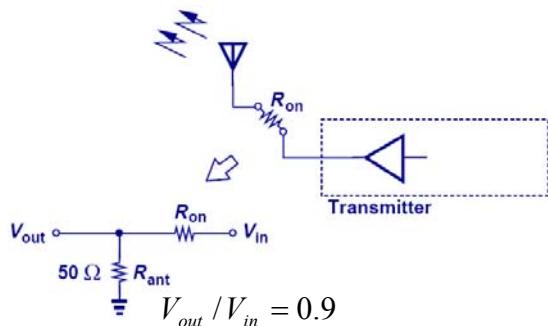8. (5%) The switch connecting the transmitter to the antenna attenuates the signal by no more than 10%. If $\mu_n C_{ox} = 200 \mu\text{A/V}^2$, and $V_{TH} = 0.4\text{V}$, and the W/L is 1500, determine the minimum required V_{GS} of the switch.

Assume the antenna can be model as a 50Ω resistor. $R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$



Ans:


$$V_{out} = \frac{R_{ant}}{R_{ant} + R_{on}} = \frac{50}{50 + R_{on}} = 0.90, R_{on} = 5.6$$

$$R_{on} = \frac{1}{\mu_n C_{ox} (W/L) (V_{GS} - V_{TH})} = 5.6 = \frac{1}{200 \times 10^{-6} \times 1500 \times (V_{GS} - 0.4)}$$


$$V_{GS} = 0.995V$$

9.

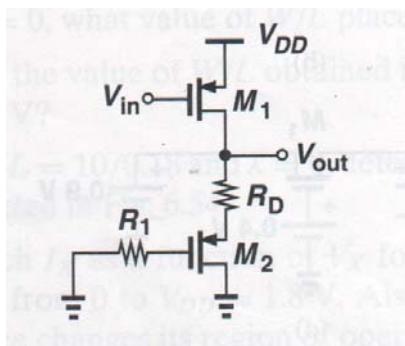
10. (5%) Construct the small signal model of circuit, if all transistor operate in saturation and $\lambda \neq 0$.




Ans:

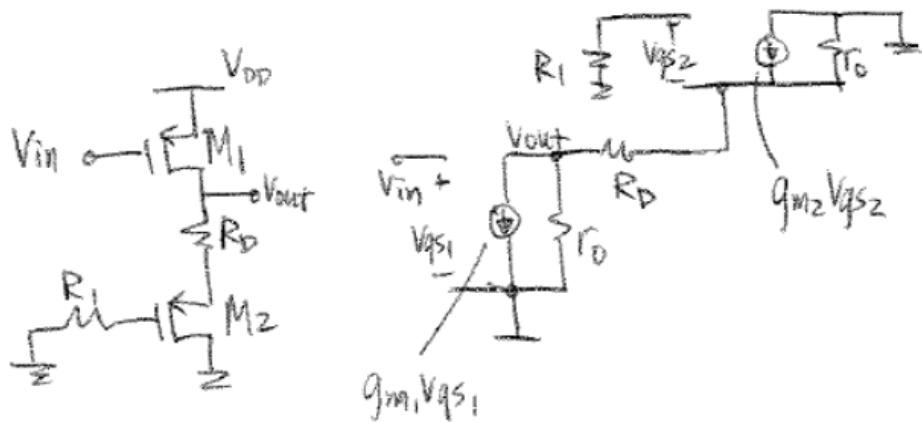

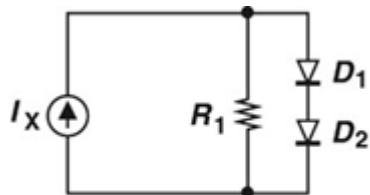11.(10%) This circuit employs two identical diodes with $I_s = 5 \times 10^{-16} \text{ A}$. Calculate the voltage across R_1 for $I_x = 2 \text{ mA}$. Assume $R_L = 2.0 \text{ k}\Omega$.



28.

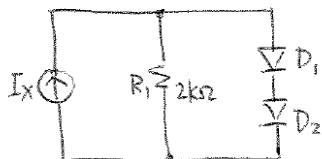

Given $D_1 = D_2$ with
 $I_s = 5 \cdot 10^{-16} \text{ A}$

Find V_{R_1} for $I_x = 2 \text{ mA}$.

Current through the diodes = I_D
 $= I_x - \frac{V_{R_1}}{R_1}$ where V_{R_1} = voltage across R_1 ,

$$\Rightarrow V_{R_1} = 2 \cdot V_T \ln \left(\frac{I_D}{I_s} \right) = 2 \left[V_T \ln \left(\frac{I_x}{I_s} - \frac{V_{R_1}}{I_s R_1} \right) \right]$$

$$V_{R_1} = 1.4 \text{ V} \Rightarrow I_D = I_x - \frac{V_{R_1}}{R_1} = 2 \text{ mA} - \frac{1.4 \text{ V}}{2 \text{ k}\Omega} = 1.3 \text{ mA}$$

$$\Rightarrow V_{R_1} = 2V_T \ln\left(\frac{I_D}{I_S}\right)$$

$$= 2(0.026 \text{ V}) \ln\left(\frac{1.3 \text{ mA}}{5 \cdot 10^{-6} \text{ A}}\right) \approx 1.49 \text{ V}$$

$$V_{R_1} = 1.49 \text{ V} \Rightarrow I_D = 2 \text{ mA} - \frac{1.49}{2 \text{ k}\Omega} = 1.26 \text{ mA}$$

$$\Rightarrow V_{R_1} = 2(0.026 \text{ V}) \ln\left(\frac{1.26 \text{ mA}}{5 \cdot 10^{-6} \text{ A}}\right) \approx 1.48 \text{ V}$$

$$V_{R_1} = 1.48 \text{ V} \Rightarrow I_D = 2 \text{ mA} - \frac{1.48 \text{ V}}{2 \text{ k}\Omega} = 1.26 \text{ mA}$$

$$\Rightarrow V_{R_1} = 1.48 \text{ V}$$

\therefore voltage across $R_1 = 1.48 \text{ V}$