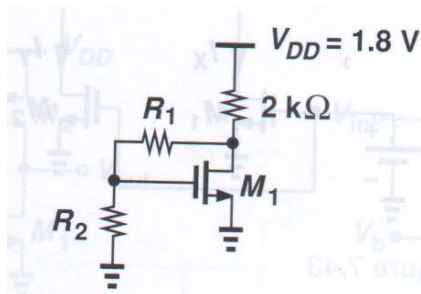


Name: ID#

$\mu_n C_{ox} = 200 \mu A/V^2$, $\mu_p C_{ox} = 100 \mu A/V^2$, NMOS $V_{TH} = 0.4 V$, PMOS $V_{TH} = -0.4 V$,

$I_D = (1/2) \mu_n C_{ox} (W/L) (V_{GS} - V_{TH})^2$, $g_m = [2 \mu_n C_{ox} (W/L) I_D]^{1/2}$, $r_o = [1/(\lambda I_D)]$

1. (10%) $I_D = 0.5 mA$, $W/L = 50/0.18$. Find R_1 and R_2 such that current of resistors is $0.05 mA$.



$$I_{D_s} = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2$$

$$0.5 \times 10^{-3} = (100 \times 10^{-6}) \left(\frac{50}{0.18}\right) (V_{GS} - V_{TH})^2$$

$$\therefore V_{GS} = 0.534 V$$

Ans:

$$\therefore R_2 = \frac{0.534}{0.05 \times 10^{-3}}$$


$$R_2 = \underline{\underline{10.68 k\Omega}}$$

$$\therefore V_{D1} = 1.8 - (0.1 \times I_{D_s} \times 2 k\Omega) = 0.1 I_{D_s} (R_1 + R_2),$$

$$\therefore 14 k\Omega = R_1 + 10.68 k\Omega.$$

$$\therefore R_1 = \underline{\underline{3320 \Omega}}$$

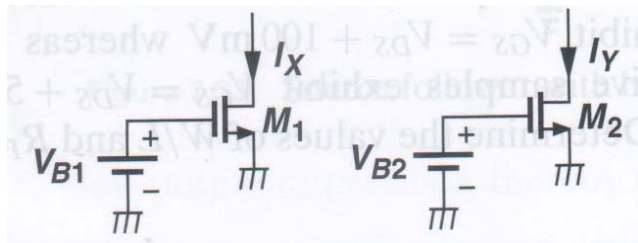2. (10%) $I_X = I_Y = 0.6 mA$. If $V_{B1} = 1.1 V$, $V_{B2} = 1.0 V$, $\lambda = 0.1 V^{-1}$ and $L_1 = L_2 = 0.25 \mu m$, calculate W_1 and W_2 . Calculate output resistance of these current sources.



Ans:

$$I_x = \frac{\beta_n}{2} (V_{GS} - V_m)^2$$

$$0.6 mA = \frac{\mu_n C_{ox} \times W_1}{2 \times L_1} (V_m - V_m)^2 = \frac{200 \times 10^{-6}}{2} \times \frac{W_1}{0.25 \times 10^{-6}} \times (1.1 - 0.4)^2 = 196 W_1$$

$$\Rightarrow W_1 = 3 \mu m.$$


$$I_y = \frac{\beta_n}{2} (V_{GS} - V_t)^2 = \frac{200 \times 10^{-6}}{2} \times \frac{W_2}{0.25 \times 10^{-6}} \times (1 - 0.4)^2 = 144 W_2$$

$$\Rightarrow W_2 = \frac{0.6 mA}{144} = 4 \mu m.$$

es

$$R_{out1} = R_{out2} = \frac{1}{\lambda I_D} = \frac{1}{0.1 \times 0.6 \times 10^{-3}} = 16.67 k\Omega.$$

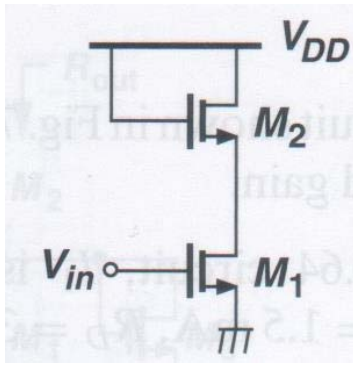3. (10%) $I_D = 1 \text{ mA}$, $(W/L)_2 = 5/1$, $(W/L)_1 = 10/1$, $\lambda_1 = 0.1 \text{ V}^{-1}$, $\lambda_2 = 0.1 \text{ V}^{-1}$, calculate R_{out}



Ans:


$$r_{O2} = \frac{1}{\lambda I_D} = \frac{1}{0.1 \times 10^{-3}} = 10 \text{ k}\Omega$$

$$r_{O1} = \frac{1}{\lambda I_D} = 10 \text{ k}\Omega$$

$$g_{m2} = \sqrt{2 \times 200 \times 10^{-6} \times \frac{5}{1} \times 1 \times 10^{-3}} = 0.00141 \text{ S}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{O2} \parallel r_{O1} = 709 \parallel 10 \text{ k}\Omega \parallel 10 \text{ k}\Omega \approx 709 \Omega$$

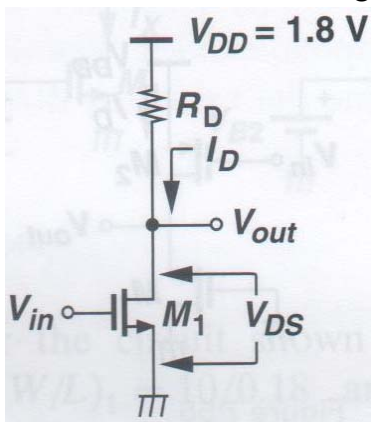4. (10%) determine the gate voltage at which M_2 operates at the edge of saturation.



Ans:

Solution We know at the edge of saturation of M_1

$$(V_{GS} - V_t) = V_{DS}$$

Here,

$$(V_{in} - 0) = V_{GS}$$

So, $(V_{in} - V_t) = V_{DS}$. Therefore,


$$\begin{aligned} V_{DS} &= V_{DD} - I_D R_D \\ &= 1.8 - I_D R_D \end{aligned}$$

As

$$(V_{in} - V_t) = 1.8 - I_D R_D$$

$$\Rightarrow \text{Gate voltage } \boxed{V_{in} = 1.8 - I_D R_D + V_t}$$

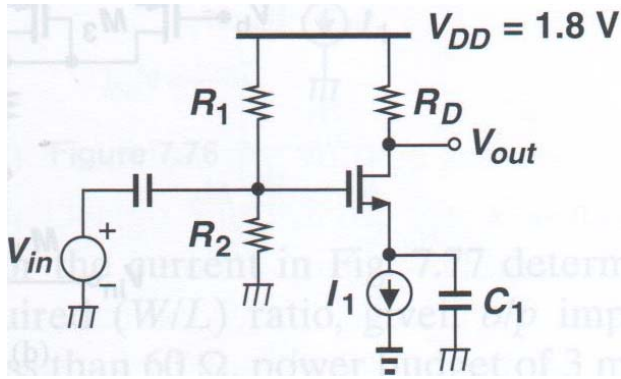5. (10%) $I_D = 1.5 \text{ mA}$, $R_D = 350 \Omega$, $\lambda = 0$, C is large, compute (W/L) to obtain gain of 7. $A_v = g_m R_D$



Ans:

Solution $I_D = 1.5 \text{ mA}$, $R_D = 350 \Omega$, $\lambda = 0$, I_1 ideal source, $(W/L) = ?$ for $A_v = 7$.

$$I_D = \frac{1}{2} \mu_n C_0 \times \frac{W}{L} \cdot (V_{G_s} - V_t)^2$$

$$g_m = \sqrt{2 \mu_n C_0 \times \frac{W}{L} I_D} = \sqrt{2 \times 200 \times 10^{-6} \times \frac{W}{L} \times 1.5 \times 10^{-3}} \quad (1)$$


$$A_v = g_m \cdot R_D \Rightarrow 7 = g_m (350) \quad (2)$$

$g_m = 7/350$. Putting g_m value in Eq. (1), we get

$$\frac{7}{350} = \sqrt{2 \times 200 \times 10^{-6} \times \frac{W}{L} \times 10^{-3}} \Rightarrow \frac{W}{L} = 667.$$

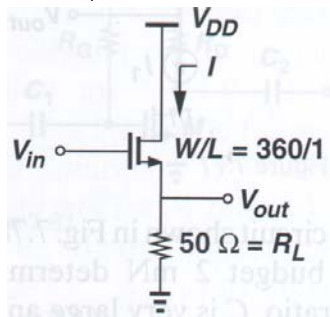6. (10%) Transistor with $W/L = 360$, $R_L = 50 \Omega$, power is 20 mW, find voltage gain ($V_{DD} = 2 \text{ V}$).

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$




Ans:

Solution $p = 20 \text{ mW}$; $V_{DD} = 2 \text{ V} \Rightarrow \max I = \frac{20 \times 10^{-3}}{2 \text{ V}} = 10 \text{ mA}$

We know $g_m = \sqrt{2 \mu_n C_0 \times \frac{W}{L} I_D} = \sqrt{2 \times 200 \times 10^{-6} \times 360 \times 10 \times 10^{-3}} = 0.0379 \text{ S}$

We have $A_v = \frac{R_L}{\frac{1}{g_m} + R_L} = \frac{50}{26.38 + 50} = 0.65 \text{ v/v}$.

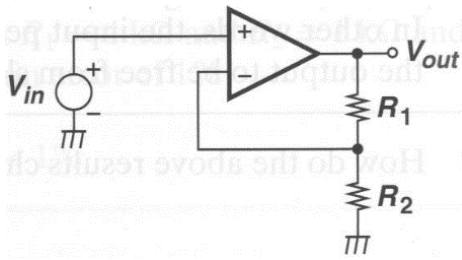7. (10%) For noninverting amplifier, Find the expression for V_{out} ..



Ans:


$$\left[\left(V_{in} - V_{out} \frac{R_2}{R_1 + R_2} \right) A_0 - V_{out} \right] \frac{1}{R_{out}} = \frac{V_{out}}{R_1 + R_2}$$

Since, $R_{out} \ll (R_1 + R_2)$, so,

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{\left[1 + A_0 \cdot \frac{R_2}{(R_1 + R_2)} \right]}$$

$$\Rightarrow V_{out} = \frac{A_0 V_{in}}{\left[1 + A_0 \frac{R_2}{(R_1 + R_2)} \right]}$$

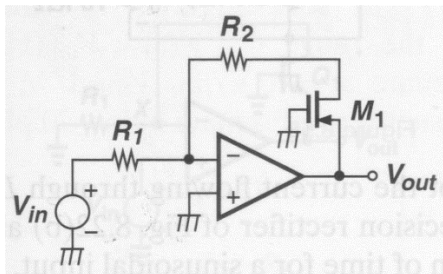8. (10%) Derive the expression for output voltage in terms of input voltage.



ANS:

$$i_1 = \frac{V_i - V_A}{R_1} = \frac{V_i}{R_1} \quad (1)$$

$$i_2 = \frac{V_A - V_{out}}{R_2} = \frac{-V_{out}}{R_2} \quad (2)$$


$$i_1 = i_2 \Rightarrow \frac{V_i}{R_1} = \frac{-V_{out}}{R_2}$$

$$\frac{V_{out}}{V_i} = \frac{-R_2}{R_1}$$

$$V_{out} = \frac{-R_2}{R_1} V_i$$

$$V_{out} = (-R_2/R_1)V_i$$

9. (10%) calculate the transfer function of the circuit shown below if $A_0 = \infty$. What choice of component values reduces $|V_{out}/V_{in}|$ to unity at all frequencies. $X_{C1}=1/(sC1)$, $X_{C2}=1/(sC2)$

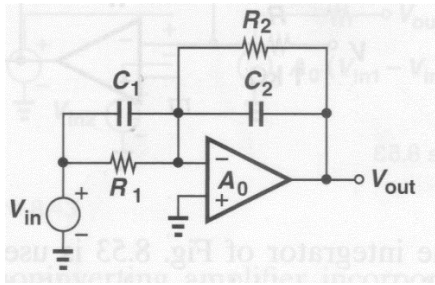

Ans:

$$\because A_0 = \infty,$$

$$V_+ = V_- = 0$$

By KCL,

$$\frac{V_{in}}{R_1 \parallel \frac{1}{sC_1}} = - \frac{V_{out}}{R_2 \parallel \frac{1}{sC_2}}$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{R_2 \parallel \frac{1}{sC_2}}{R_1 \parallel \frac{1}{sC_1}}$$

$$= - \frac{R_2}{R_1} \times \frac{1 + R_1 C_1 s}{1 + R_2 C_2 s}$$


$$\text{For } \left| \frac{V_{out}}{V_{in}} \right| = 1,$$

$$R_2 \parallel \frac{1}{sC_2} = R_1 \parallel \frac{1}{sC_1}$$

That is, choose the components such that the impedance of $R_2 \parallel \frac{1}{sC_2}$ is equal to $R_1 \parallel \frac{1}{sC_1}$ at the specific frequency.

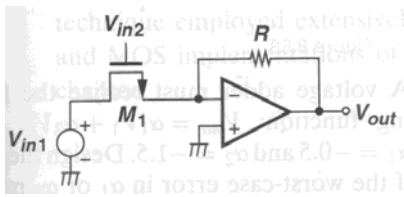10.(10%) analyze the function of a circuit and verify its function mathematically.

$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$



ANS:

Solution In negative feedback circuits another resistance is replaced by M_1 . We know that

$$\frac{V_0}{V_{in}} = \frac{-R_2}{R_1}$$

is that case. R_1 is now equivalent to resistance of M_1 . Here we must know minimum V_{in2} required, which will provide equivalent resistance of R_1 for required gain. Based on this we can get acceptable range of V_{in1} values, ensuring the required gains.


For Fig. 8.60, we can write

$$\frac{V_{out}}{V_{in1}} = \frac{-R_2}{R_1} = \frac{-R_2}{1/kn' \frac{W}{L} V_{in2}} = -kn' \frac{W}{L} V_{in2} R_2$$

$$\Rightarrow V_{out} = (V_{in1} \cdot V_{in2}) \left(kn' \frac{W}{L} R_2 \right) \Rightarrow V_{in2} \text{ should be at least } \frac{1}{kn' \frac{W}{L} R_2} \Rightarrow V_{in2} \text{ at least } (V_{GS} - V_{TH})$$

\Rightarrow Circuit works as a multiplier; \Rightarrow o/p voltage proportional to product of V_{in1} and V_{in2} .

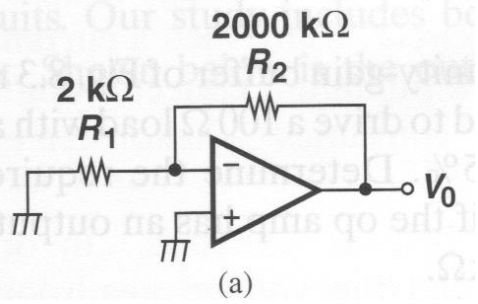11. (10%) calculate output voltage V_0 for input offset voltage of 2 mV.





Ans:

the output voltage for the above current is

$$\pm \frac{R_2}{R_1} \times \text{input offset voltage}$$


$$= \pm \frac{2000 \times 10^3}{2 \times 10^3} \times 2 \text{ mV} = \pm 2 \text{ V.}$$

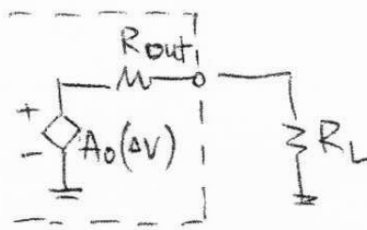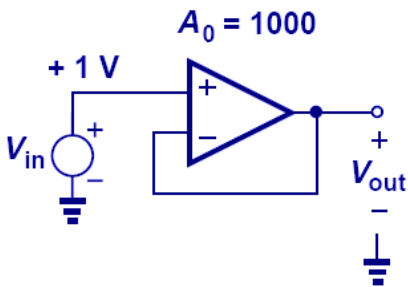12. (10%) The unity gain buffer must be designed to drive a 100 Ω load with a gain error of 0.5%. Determine the required op amp gain if the op amp has an output resistance of 1kΩ.




Ans:

48

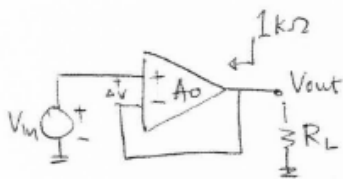

$R_L = 100 \Omega$
Gain Error = 0.5%
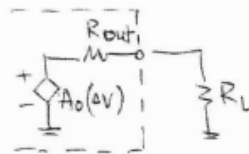
$$(V_{in} - V_{out}) A_0 \times \frac{R_L}{R_{out} + R_L} = V_{out}$$



$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{R_{out} + R_L}{A_0 R_L}} \approx 1 - \frac{R_{out} + R_L}{A_0 R_L} = \epsilon$$

$$\therefore \epsilon = \frac{R_{out} + R_L}{A_0 R_L} \Rightarrow A_0 = \frac{R_{out} + R_L}{\epsilon R_L} = \frac{1000 + 100}{0.5\% \times 100} \approx 2200.$$