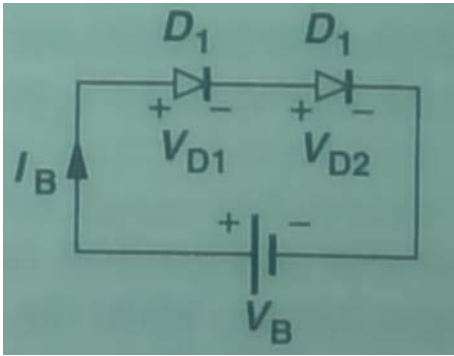


Name:

ID#

1. Two diodes with reverse saturation currents of I_{S1} and I_{S2} placed series. Calculate I_B , V_{D1} , and V_{D2} in terms of V_B , I_{S1} , and I_{S2} .



By KVL, $V_B = V_{D1} + V_{D2} = V_T \ln\left(\frac{I_B}{I_{S1}}\right) + V_T \ln\left(\frac{I_B}{I_{S2}}\right)$

$\Rightarrow V_B = V_T \ln\left(\frac{I_B^2}{I_{S1} I_{S2}}\right)$

$\therefore I_B = \sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right) = \sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right)$


$$V_{D1} = V_T \ln\left(\frac{I_B}{I_{S1}}\right) = V_T \ln\left(\frac{\sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right)}{I_{S1}}\right)$$

$$= V_T \ln\left(\frac{I_{S2}}{\sqrt{I_{S1}}}\right) + \frac{V_B}{2}$$


$$V_{D2} = V_T \ln\left(\frac{I_B}{I_{S2}}\right) = V_T \ln\left(\frac{\sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right)}{I_{S2}}\right)$$

$$= V_T \ln\left(\frac{I_{S1}}{\sqrt{I_{S2}}}\right) + \frac{V_B}{2}$$

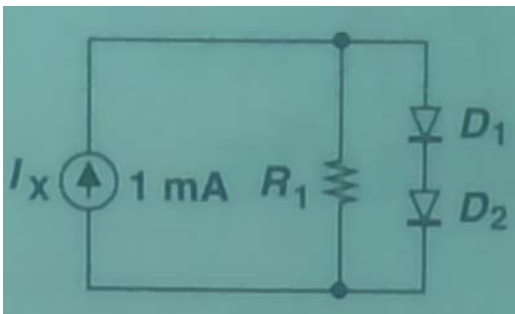2. (10%) Determine the value of R_1 such that R_1 carries 0.5mA. Assume $I_S = 5 \times 10^{-16}$ A for each diode.



Ans:

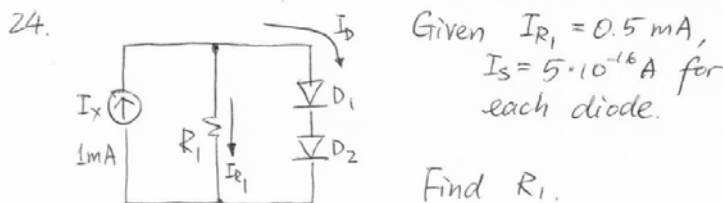


By KCL, $I_D = I_x - I_{R1} = 0.5 \text{ mA}$

$\Rightarrow V_{D1} = V_{D2} = V_T \ln\left(\frac{I_D}{I_S}\right) = 0.026 \ln\left(\frac{0.5 \text{ mA}}{5 \cdot 10^{-16} \text{ A}}\right)$
 $\approx 0.718 \text{ V}$

$\therefore R_1 = \frac{V_{R1}}{I_{R1}} = \frac{2 V_{D1}}{I_{R1}} = \frac{2(0.718 \text{ V})}{0.5 \text{ mA}} \approx 2.87 \text{ k}\Omega$

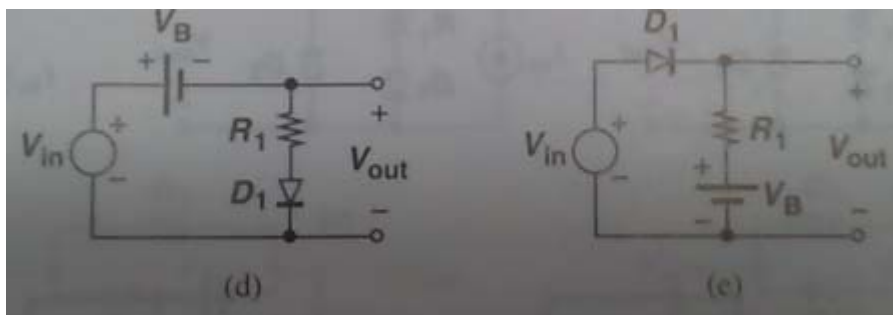
3. (10%) Plot the input/output characteristics of the circuit shown below using an ideal model for the diode. (Assume $V_B = 2V$).




Ans:

(d)

(e)

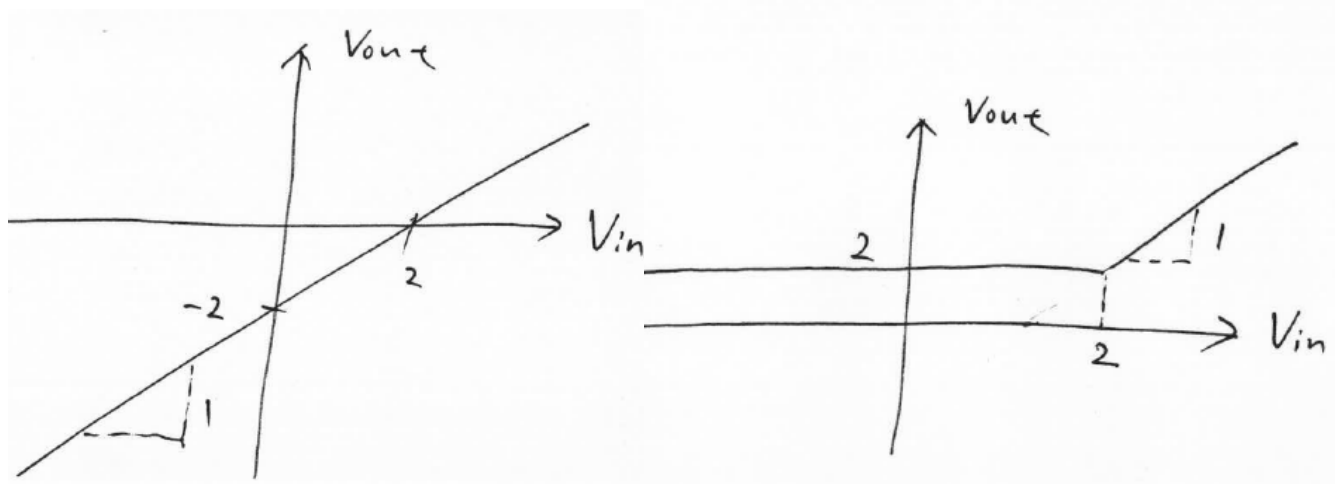

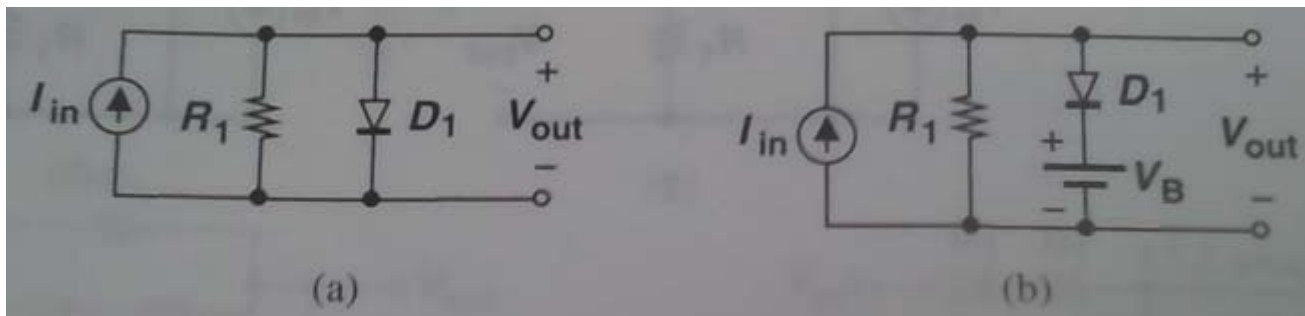
4. (10%) Assume constant voltage diode model, plot V_{out} as a function of I_{in} for the circuits shown below. (Assume $V_B = 2V$).




Ans:

(a)


(b)

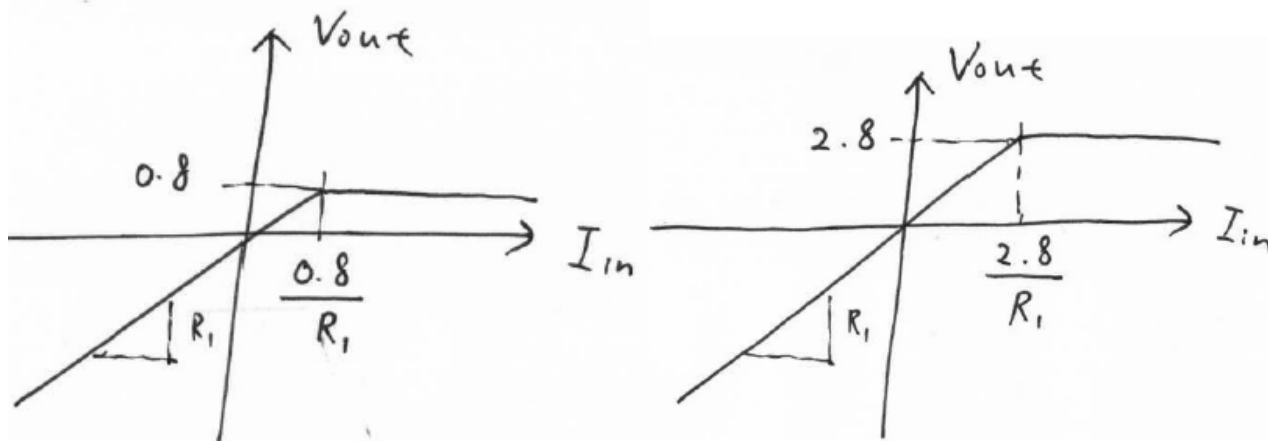

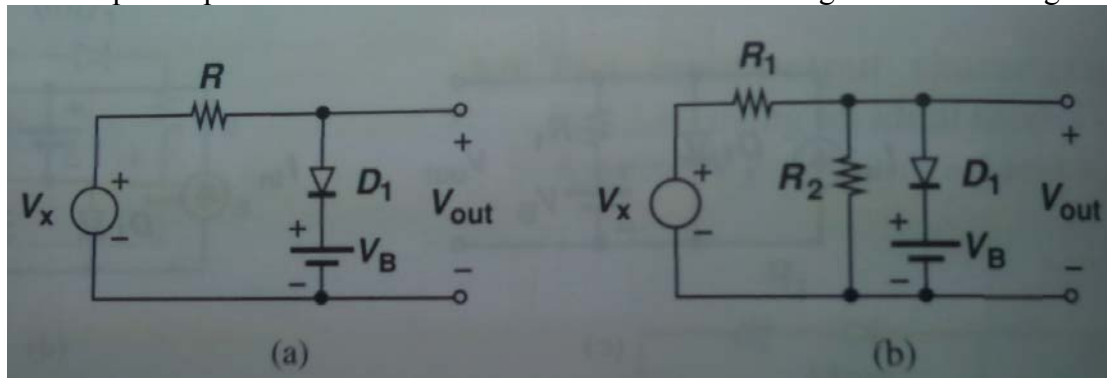
5. (10%) Plot the input/output characteristics of the circuit below. Assuming a constant voltage diode model.



Ans:

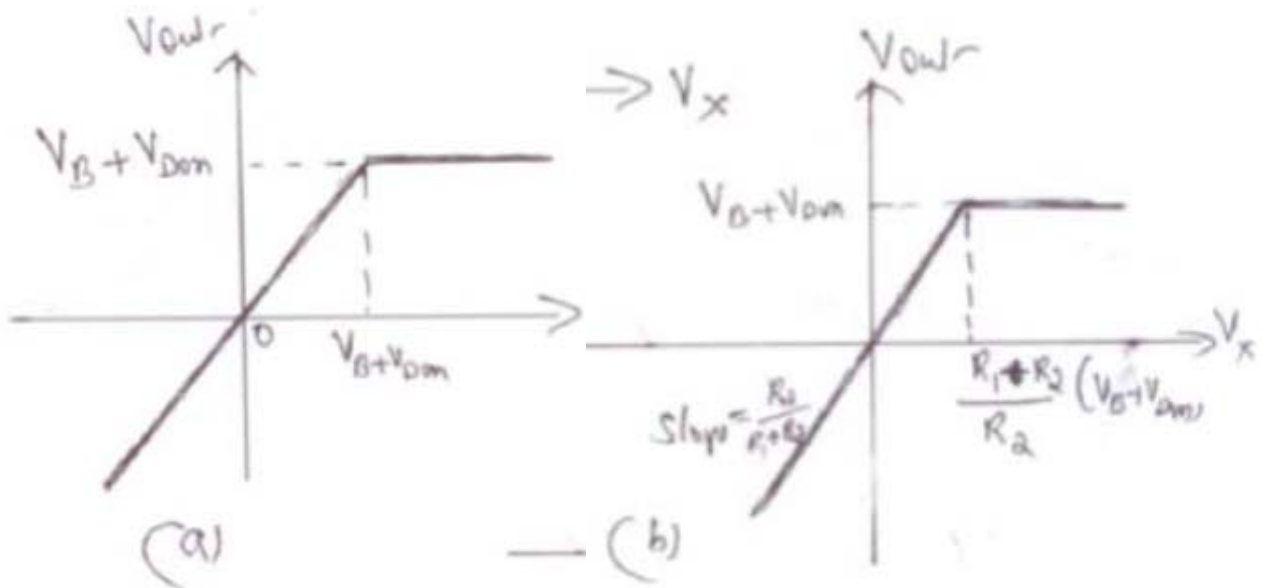

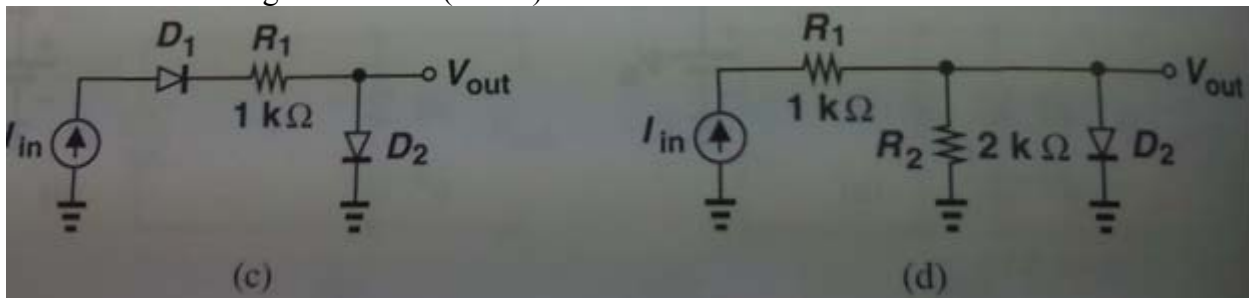6. (10%) Beginning with $V_{D,on} \cong 800\text{mV}$ for each diode, calculate the change in V_{out} if I_{in} changes from 3 mA to 3.1 mA in following circuits. $r_d = (26\text{mV})/I$



Ans:

$$\begin{aligned}
 \text{c) } V_{out} &= i \times r_{d2} \\
 &= 0.1 \text{ mA} \times 8.67 \quad (\text{from (b)}) \\
 &= 0.867 \text{ mV}
 \end{aligned}$$

$$\begin{aligned}
 \text{d) } V_{out} &= i \times (R_2 \parallel r_{d2}) \\
 &\approx i \times r_{d2} \quad (\because R_2 \gg r_{d2}) \\
 &= 0.867 \text{ mV}
 \end{aligned}$$

$\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$, NMOS $V_{TH} = 0.4 \text{ V}$, PMOS $V_{TH} = -0.4 \text{ V}$,

7. (10%) Calculate the value of drain current in the circuit shown below, with $W = 5 \mu\text{m}$, $L = 0.5 \mu\text{m}$, and $\lambda = 0$.

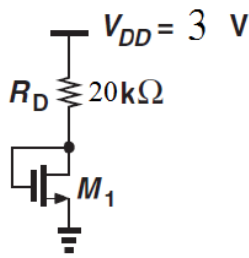


Fig 6.37

Ans:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$V_{GS} = V_{DD} - I_D R_D$$

$$= 3 - I_D 20k$$

$$I_D = \frac{1}{2} \times 200 \times 10^{-6} \times \frac{5 \times 10^{-6}}{0.5 \times 10^{-6}} \times (3 - I_D 20k - 0.4)^2$$

$$(I_D 20k)^2 - 105I_D + 2.6^2 = 0.$$

$$I_D = 113.17 \mu\text{A}$$

$$\text{Overdrive voltage } V_{ov} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = 0.336 \text{ V}$$

$$V_{GS} = V_{TH} + V_{ov}$$

$$= 0.736 \text{ V}.$$

8. (10%) What is the current when $V_{GS} = 2V_{TH}$? Find the region in which the device operates.

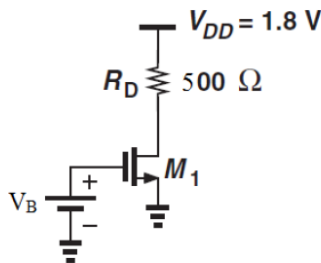


Fig 6.42

ANS:

Assume that the device is in the saturation region. Then,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} \times 200 \times 10^{-6} \times \frac{10}{0.14} (2V_{TH} - V_{TH})^2$$

$$= \frac{1}{2} \times 200 \times 10^{-6} \times \frac{10}{0.14} (V_{TH})^2$$

$$= \frac{1}{2} \times 200 \times 10^{-6} \times \frac{10}{0.14} (0.4)^2$$

$$= 1.142 \text{ mA}$$


$$V_{DS} = V_{DD} - I_D R_D$$

$$= 1.8 - 500 \times 1.142 \times 10^{-3}$$

$$= 1.23 \text{ V}.$$



Since $V_{DS} > V_{GS} - V_{TH}$, the device operates in the saturation region.

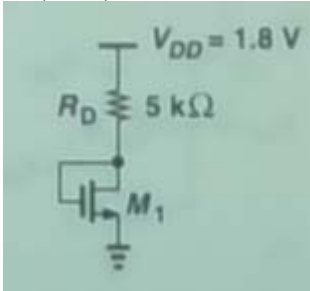9. (10%) If $\lambda = 0.1 \text{ V}^{-1}$, $W/L = 20/0.18$, construct the small-signal model of each of the circuits shown below



Ans:

(b)

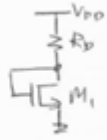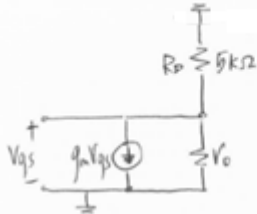


$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \frac{200 \mu\text{A}}{\text{V}^2} \left(\frac{20}{0.18} \right) (0.146 \text{V}) \approx 0.00324 \text{ V}^{-1}$$

By KCL, $\frac{V_{DD} - V_{GS}}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS})$

Solving this yields $V_{GS} \approx 0.546 \text{ V} > V_{TH}$


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{\lambda \left(\frac{V_{DD} - V_{GS}}{R_D} \right)} = \frac{1}{0.1 \text{ V}^{-1} \left(\frac{1.8 - 0.546}{5 \text{ k}} \right)} \approx 40 \text{ k}\Omega$$

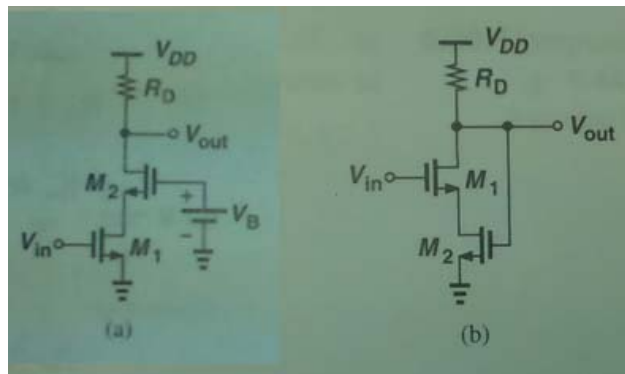10. (10%) Construct the small-signal model of the circuits. Assume all transistors operate in saturation and $\lambda \neq 0$.



ANS:

(a)

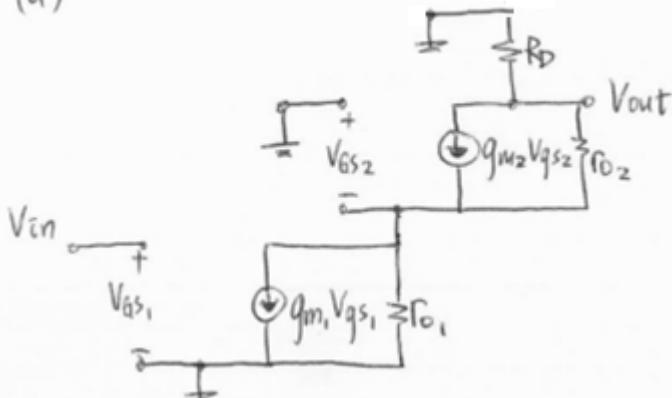

(b)

