

國立中山大學 103 學年度第一學期資工系數位系統期末考試

學號：

姓名：

一、選擇與是非題 (每題 3 分, 12 分)

- () 1. What kind of flip-flop is the most popular component to construct a register? ①SR ②D ③JK ④T
- () 2. How many address lines are required in a 16M×16 RAM? ①14 ②16 ③24 ④34.
- () 3. In DRAM, information is stored in the form of charges on capacitors. When compared to SRAM, DRAM has shorter read/write cycle.
- () 4. Programmable read-only memory (PROM) has programmable AND array and fixed OR array.

二、問答題 (88 分)

1. Derive the following terms for the sequential circuit shown in Fig. 1.

- (1) Input (Excitation) equations (6%) (2) State equations and output equation (6%)
- (3) State table (Table 1) (6%) (4) State diagram (4%)

2. Design a counter with the following repeated binary sequence: 0, 1, 2, 4, 6. Assume that binary states 011, 101 and 111 are considered as don't care conditions.

- (1) Complete the state table as shown in Table 2 using natural binary encoding for state assignment. (4%)
- (2) Use D flip-flops and derive the simplified flip-flop input (excitation) equations using the K-map (find the minimal sum of products expressions). (6%)
- (3) Draw the logic diagram of the counter with D flip-flops as shown in Fig. 2(a). (4%)
- (4) Use T flip-flops and complete the state table and T flip-flop input as shown in Table 2. (4%)
- (5) Use T flip-flops and derive the simplified flip-flop input (excitation) equations using the K-map (find the minimal sum of products expressions). (6%)
- (6) Draw the logic diagram of the counter with T flip-flops as shown in Fig. 2(b). (4%)

3. A 64K × 8 memory uses coincident decoding by splitting the internal decoder into X-selection and Y-selection as shown in Fig. 3.

- (1) What is the size of each decoder, and how many AND gates are required for decoding the address? (6%)
- (2) Determine the X and Y selection lines that are enabled when the input address is the binary equivalent of 36,952. (6%)

4. Using an 8 × 3 ROM shown in Fig. 4 and a 3 × 4 × 3 PLA shown in Fig. 5, implement the truth table shown in Table 3. (6%) (10%)

5. Explain the read and write operations of the 4 × 4 RAM and the memory cell as shown in Fig. 6(a) and 6(b), respectively. (10%)

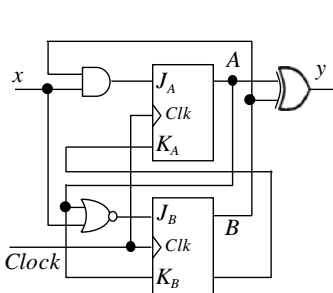


Fig. 1

Present state		Input	Next state		Output
A	B	x	A	B	y

Present state			Next state			Flip-Flop Inputs		
A ₂	A ₁	A ₀	A ₂	A ₁	A ₀	T _{A2}	T _{A1}	T _{A0}

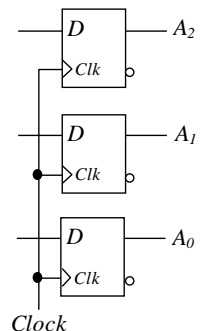


Fig. 2(a)

國立中山大學 102 學年度第一學期資工系數位系統期末考試

學號：

姓名：



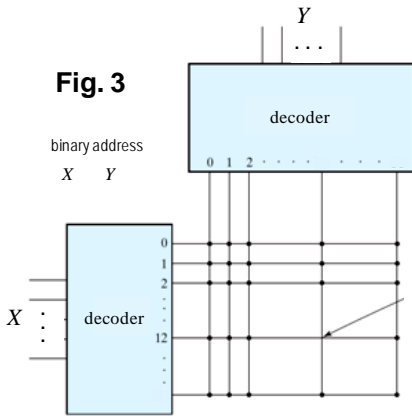


Table 3

A	B	C	F_1	F_2	F_3
0	0	0	1	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	1	0	1

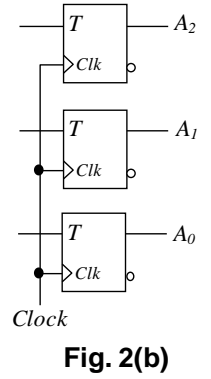

Flop-flop	D	JK	T																																			
characteristic equation	$Q(t+1) = D$	$Q(t+1) = JQ' + K'Q$	$Q(t+1) = T \oplus Q$																																			
characteristic table	<table border="1"> <thead> <tr><th>D</th><th>Q(t+1)</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	D	Q(t+1)	0	0	1	1	<table border="1"> <thead> <tr><th>J</th><th>K</th><th>Q(t+1)</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>Q(t)</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>Q'(t)</td></tr> </tbody> </table>	J	K	Q(t+1)	0	0	Q(t)	0	1	0	1	0	1	1	1	Q'(t)	<table border="1"> <thead> <tr><th>T</th><th>Q(t+1)</th></tr> </thead> <tbody> <tr><td>0</td><td>Q(t)</td></tr> <tr><td>1</td><td>Q'(t)</td></tr> </tbody> </table>	T	Q(t+1)	0	Q(t)	1	Q'(t)								
D	Q(t+1)																																					
0	0																																					
1	1																																					
J	K	Q(t+1)																																				
0	0	Q(t)																																				
0	1	0																																				
1	0	1																																				
1	1	Q'(t)																																				
T	Q(t+1)																																					
0	Q(t)																																					
1	Q'(t)																																					
excitation table	<table border="1"> <thead> <tr><th>Q(t)</th><th>Q(t+1)</th><th>J</th><th>K</th><th>Q(t)</th><th>Q(t+1)</th><th>T</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>X</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>X</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>X</td><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>X</td><td>0</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>			Q(t)	Q(t+1)	J	K	Q(t)	Q(t+1)	T	0	0	0	X	0	0	0	0	1	1	X	0	1	1	1	0	X	1	1	0	1	1	1	X	0	1	1	0
Q(t)	Q(t+1)	J	K	Q(t)	Q(t+1)	T																																
0	0	0	X	0	0	0																																
0	1	1	X	0	1	1																																
1	0	X	1	1	0	1																																
1	1	X	0	1	1	0																																

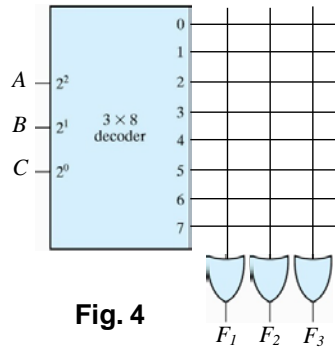