

國立中山大學 103 學年度第一學期資工系數位系統期中考試

學號：

姓名：

一、選擇與是非題 (每題 3 分, 12 分)

- ( ) 1. 關於 Karnaugh maps 而言, 下列何者錯誤? ① a pictorial form of a truth table ② each square represents one maxterm ③ any two adjacent squares in the map differ by only one variable ④ applicable if the number of variables < 7。
- ( ) 2. 下列那一個 two-level form 是 nondegenerate form (亦即不可轉換成 a single operation)? ① AND-NOR ② AND-NAND ③ NAND-OR ④ NOR-NAND。
- ( ) 3. 關於 XOR 以及 XNOR, 何者錯誤? ①  $(x \oplus y)' = x \odot y$  ②  $x \oplus y' = (y \oplus x)'$  ③  $x \oplus 1 = x'$  ④  $x \odot x' = 1$ 。
- ( ) 4. 一般而言, Product of sums 應該轉換成 NAND Implementation, 而 Sum of products 則應該轉換成 NOR Implementation 以獲得較簡單的電路。

二、問答題 (88 分)

1. (1) Derive the sum-of-minterms and the product-of-maxterms canonical forms for Boolean function  $F(w, x, y, z) = (w'+x)(y+z)(y'+z)$ . (6%)
- (2) Using the Karnaugh map to find the simplest sum-of-products and product-of-sums of this Boolean function. (6%)
- (3) Implement the function  $F(w, x, y, z)$  with the simplest NAND-NAND and NOR-NOR logics, draw the logic diagrams. (6%)

2.  $F(w, x, y, z) = \sum (2, 6, 7, 8, 9, 13, 15)$ .

- (1) Find all the prime implicants for  $F(w, x, y, z)$  and determine which are essential. (6%)
- (2) Find all the simplest sum-of-products of this Boolean function. (6%)

3. Draw the Karnaugh map of Boolean function  $F(v, w, x, y, z) = \sum (0, 1, 2, 3, 8, 9, 10, 11, 13, 15, 16, 17, 18, 19, 24, 26, 29, 31)$  and find all the simplest sum-of-products of this Boolean function. (10%)

4. A majority circuit is a combinational circuit whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise. Design a 3-input majority circuit by

- (1) listing the circuit's truth table (assume that input variables are  $x, y, z$  and output variable is  $F$ ) (3%)
- (2) drawing the Karnaugh map and deriving the simplest Boolean function of  $F$  (3%)
- (3) drawing the logic diagram. (3%)

5. Design a 4-bit carry lookahead adder with inputs  $A = A_3A_2A_1A_0$  and  $B = B_3B_2B_1B_0$ , and outputs  $S = S_3S_2S_1S_0$  and  $C_4$ . Let carry propagate  $P_i = A_i \oplus B_i$  and carry generate  $G_i = A_i B_i$ , then sum  $S_i = P_i \oplus C_i$  and carry  $C_{i+1} = G_i + P_i C_i$ , where  $0 \leq i \leq 3$ .

- (1) Derive the Boolean functions of  $C_1, C_2, C_3$ , and  $C_4$  with input variables  $G_i, P_i$  and  $C_0$ . (6%)
- (2) Draw the logic diagram of carry lookahead generator to generate  $C_1, C_2, C_3$ , and  $C_4$  (6%)

6. (1) Draw a three-to-eight-line decoder composed of Inverters and AND gates. (6%)

- (2) Draw a four-to-one-line multiplexer composed of Inverters, AND and OR gates with the function table shown in Table 1. (6%)

- (3) Implement  $F(A, B, C) = \sum(0, 3, 4, 5)$  using 4-to-1 MUX shown in Fig. 1. (5%)

7. Design one digit of decimal adder.

- (1) Complete the truth table shown in Table 2. (4%)
- (2) Derive the Boolean function of C and draw its logic diagram. (6%)

**Table 1**

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

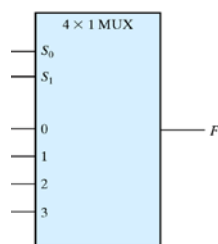


Fig. 1

Table 2

K	Binary Sum				BCD Sum					Decimal
	$Z_8$	$Z_4$	$Z_2$	$Z_1$	C	$S_8$	$S_4$	$S_2$	$S_1$	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0						10
0	1	0	1	1						11
0	1	1	0	0						12
0	1	1	0	1						13
0	1	1	1	0						14
0	1	1	1	1						15
1	0	0	0	0						16
1	0	0	0	1						17
1	0	0	1	0						18
1	0	0	1	1						19