


Name:

ID#

$$\mu_n C_{ox} = 200 \mu A/V^2, \mu_p C_{ox} = 100 \mu A/V^2, \text{ NMOS } V_{TH} = 0.4 \text{ V, PMOS } V_{TH} = -0.4 \text{ V,}$$

$$\text{Saturation current } I_D = (1/2) \mu_n C_{ox} (W/L) (V_{GS} - V_{TH})^2; g_m = [2\mu_n C_{ox} (W/L) I_D]^{1/2}; r_o = [1/(\lambda I_D)]$$

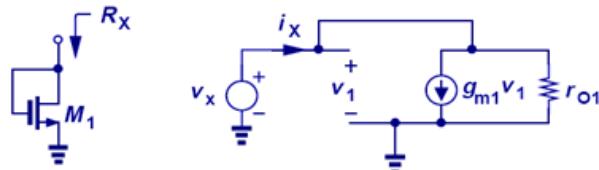1. (10%) Find  $R_X$  of the following circuit.




ANS:

$$R_X = \frac{v_x}{i_x} \Rightarrow (g_{m1} v_x + \frac{v_x}{r_{o1}}) = i_x$$

$$(g_{m1} + \frac{1}{r_{o1}}) v_x = i_x$$

$$R_X = \frac{v_x}{i_x} = \frac{1}{g_{m1} + \frac{1}{r_{o1}}} = \frac{1}{g_{m1}} \| r_{o1}$$

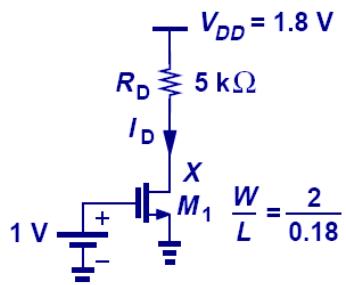2. (10%) Determine the W/L of the figure that place the  $M_1$  at the edge of saturation. In this case, the edge of saturation should follow  $V_{DS} = V_{GS} - V_{TH}$



ANS:

$V_{GS} = +1V$ , drain voltage must fall to  $V_{GS} - V_{TH} = 0.4V$  for  $M_1$  enter triode region.


$$I_D = \frac{V_{DD} - V_{DS}}{R_D} = 280 \mu A = I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$280 \mu A = \frac{1}{2} \times 200 \mu A/V^2 \times \frac{W}{L} (1 - 0.4)^2$$

$$\frac{W}{L} = \frac{280}{100 \times 0.36} = \frac{1.4}{0.18} = 7.78$$

3. (10%)  $I_D = 1 \text{ mA}$ ,  $(W/L)_2 = 5/1$ ,  $(W/L)_1 = 10/1$ ,  $\lambda_1 = 0.1 \text{ V}^{-1}$ ,  $\lambda_2 = 0.1 \text{ V}^{-1}$ , calculate  $R_{out}$ .

$$R_{out} = (1/g_{m2}) || (r_{O2}) || (r_{O1}),$$

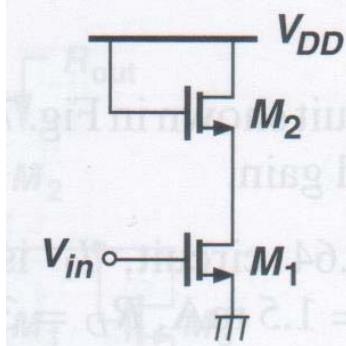

ANS:

$$r_{O2} = \frac{1}{\lambda I_D} = \frac{1}{0.1 \times 10^{-3}} = 10 \text{ k}\Omega.$$

$$r_{O1} = \frac{1}{\lambda I_D} = 10 \text{ k}\Omega.$$

$$g_{m2} = \sqrt{2 \times 200 \times 10^{-6} \times \frac{5}{1} \times 1 \times 10^{-3}} = 0.00141 \text{ S.}$$

$$R_{out} = \frac{1}{g_{m2}} || r_{O2} || r_{O1} = 709 || 10 \text{ k}\Omega || 10 \text{ k}\Omega = 709 \Omega.$$

4. (10%) In Fig. 6.42, what is the current when  $V_{GS} = 2V_{TH}$  and  $W/L=10/0.14$ ? Find the region in which the device operates. [ $V_{DS} > V_{GS} - V_{TH} \rightarrow \text{Saturation}$ ,  $V_{DS} < V_{GS} - V_{TH} \rightarrow \text{Triode}$ ]

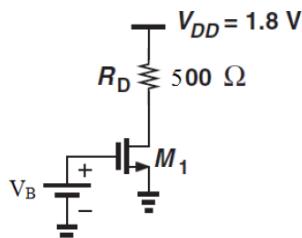


Fig 6.42

ANS:


$$\begin{aligned} I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\ &= \frac{1}{2} \times 200 \times 10^{-6} \times \frac{10}{0.14} (2V_{TH} - V_{TH})^2 \\ &= \frac{1}{2} \times 200 \times 10^{-6} \times \frac{10}{0.14} (V_{TH})^2 \\ &= \frac{1}{2} \times 200 \times 10^{-6} \times \frac{10}{0.14} (0.4)^2 \\ &= 1.142 \text{ mA} \end{aligned}$$

$$\begin{aligned} V_{DS} &= V_{DD} - I_D R_D \\ &= 1.8 - 500 \times 1.142 \times 10^{-3} \\ &= 1.23 \text{ V.} \end{aligned}$$

Since  $V_{DS} > V_{GS} - V_{TH}$ , the device operates in the saturation region.

5. (10%) Calculate voltage gain,  $R_G=40\text{k}\Omega$ ,  $I_D=5\text{mA}$ ,  $\lambda_1=\lambda_2=0.001\text{V}^{-1}$ ,  $(W/L)_1 = (W/L)_2 = 300/1$ .

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \quad A_V = \frac{r_{o1} \| r_{o2}}{\frac{1}{g_m} + r_{o1} \| r_{o2}}$$

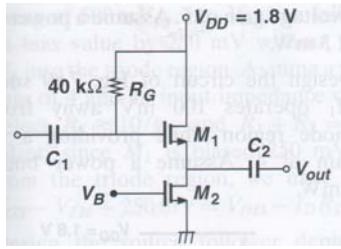

ANS:


$$A_V = \frac{r_{o1} \| r_{o2}}{\frac{1}{g_m} + (r_{o1} \| r_{o2})}$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda \cdot I_D} = \frac{1}{0.001 \times 5 \times 10^{-3}} = 200\text{k}\Omega$$

$$\begin{aligned} g_m &= \sqrt{2\mu_n C_0 \frac{W}{L} \times I_D} \\ &= \sqrt{2 \times 200 \times 10^{-6} \times \frac{300}{1} \times 5 \times 10^{-3}} = 0.0245\text{S} \end{aligned}$$


$$\begin{aligned} A_V &= \frac{200\text{k} \| 200\text{k}}{(1/0.0245) + (200\text{k} \| 200\text{k})} \\ &= 0.9995 \text{V/V} \end{aligned}$$

circuit is,

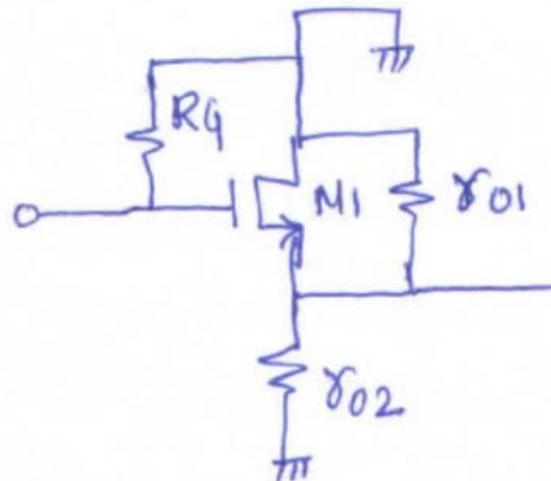

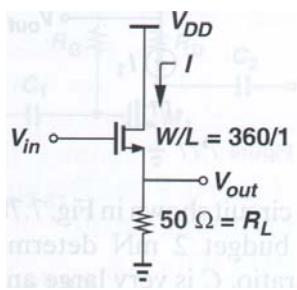6. (10%) Transistor with  $W/L = 360$ ,  $R_L = 50\Omega$ , power is 20 mW, find voltage gain ( $V_{DD} = 2\text{V}$ ).

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \quad A_V = \frac{R_L}{\frac{1}{g_m} + R_L}$$




ANS:

$$\text{Solution } p = 20\text{mW}; V_{DD} = 2\text{V} \Rightarrow \max I = \frac{20 \times 10^{-3}}{2\text{V}} = 10\text{mA}$$

$$\text{We know } g_m = \sqrt{2\mu_n C_0 \frac{W}{L} I_D} = \sqrt{2 \times 200 \times 10^{-6} \times 360 \times 10 \times 10^{-3}} = 0.0379\text{S}$$

$$\text{We have } A_V = \frac{R_L}{\frac{1}{g_m} + R_L} = \frac{50}{26.38 + 50} = 0.65 \text{v/v.}$$

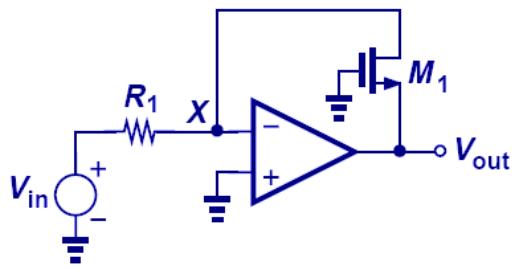7. (10%) For the square root amplifier, Find the expression for  $V_{out}$  in terms of  $V_{in}$ .




ANS:

$$\frac{V_{in}}{R_1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$V_{out} = -\sqrt{\frac{2V_{in}}{\mu_n C_{ox} \frac{W}{L} R_1}} - V_{TH}$$

$$(V_{GS} = -V_{out})$$

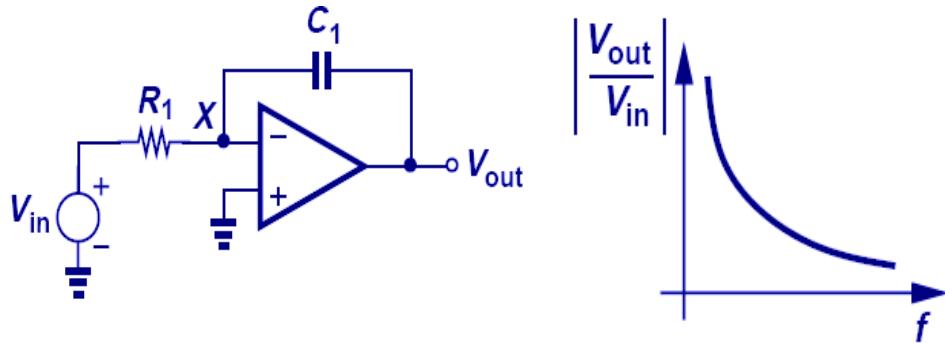8. (10%) Derive the expression ( $V_{out}/V_{in}$ )? [  $X_{C1}=1/(sC1)$  ]




ANS:

$$\frac{V_{out}}{V_{in}} = -\frac{1}{R_1 C_1 s}$$

$$\frac{V_{out}}{V_{in}} = -\frac{1}{R_1 C_1 s}$$

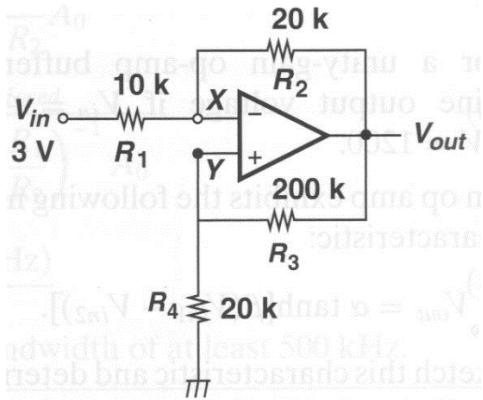9. (10%) Calculate output voltage  $V_{out}$ .



ANS:

$$\frac{V_{in} - V_X}{10\text{K}} = \frac{V_X - V_{out}}{20\text{K}}$$

$$\frac{V_{in}}{10\text{K}} + \frac{V_{out}}{20\text{K}} = V_X \left( \frac{1}{20\text{K}} + \frac{1}{10\text{K}} \right).$$

$$V_Y = \frac{20\text{K}}{(20\text{K} + 200\text{K})} \cdot V_{out}$$

$V_X = V_Y$  due to virtual ground concept.  
So,

$$V(Y) = (1/11)V_{out}$$


$$V(X) = (20V_{in} + 10V_{out})/30$$

$$V(X) = V(Y) \quad 220V_{in} + 110V_{out} = 30V_{out}$$

$$V_{out}/V_{in} = -(11/4) \text{ V/V}$$

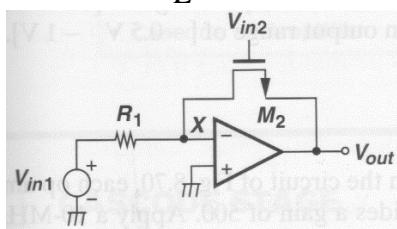10. (10%) analyze the function of a circuit and verify its function mathematically.

$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$




ANS:

$$\frac{V_{out}}{V_{in1}} = \frac{-R_2}{R_1} = -\frac{1}{R_1 \mu_n C_{ox} \frac{W}{L} (V_{in2})}$$

$$V_{out} = -\left(\frac{V_{in1}}{V_{in2}}\right) \frac{1}{\mu_n C_{ox} \frac{W}{L} R_1}$$

output voltage is proportional to ration  $(\frac{V_{in1}}{V_{in2}})$

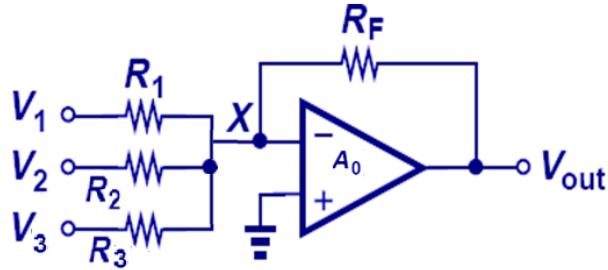11. (10%) Find the output voltage of the following circuit in terms of  $V_1$ ,  $V_2$ ,  $V_3$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_F$ .




ANS:

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{-V_{out}}{R_F}$$

$$V_{out} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

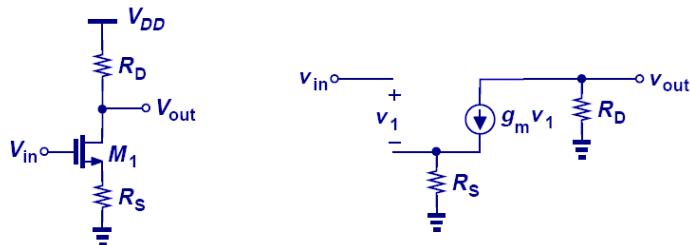12. (10%) Find the small signal gain of the following circuit. (Assuming  $\lambda=0$ ) (10%)



ANS:

$$v_{in} = v_1 + g_m v_1 R_s \Rightarrow v_1 = \frac{v_{in}}{1 + g_m R_s}$$

$$v_{out} = -g_m v_1 R_D \quad \frac{v_{out}}{v_{in}} = -\frac{g_m R_D}{1 + g_m R_s} = -\frac{R_D}{\frac{1}{g_m} + R_s}$$