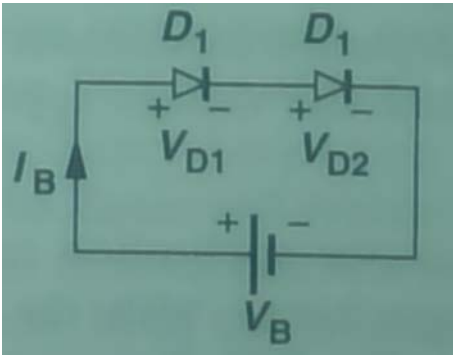



Name:

ID#

1. (10%) Two diodes with reverse saturation currents of I_{S1} and I_{S2} placed series. Calculate I_B , V_{D1} , and V_{D2} in terms of V_B , I_{S1} , and I_{S2} .




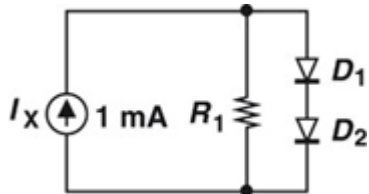2. (10%) Determine the value of R_I such that R_I carries 0.5mA. Assume $I_S = 5 \times 10^{-16}$ A for each diode.



Ans:

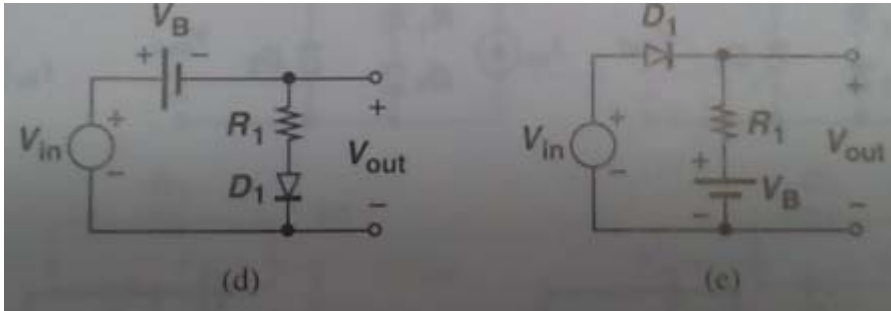
3. (10%) Plot the input/output characteristics of the circuit shown below using an ideal model for the diode. (Assume $V_B = 2V$).



Ans:

(d) (e)

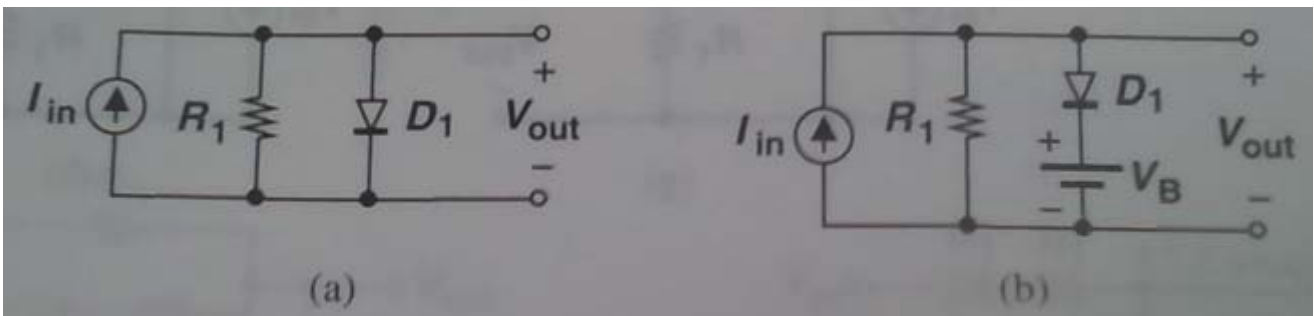
4. (10%) Assume constant voltage diode model, plot V_{out} as a function of I_{in} for the circuits shown below. (Assume $V_B = 2V$).



Ans:


(a) (b)

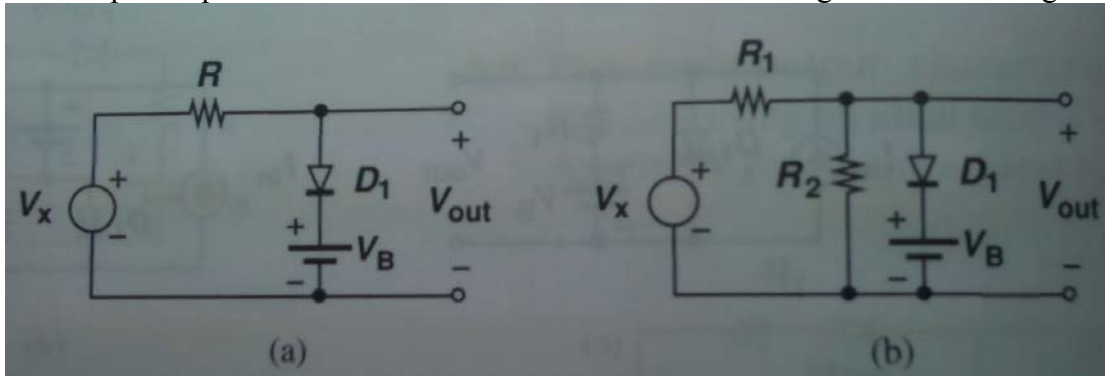5. (10%) Plot the input/output characteristics of the circuit below. Assuming a constant voltage diode model.




Ans:

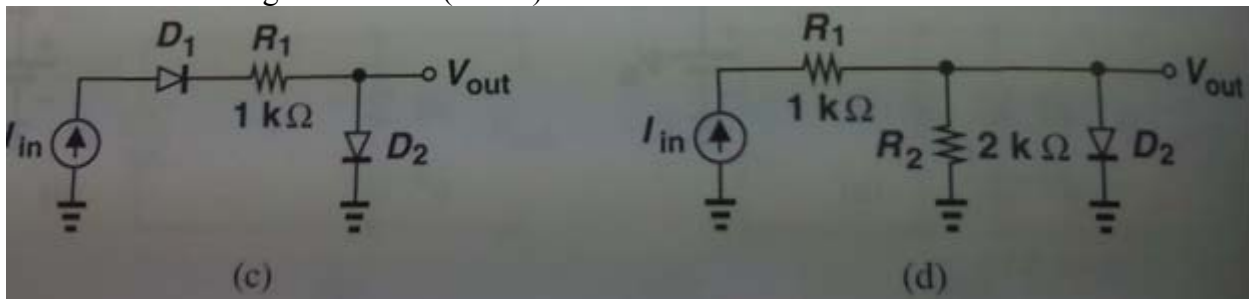6. (10%) Beginning with $V_{D,on} \cong 800\text{mV}$ for each diode, calculate the change in V_{out} if I_{in} changes from 3 mA to 3.1 mA in following circuits. $r_d = (26\text{mV})/I$



Ans:

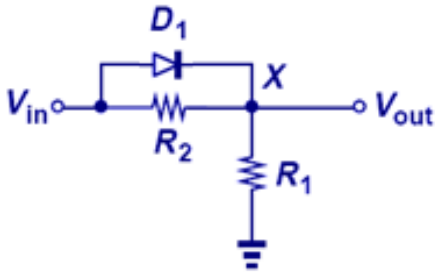7. (10%) Plot the input/output characteristic of the following circuit using the constant voltage model.




Ans:

8. (10%) A cellphone incorporates a 2.4GHz oscillator whose frequency is defined by the resonance frequency of an LC tank. If the tank capacitance is realized as the pn junction of Example 2.15, calculate the change in the oscillation frequency while the reverse voltage goes from 0 to 1.5 V. Assume the circuit operates at 2.4 GHz at a reverse voltage of 0 V, and the junction area is $2500 \mu\text{m}^2$.

$$f_{res} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}, C_j = 0.265 \text{ fF} / \mu\text{m}^2, C_{j,tot} = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_0}}}, V_0 = 0.73\text{V}$$


Ans:

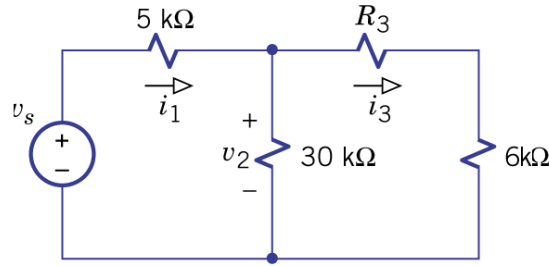9. (10%) If the circuit in the following figure represents a source and load with $v_s=90V$, and $i_1=6mA$, then what are the values of i_3 and R_3 ?




Ans:

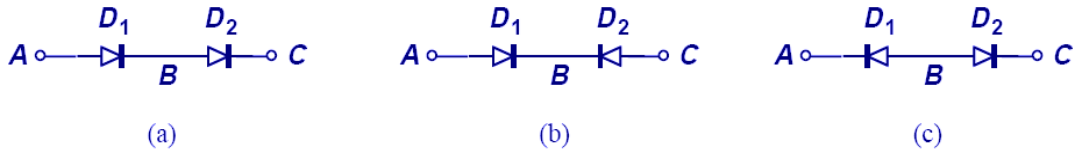
10.1 () Which one of the following figure can conduct current from A to C (2%)



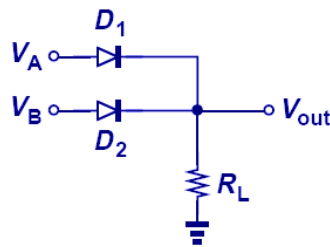
10.2 () What function does the following figure perform? (a) NOT (b) AND (c) OR gate (2%)



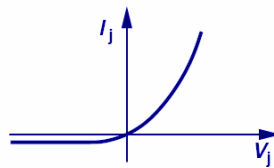10.3 () What is the diode model of the following figure ? (a) Constant voltage model (b) Exponential model (c) Ideal model (2%)



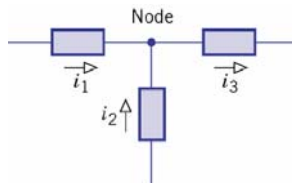10.4. () What is the current equation in following figure ? (a) $i_1= i_2+ i_3$ (b) $i_2= i_1+ i_2$ (c) $i_3= i_1+ i_2$ (2%)



10.5. () Which is the node of cathode of diode in the following figure ? (a) A (b) B (2%)

