

Name:

ID#

1. A 3-V adaptor using a half-wave rectifier must supply a current of 0.5A with a maximum ripple of 300mV. For a frequency of 60 Hz, compute the minimum required smoothing capacitor. The relation of the load current, capacitor, frequency, ripple is $V_R = I_L / (C_1 f_{in})$ (8%)

Ans:


$$V_R = \frac{I_L}{C_1 f_{in}} \leq 300 \text{ mV}$$

$$f_{in} = 60 \text{ Hz}$$


$$I_L = 0.5 \text{ A}$$

$$C_1 \geq \frac{I_L}{(300 \text{ mV}) f_{in}} = \boxed{27.78 \text{ mF}}$$

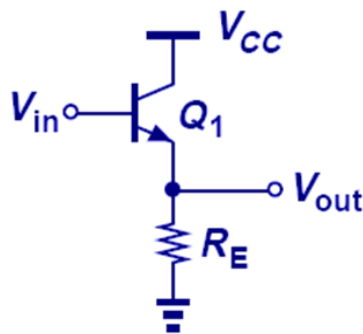2. Draw the small-signal equivalent circuit for the amplifier shown below, neglecting r_o . (8%)



Ans:

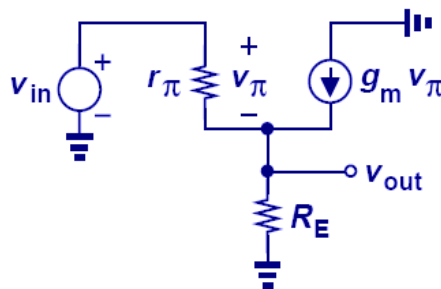


3. A transistor with $I_S = 6 \times 10^{-16} \text{ A}$ must provide a transconductance of $(1/13) \Omega$. What is base-emitter voltage is required? (8%)


Ans:

$$\begin{aligned} \textcircled{A} \quad g_m &= \frac{I_C}{V_T} \\ \Rightarrow g_m &= \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{V_T} \Rightarrow V_{BE} = V_T \ln\left(\frac{g_m V_T}{I_S}\right) \\ \frac{I_S = 6 \times 10^{-16} \text{ A}}{g_m = \frac{1}{13 \Omega}} &\rightarrow V_{BE} = 26 \text{ mV} \cdot \ln\left(\frac{\frac{1}{13 \Omega} \times 26 \times 10^{-3}}{6 \times 10^{-16}}\right) \\ &\Rightarrow V_{BE} \approx \boxed{750 \text{ mV}} \end{aligned}$$

4. Determine V_{out} / V_{in} . (8%)

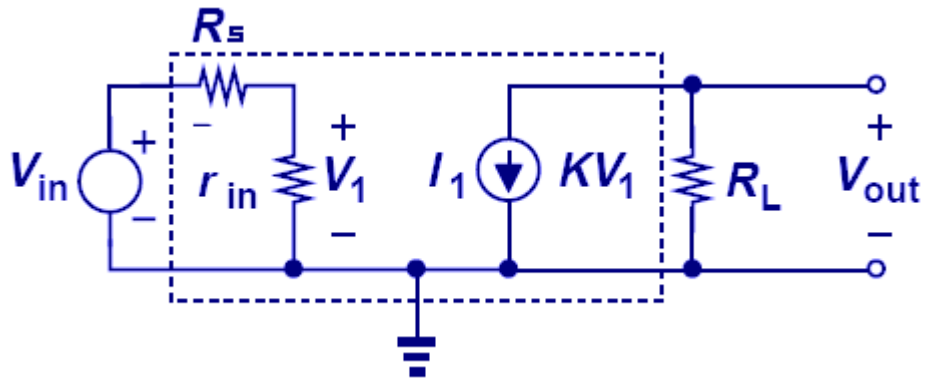


Ans:

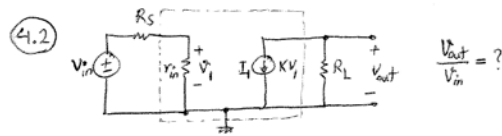

$$\left. \begin{aligned} V_1 &= \frac{r_{in}}{r_{in} + R_S} V_{in} \\ I_1 &= K V_1 \\ V_{out} &= -R_L I_1 \end{aligned} \right\} \Rightarrow V_{out} = -K R_L \frac{r_{in}}{r_{in} + R_S} V_{in}$$

$$\Rightarrow A_V = \frac{V_{out}}{V_{in}} = -K R_L \frac{r_{in}}{r_{in} + R_S}$$

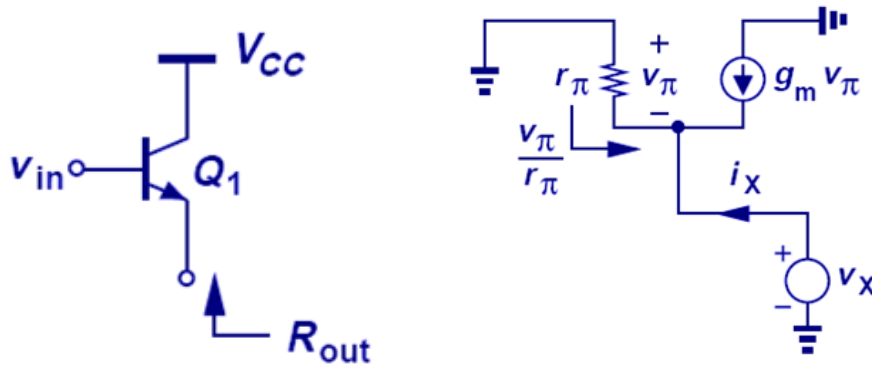5. Calculate the impedance seen at the emitter of Q_1 in the following figure. Neglect the Early effect for simplicity. (8%)




Ans:

$$g_m v_\pi + \frac{v_\pi}{r_\pi} = -i_x$$

$$\frac{v_x}{i_x} = \frac{1}{g_m + \frac{1}{r_\pi}} \quad R_{out} \approx \frac{1}{g_m} \quad (V_A = \infty)$$

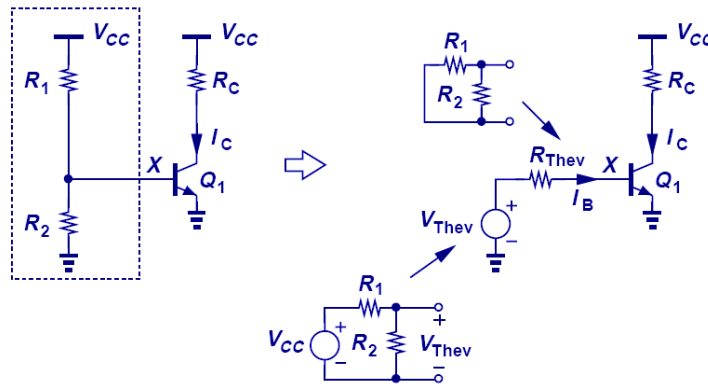6. Determine the V_{Thev} and R_{Thev} of the following figure? (8%) $R_1=170K\Omega$, $R_2=80 K\Omega$, $R_C=5 K\Omega$, $V_{CC}=2.5V$




Ans:


$$V_{Thev} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{80k}{170k + 80k} 2.5 = 800mV$$

$$R_{Thev} = R_1 \parallel R_2 = 170k \parallel 80k = 54.4k$$

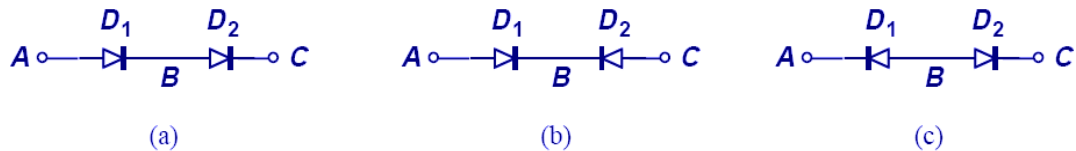
7. 1 (a) Which one of the following figure can conduct current from A to C (2%)



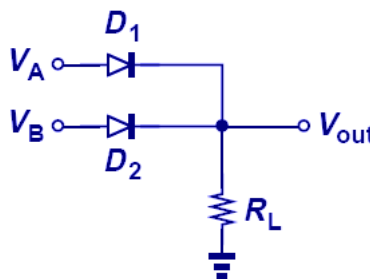
7.2 (c) What function does the following figure perform? (a) NOT (b) AND (c) OR gate (2%)



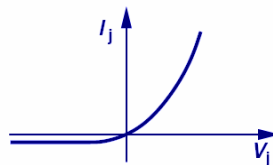
7.3 (b) What is the diode model of the following figure ? (a) Constant voltage model (b) Exponential model (c) Ideal model (2%)



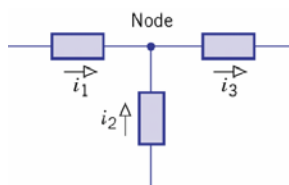7.4. (c) What is the current equation in the following figure ? (a) $i_1 = i_2 + i_3$ (b) $i_2 = i_1 + i_3$ (c) $i_3 = i_1 + i_2$ (2%)



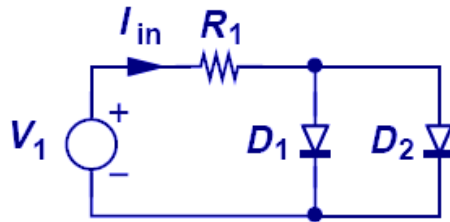8. D_1 and D_2 have different cross section areas but are otherwise identical. Determine the current flowing through each diode. (8%)



Ans:


$$I_{in} = I_{D1} + I_{D2}$$

$$V_T \ln \frac{I_{D1}}{I_{S1}} = V_T \ln \frac{I_{D2}}{I_{S2}}$$


$$\frac{I_{D1}}{I_{S1}} = \frac{I_{D2}}{I_{S2}}$$

$$I_{D1} = \frac{I_{in}}{1 + \frac{I_{S2}}{I_{S1}}} \quad I_{D2} = \frac{I_{in}}{1 + \frac{I_{S1}}{I_{S2}}}$$

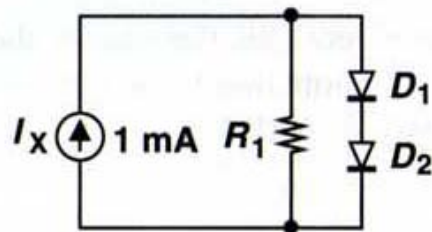9. In the circuit, determine the value of R_1 such that this resistor carries 0.5 mA. Assume $I_S = 5 \times 10^{-16}$ A for each diode. (8%)



29.

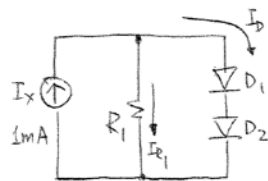

Given $I_{R1} = 0.5 \text{ mA}$,
 $I_S = 5 \cdot 10^{-16} \text{ A}$ for
each diode.


Find R_1 .

By KCL, $I_D = I_X - I_{R1} = 0.5 \text{ mA}$

$$\Rightarrow V_{D1} = V_{D2} = V_T \ln \left(\frac{I_D}{I_S} \right) = 0.026 \ln \left(\frac{0.5 \text{ mA}}{5 \cdot 10^{-16} \text{ A}} \right) \approx 0.718 \text{ V}$$

$$\therefore R_1 = \frac{V_{R1}}{I_{R1}} = \frac{2 V_{D1}}{I_{R1}} = \frac{2(0.718 \text{ V})}{0.5 \text{ mA}} = 2.87 \text{ k}\Omega$$

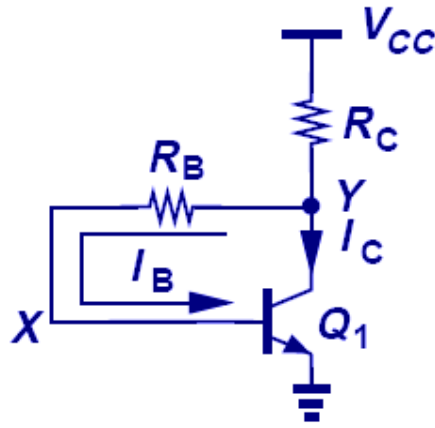10. For the self-biasing circuit, please find the current I_C respect to the V_{CC} , V_{BE} , R_C , R_B , and β . (10%)




Ans:

$$V_Y = V_{CC} - R_C I_C$$

$$V_Y = R_B I_B + V_{BE} = \frac{R_B I_C}{\beta} + V_{BE}$$

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta}}$$

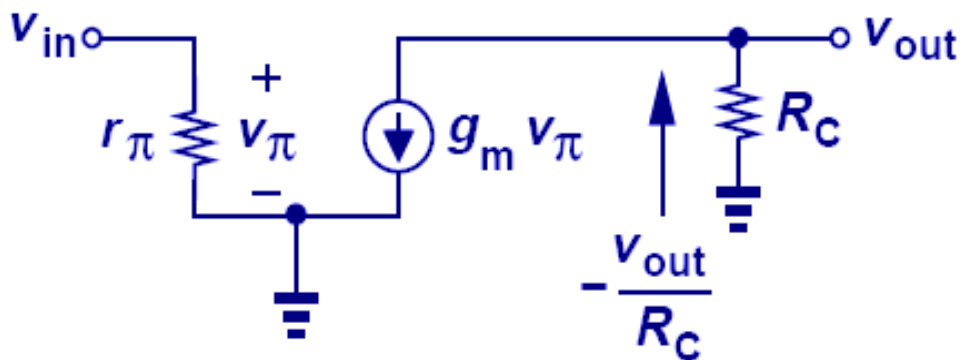11. Please find the voltage gain of the common emitter configuration. (8%) $A_v = V_{out} / V_{in}$




Ans:

$$A_v = \frac{V_{out}}{V_{in}}$$

$$-\frac{V_{out}}{R_C} = g_m v_\pi = g_m v_{in}$$

$$A_v = -g_m R_C$$

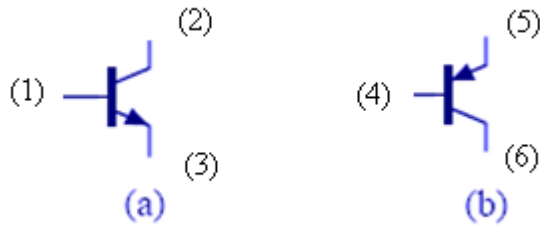12. Please use the following figure to answer the questions. (8%)




12.1 (b) Which of these two figures is PNP transistor. (please determine a or b)?

12.2 (1, 4) Which labels (1, 2, 3, 4, 5, or 6) of these two figures are the base terminals?

12.3 (2, 6) Which labels (1, 2, 3, 4, 5, or 6) of these two figures are the collector terminals?

12.4 (3, 5) Which labels (1, 2, 3, 4, 5, or 6) of these two figures are the emitter terminals?

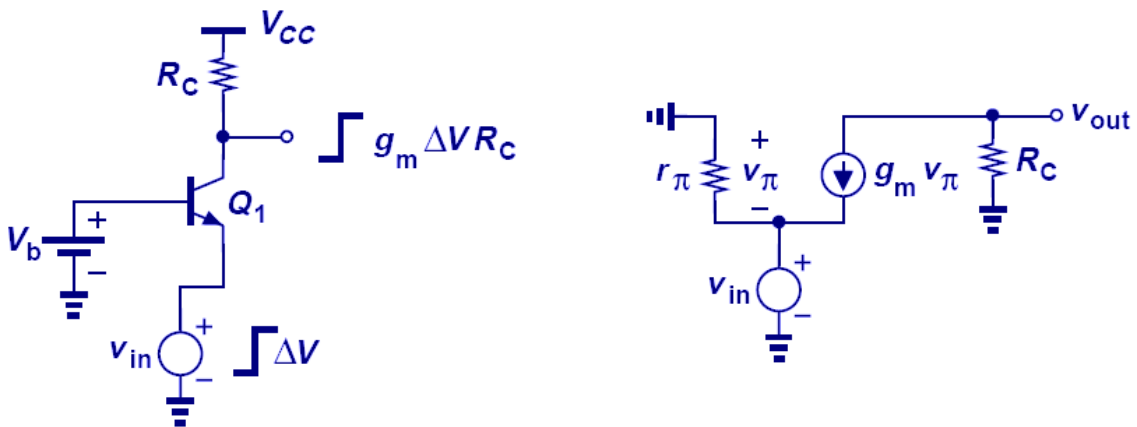
13. Please find the voltage gain of the common base configuration. (8%) $A_v = V_{out} / V_{in}$



$$-\frac{V_{out}}{R_C} = g_m v_\pi \quad v_\pi = -v_{out} / (g_m R_C)$$

$$\frac{V_{out}}{V_{in}} = g_m R_C \quad A_v = g_m R_C$$

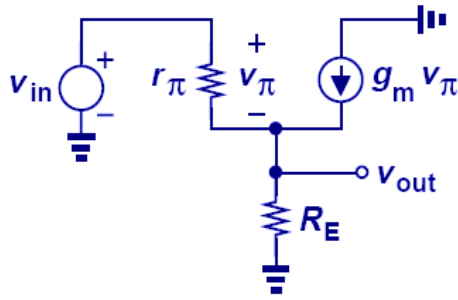14. Please find the voltage gain of the common collector configuration. (8%) $A_v = V_{out} / V_{in}$



Ans:


$$V_A = \infty$$

$$\frac{v_\pi}{r_\pi} + g_m v_\pi = \frac{v_{out}}{R_E} \Rightarrow v_\pi = \frac{r_\pi}{\beta + 1} \cdot \frac{v_{out}}{R_E}$$


$$v_{in} = v_\pi + v_{out}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + \frac{r_\pi}{\beta + 1} \cdot \frac{1}{R_E}} \quad \text{or} \quad \frac{v_{out}}{v_{in}} = \frac{1}{1 + \frac{r_\pi}{g_m r_\pi + 1} \cdot \frac{1}{R_E}}$$

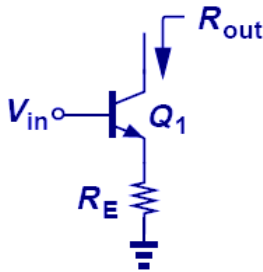15. Please find the output impedance of the following figure. (8%)



(a)

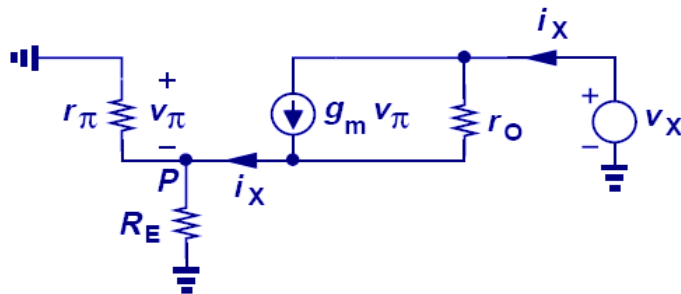

(b)

Ans:

$$v_\pi = -i_x (R_E \parallel r_\pi) \quad v_x = (i_x - g_m v_\pi) r_o - v_\pi$$

$$v_x = [i_x + g_m i_x (R_E \parallel r_\pi)] r_o + i_x (R_E \parallel r_\pi)$$

$$R_{out} = [1 + g_m (R_E \parallel r_\pi)] r_o + R_E \parallel r_\pi$$

or

$$R_{out} = r_o + (g_m r_o + 1)(R_E \parallel r_\pi)$$