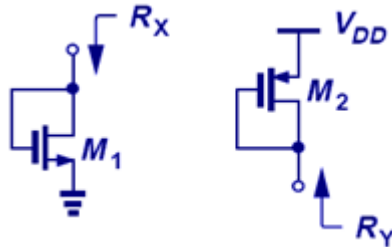



Name:

ID#

1. In the following circuit, determine the small signal resistances of R_X and R_Y . (5%)



Ans:

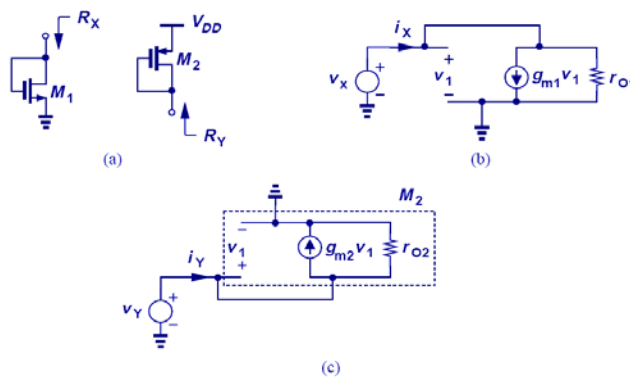


Ans:

$$R_X = \frac{v_X}{i_X} = (g_{m1}v_X + \frac{v_X}{r_{O1}}) \frac{1}{i_X} = \frac{1}{g_{m1}} \parallel r_{O1}$$


$$R_Y = \frac{v_Y}{i_Y} = (g_{m2}v_Y + \frac{v_Y}{r_{O2}}) \frac{1}{i_Y} = \frac{1}{g_{m2}} \parallel r_{O2}$$

2. Determine the region of operation of M_1 in each of circuits shown below. (10%)


$V_{THN}=0.6V$

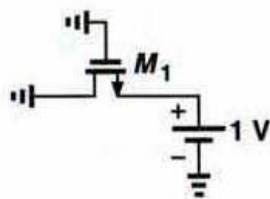


(a)

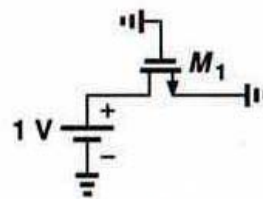

(b)

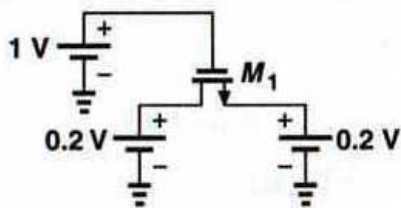

(c)

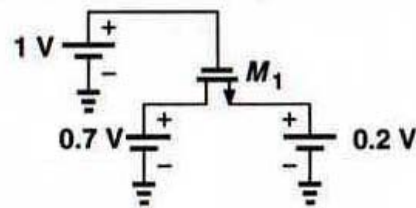


(d)


Ans:

20. (a) OFF $\because V_{GS} = 0$ ($V_{GS} < V_{TH}$)
- (b) OFF $\because V_{GS} = 0$ ($V_{GS} < V_{TH}$)
- (c) TRIODE (LINEAR) $\because V_{GS} > V_{TH}$ &
 $V_{DS} \ll 2(V_{GS} - V_{TH})$
- (d) SATURATION $\because V_{GS} > V_{TH}$ & $V_{DS} > V_{GS} - V_{TH}$

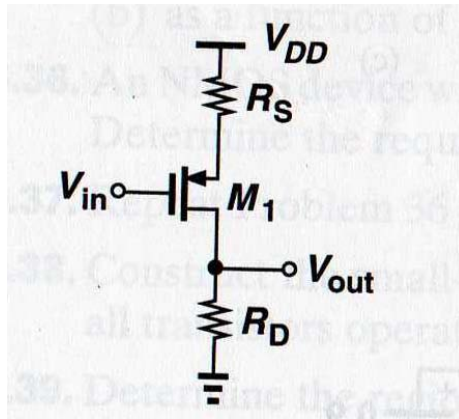3. Construct the small-signal model of the following circuit if the transistor operates in saturation and assume $\lambda=0$ (5%).



Ans:

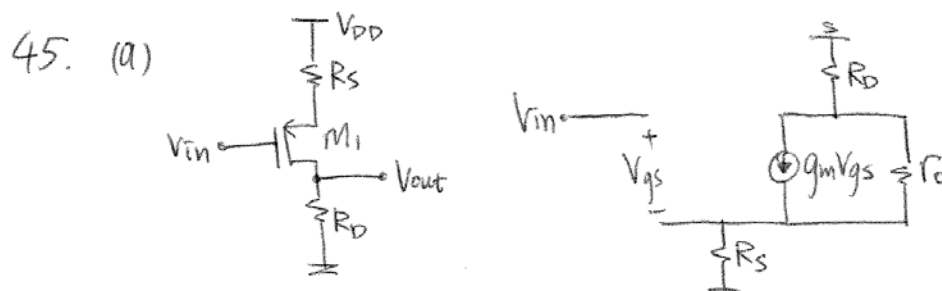

5. An NMOS device with $\lambda=0.1V^{-1}$ must provide a $g_m r_o$ of 20 with $V_{DS}=1.5V$, Determine the required value of W/L if $I_D=0.5mA$. (10%)

$$\mu_n C_{ox} = 200 \mu A/V^2 \quad \mu_p C_{ox} = 100 \mu A/V^2 \quad V_{THN} = 0.4V \quad V_{THP} = -0.4V$$

Ans:

3b. Given NMOS with $\lambda = 0.1 V^{-1}$ $g_m r_o = 20$
 $V_{DS} = 1.5V$
 determine W/L if $I_D = 0.5mA$.


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 V^{-1}) (0.5 mA)} = 20 k\Omega$$

$$\Rightarrow g_m = \frac{20}{20 k\Omega} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\therefore \frac{W}{L} = \left(\frac{20}{20 k\Omega} \right)^2 \frac{1}{2 \mu_n C_{ox} I_D}$$

$$= \left(\frac{1}{1 k\Omega} \right)^2 \frac{1}{2 \left(200 \frac{\mu A}{V^2} \right) (0.5 mA)} \approx 5.$$

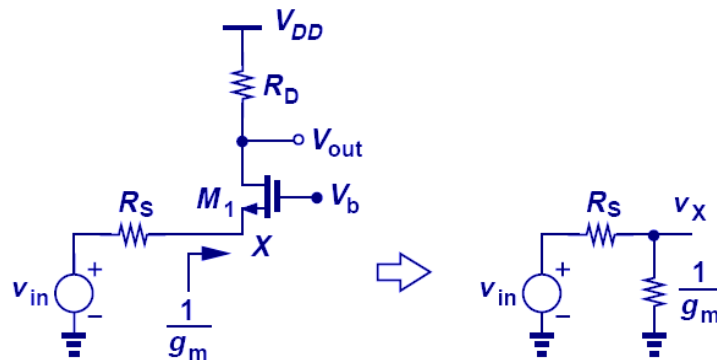6. Please find the gain of following common gate stage with signal source resistance. (10%)



Ans:


$$v_X = \frac{1}{\frac{1}{g_m} + R_S} v_{in} = \frac{1}{1 + g_m R_S} v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_X} \frac{v_X}{v_{in}} = \frac{g_m R_D}{1 + g_m R_S} = \frac{R_D}{\frac{1}{g_m} + R_S}$$

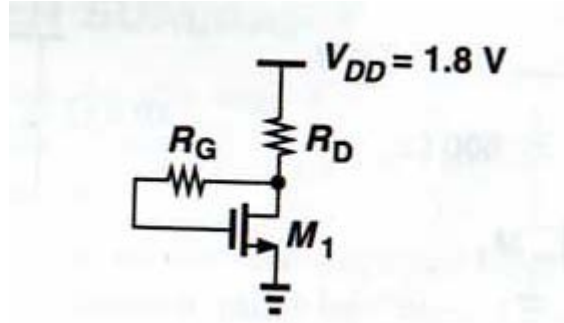7. The self-biased stage of the following figure must be designed for a drain current of 1 mA. If M_1 is to provide a transconductance of $1/(100\Omega)$, calculate the

required value of R_D . (5%)

$$\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2 \quad \mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2 \quad V_{THN} = 0.4\text{V} \quad V_{THP} = -0.4\text{V}$$



Ans:

7.6

$$I_D = 1 \text{ mA}$$


$$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{1}{100}$$

$$V_{GS} = 0.6 \text{ V}$$

$$V_{GS} = V_{DD} - I_D R_D$$

$$R_D = \boxed{1.2 \text{ k}\Omega}$$

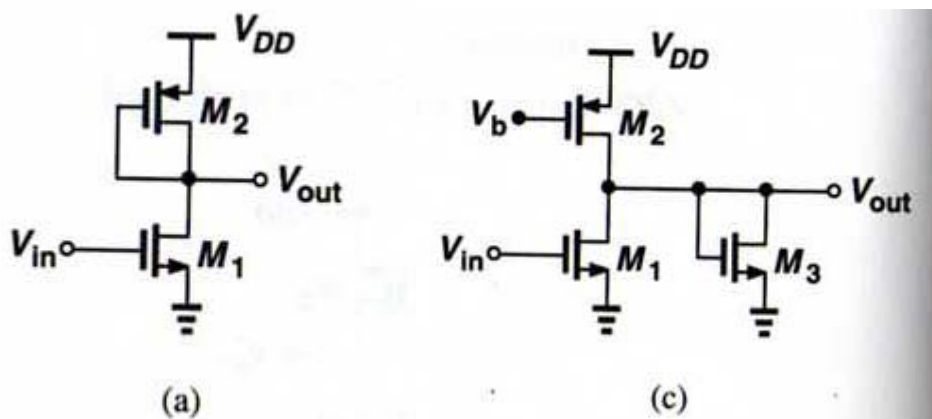8. If $\lambda \neq 0$, determine the voltage gain of the stages shown in the following Figure (5%)



Ans:


(a)

$$A_v = \boxed{-g_{m1} \left(r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

(c)

$$A_v = -g_{m1} \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)$$

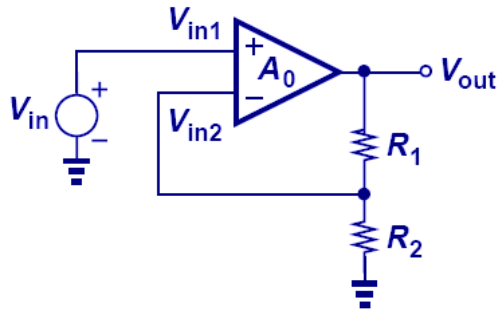9. Please find the gain of the following non-inverting amplifier (Infinite A_0) (10%).



Ans:


$$V_{in2} = \frac{R_2}{R_1 + R_2} V_{out}$$

$$V_{in2} \approx V_{in1} \approx \frac{R_2}{R_1 + R_2} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_2}$$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

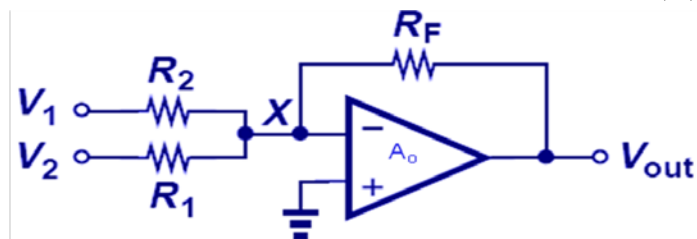
9. The OP in the following figure suffers from a finite gain. Calculate V_{out} in terms of V_1 and V_2 . (Be aware V_1 connect to R_2 , Be aware V_2 connect to R_1) (10%)



Ans:

$$\begin{aligned}
 v_{out} &= -A_0 v_X \\
 \frac{v_1 - v_X}{R_2} + \frac{v_2 - v_X}{R_1} &= \frac{v_X - v_{out}}{R_F} \\
 \frac{v_{out}}{R_F} + \frac{v_1}{R_2} + \frac{v_2}{R_1} &= \frac{v_X}{R_1 \parallel R_2 \parallel R_F} \\
 v_{out} &= -A_0 (R_1 \parallel R_2 \parallel R_F) \left(\frac{v_{out}}{R_F} + \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \\
 v_{out} \left[1 + A_0 \frac{(R_1 \parallel R_2 \parallel R_F)}{R_F} \right] &= -A_0 (R_1 \parallel R_2 \parallel R_F) \left(\frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \\
 v_{out} &= -A_0 (R_1 \parallel R_2 \parallel R_F) \frac{\frac{v_1}{R_2} + \frac{v_2}{R_1}}{1 + A_0 \frac{(R_1 \parallel R_2 \parallel R_F)}{R_F}} \\
 &= -A_0 R_F (R_1 \parallel R_2 \parallel R_F) \frac{\frac{v_1}{R_2} + \frac{v_2}{R_1}}{R_F + A_0 (R_1 \parallel R_2 \parallel R_F)} \\
 &= \boxed{- \left(\frac{v_1}{R_2} + \frac{v_2}{R_1} \right) [R_F \parallel A_0 (R_1 \parallel R_2 \parallel R_F)]}
 \end{aligned}$$

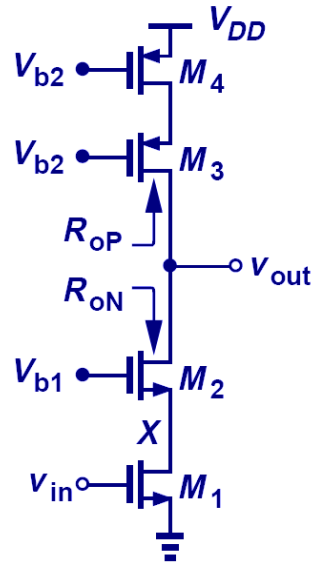10. Please find the voltage gain of the following cascode stage. (5%)



Ans:


$$R_{on} \approx g_{m2} r_{O2} r_{O1}$$

$$R_{op} \approx g_{m3} r_{O3} r_{O4}$$

$$R_{out} = R_{on} \parallel R_{op}$$

$$A_v = -g_{m1} [(g_{m2} r_{O2} r_{O1}) \parallel (g_{m3} r_{O3} r_{O4})]$$

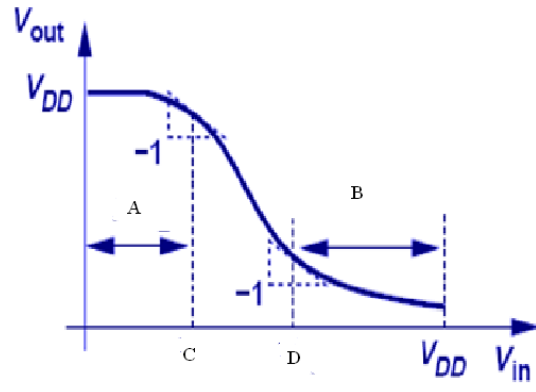11. In the following figure, I_{REF} is 0.3mA, what are the value of I_1 and I_2 ? (5%)



Ans:

- (1) V_{IL} (C) (2) V_{IH} (D) (3) NM_L (A) (4) NM_H (B)