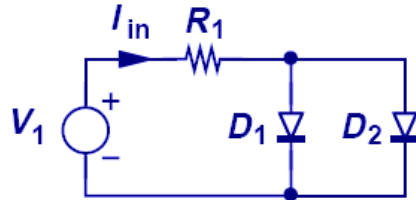


Name:

ID#

1. D_1 and D_2 have different cross section areas but are otherwise identical. Determine the current flowing through each diode in terms of I_{in} , I_{S1} , and I_{S2} . (10%)



Ans:

$$I_{in} = I_{D1} + I_{D2}$$


$$V_T \ln \frac{I_{D1}}{I_{S1}} = V_T \ln \frac{I_{D2}}{I_{S2}}$$

$$\frac{I_{D1}}{I_{S1}} = \frac{I_{D2}}{I_{S2}} \quad I_{D1} = \frac{I_{D2} I_{S1}}{I_{S2}} \quad I_{D2} = \frac{I_{D1} I_{S2}}{I_{S1}}$$


$$I_{D1} = \frac{I_{in}}{1 + \frac{I_{S2}}{I_{S1}}} \quad I_{D2} = \frac{I_{in}}{1 + \frac{I_{S1}}{I_{S2}}}$$

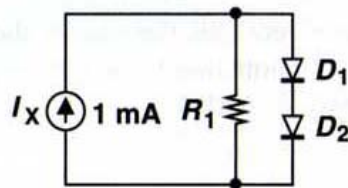2. In the circuit, determine the value of R_1 such that this resistor carries 0.5 mA.

Assume $I_s = 5 \times 10^{-16}$ A for each diode. (10%)



29.

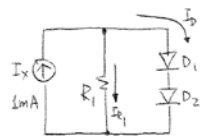

Given $I_{R1} = 0.5 \text{ mA}$,
 $I_s = 5 \cdot 10^{-16} \text{ A}$ for
 each diode.


Find R_1 .

By KCL, $I_D = I_x - I_{R1} = 0.5 \text{ mA}$

$$\Rightarrow V_{D1} = V_{D2} = V_T \ln \left(\frac{I_D}{I_s} \right) = 0.026 \ln \left(\frac{0.5 \text{ mA}}{5 \cdot 10^{-16} \text{ A}} \right) \approx 0.718 \text{ V}$$


$$\therefore R_1 = \frac{V_{R1}}{I_{R1}} = \frac{2V_{D1}}{I_{R1}} = \frac{2(0.718 \text{ V})}{0.5 \text{ mA}} = 2.87 \text{ k}\Omega$$

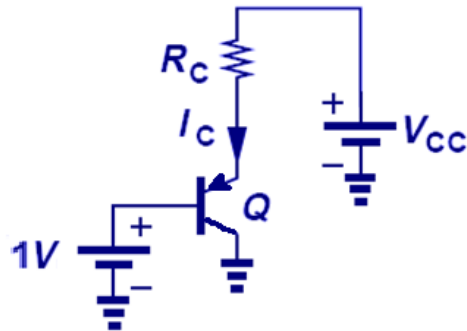3. Calculate the collector current of Q in the following figure? Assume $I_S=3 \times 10^{-17} \text{ A}$, $R_C=1 \text{ k}\Omega$, and $V_{CC}=2.5 \text{ V}$. (10%)



Ans:

④ $I_S = 3 \times 10^{-17} \text{ A}$

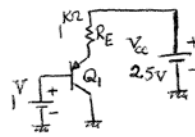

Applying KVL,

$$V_{CC} = R_E I_E + V_{EB} + 1 \text{ V} \quad \xrightarrow{I_E \approx I_C} \quad V_{CC} = R_E I_C + V_{EB} + 1 \text{ V}$$


$$\Rightarrow 2.5 = 1 \text{ k}\Omega \times 3 \times 10^{-17} e^{\frac{V_{EB}}{26 \text{ mV}}} + V_{EB} + 1 \text{ V}$$

$$\Rightarrow V_{EB} + 3 \times 10^{-14} e^{\frac{V_{EB}}{26 \text{ mV}}} = 1.5 \text{ V}$$

$$\Rightarrow \boxed{V_{EB} \approx 800.5 \text{ mV}}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} = 3 \times 10^{-17} e^{\frac{800.5}{26}} \Rightarrow \boxed{I_C \approx 0.705 \text{ mA}}$$

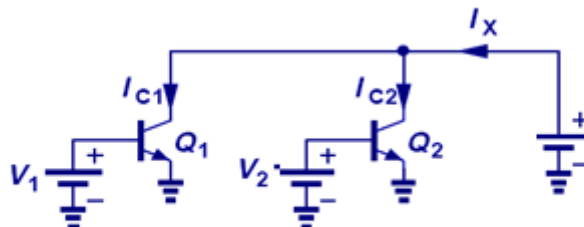4. In the following circuit Q_1 and Q_2 are identical and operate in the active mode. Determine $V_1 - V_2$ such that $I_{C1} = 10 I_{C2}$ (10%)




Ans:

$$\frac{I_{C1}}{I_{C2}} = \frac{I_S \exp \frac{V_1}{V_T}}{I_S \exp \frac{V_2}{V_T}} \quad \exp \frac{V_1 - V_2}{V_T} = 10$$


$$V_1 - V_2 = V_T \ln 10 \approx 60 \text{ mV at } T = 300^\circ \text{ K}$$

5. Draw the small-signal equivalent circuit for the amplifier shown below. (10%)


$V_A \neq \infty$

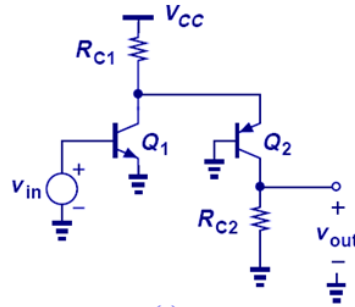


Ans:

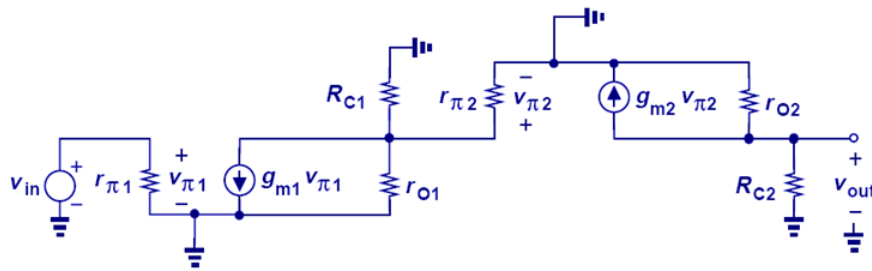

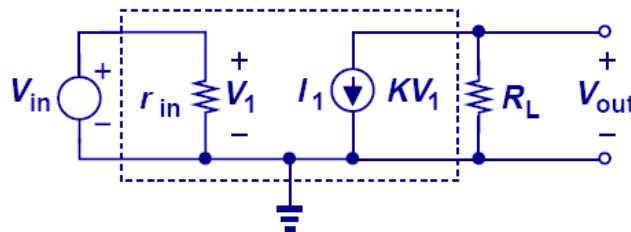6. A resistance of R_S is placed in series with the input voltage source in the following figure. Determine V_{out} / V_{in} . (10%)




Ans:

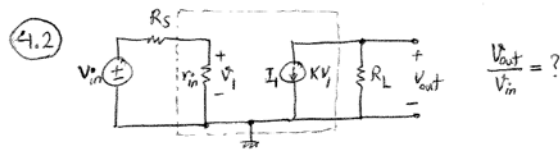


$$\left. \begin{aligned} V_1 &= \frac{r_{in}}{r_{in} + R_S} V_{in} \\ I_1 &= K V_1 \\ V_{out} &= -R_L I_1 \end{aligned} \right\} \Rightarrow V_{out} = -K R_L \frac{r_{in}}{r_{in} + R_S} V_{in}$$

$$\Rightarrow A_V = \frac{V_{out}}{V_{in}} = -K R_L \frac{r_{in}}{r_{in} + R_S}$$

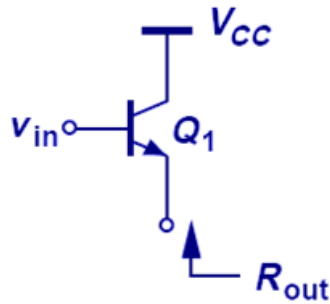
7. Calculate the impedance seen at the emitter of Q_1 in the following figure. Neglect the Early effect for simplicity. (10%)



Ans:

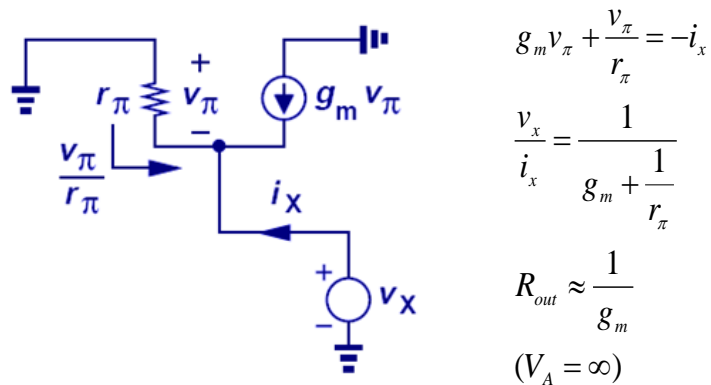

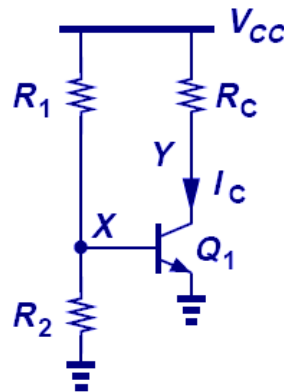8. Determine the collector and base current of the following figure if $I_S=10^{-17}A$ and $\beta=100$, $R_1=31k$, $R_2=14k$? (10%)




Ans:

$$V_x = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{14k}{31k + 14k} 2.5V = 778mV$$


$$I_C = I_S \exp \frac{V_{BE}}{V_T} = 10^{-17} \times \exp \frac{778mV}{26mV} = 98.1\mu A$$

$$I_B = I_C / \beta = 98.1 / 100 = 0.981\mu A$$

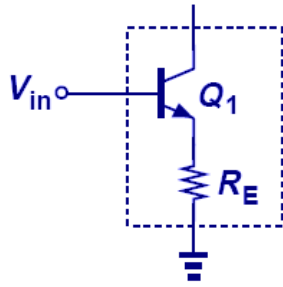9. Please find the G_m of following figure. (10%) where $G_m = \frac{i_{out}}{v_{in}}$, $V_A = \infty$



(a)

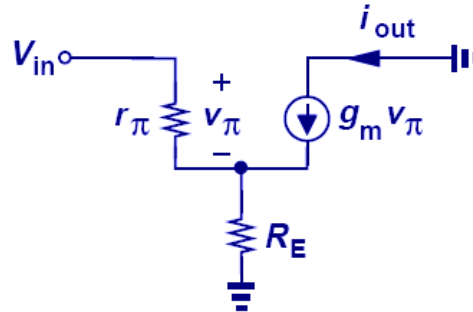


(b)

Ans:


$$V_A = \infty \quad i_{out} = g_m v_\pi \quad v_{in} = v_\pi + v_{RE} = v_\pi + \left(\frac{v_\pi}{r_\pi} + g_m v_\pi\right) R_E = v_\pi \left[1 + \left(\frac{1}{r_\pi} + g_m\right) R_E\right]$$

$$i_{out} = g_m \frac{v_{in}}{1 + (r_\pi^{-1} + g_m) R_E} \quad G_m = \frac{i_{out}}{v_{in}} \approx \frac{g_m}{1 + g_m R_E}$$

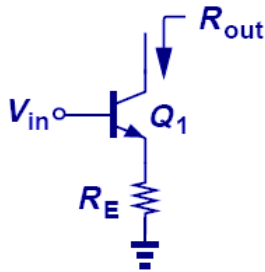10. Please find the R_{out} of following figure. (10%) $V_A \neq \infty$



(a)

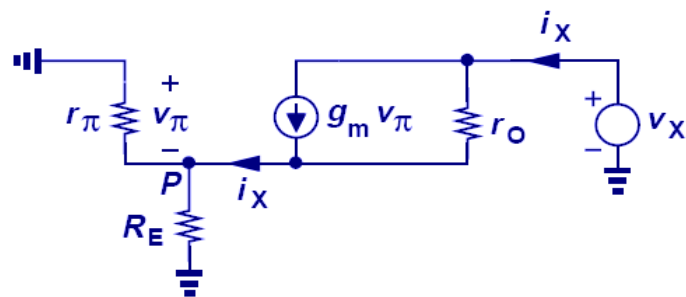

(b)

Ans:


$$v_\pi = -i_x (R_E \parallel r_\pi) \quad v_x = (i_x - g_m v_\pi) r_o - v_\pi$$

$$v_x = [i_x + g_m i_x (R_E \parallel r_\pi)] r_o + i_x (R_E \parallel r_\pi)$$

$$R_{out} = [1 + g_m (R_E \parallel r_\pi)] r_o + R_E \parallel r_\pi \quad R_{out} = r_o + (g_m r_o + 1)(R_E \parallel r_\pi)$$

$$R_{out} \approx r_o [1 + g_m (R_E \parallel r_\pi)]$$

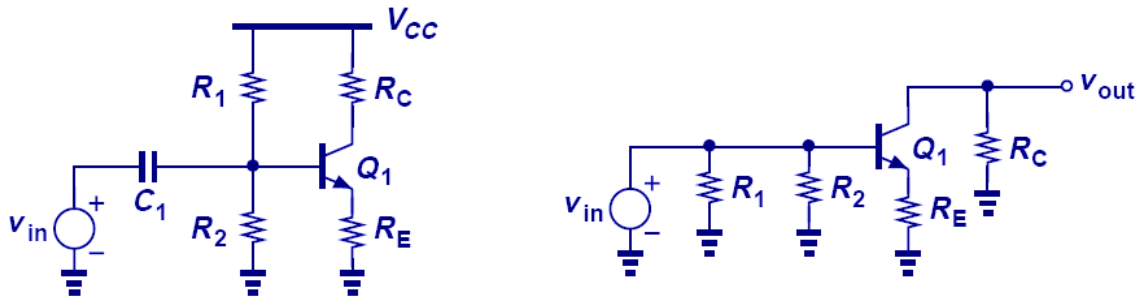11. Please find the R_{in} of following figure. (5%) $V_A = \infty$




Ans:

$$v_X = r_\pi i_X + R_E (1 + \beta) i_X$$

$$R_{inQ1} = \frac{v_X}{i_X} = r_\pi + (\beta + 1) R_E$$

$$R_{in} = [r_\pi + (\beta + 1) R_E] \parallel R_1 \parallel R_2$$

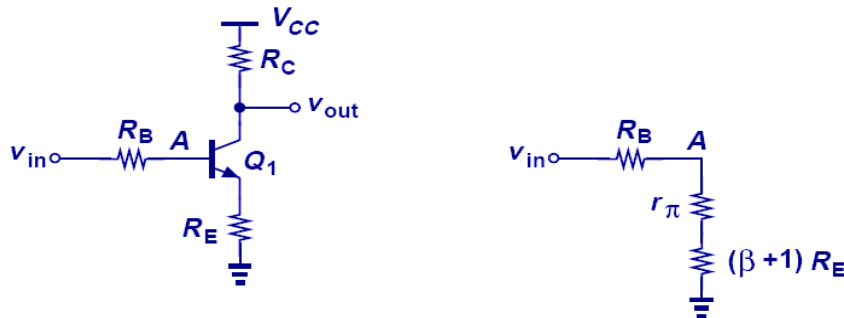12. Please find the gain of following figure. (Degenerated CE Stage with Base Resistance) (15%) $V_A = \infty$



Ans:

$$V_A = \infty \quad \frac{v_A}{v_{in}} = \frac{r_\pi + (\beta + 1) R_E}{r_\pi + (\beta + 1) R_E + R_B} \quad \frac{v_{out}}{v_A} = \frac{-g_m R_C}{1 + \left(\frac{1}{r_\pi} + g_m\right) R_E}$$

$$\frac{v_{out}}{v_{in}} = \frac{v_A}{v_{in}} \cdot \frac{v_{out}}{v_A} = \frac{r_\pi + (\beta + 1) R_E}{r_\pi + (\beta + 1) R_E + R_B} \cdot \frac{-g_m R_C}{1 + \left(\frac{1}{r_\pi} + g_m\right) R_E}$$

$$= \frac{r_\pi + (\beta + 1) R_E}{r_\pi + (\beta + 1) R_E + R_B} \cdot \frac{-g_m r_\pi R_C}{r_\pi + (1 + \beta) R_E} = \frac{-\beta R_C}{r_\pi + (\beta + 1) R_E + R_B}$$

$$A_v \approx \frac{-R_C}{\frac{1}{g_m} + R_E + \frac{R_B}{\beta + 1}}$$