

國立中山大學九十七學年度第二學期資工系數位系統期末考試題

學號：

姓名：

一、選擇與是非題 (每題 4 分, 40 分)

- ( ) 1. What kind of flip-flop is the most popular component to compose a register? ①SR ②D ③JK ④T
- ( ) 2. What kind of flip-flop is the most popular component to compose an asynchronous counter? ①SR ②D ③JK ④T。
- ( ) 3. Compared with a synchronous counter, which one is the main weakness of the asynchronous counter? ①longer delay ②larger cost (area) ③larger power consumption ④more difficult to design
- ( ) 4. What kind of storage component usually merges the input data bus and output data bus into a bi-direction I/O bus to reduce the number of I/O pins? ①Register file ②ROM ③RAM ④FIFO
- ( ) 5. How many address lines are required in a 16M×16 RAM? ①16 ②20 ③24 ④28
- ( ) 6. The BCD counter can be achieved by a 4-bit up/down counter with parallel load. The '0' must be loaded when count direction is down and counter content is 9.
- ( ) 7. To extend the address space (increase the number of memory words), a larger RAM can be composed of some smaller RAMs with parallel connection (並聯).
- ( ) 8. Compared with RAM, register file has shorter access time and smaller capacity (memory words).
- ( ) 9. The control unit in a digital system is a sequential circuit and it can be regarded as a finite state machine (FSM).
- ( ) 10. The datapath in a digital system is a combinatorial circuit.

二、問答題 (80 分)

1. Derive (a) excitation equations, (b) a next-state equation, (c) a state/output table, and (d) a state diagram for the circuit shown in Fig. 1. (18%)
2. Using the synthesis procedure for FSM models, design a synchronous counter that counts in the sequence 0, 1, 3, 5, 0, 1, 3, 5, ..., using natural binary encoding as shown in Fig. 2 and: (a) D flip-flops (b) JK flip-flops. (18%)
3. Design a 4-bit register that can load new data and swap the most-significant and least-significant bits as shown in Table 1. (10%)
4. Construct a 4-bit asynchronous counter using: (a) T flip-flops (b) D flip-flops. (12%)
5. (1) Please fill in the blanks in Table 2 with the control words of one's counter example. (14%)  
 (2) Please describe the operation of the datapath shown in Fig. 3 to perform  $Ocount := 0$  and  $Ocount := Ocount + Temp$ . (8%)

Flip-flop name	Flip-flop symbol	Characteristic table	Characteristic equation	Excitation table	
D		$\begin{array}{c c} D & Q(next) \\ \hline 0 & 0 \\ 1 & 1 \end{array}$	$Q(next) = D$	$\begin{array}{c cc c} Q & Q(next) & D \\ \hline 0 & 0 & 0 \\ 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 1 & 1 \end{array}$	
		$\begin{array}{c c} T & Q(next) \\ \hline 0 & Q \\ 1 & Q' \end{array}$		$\begin{array}{c cc c} Q & Q(next) & T \\ \hline 0 & 0 & 0 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{array}$	
		$\begin{array}{c cc c} J & K & Q(next) \\ \hline 0 & 0 & Q \\ 0 & 1 & 0 \\ 1 & 0 & 1 \\ 1 & 1 & Q' \end{array}$		$\begin{array}{c cc cc} Q & Q(next) & J & K \\ \hline 0 & 0 & 0 & X \\ 0 & 1 & 1 & X \\ 1 & 0 & X & 1 \\ 1 & 1 & X & 0 \end{array}$	
T		$\begin{array}{c c} T & Q(next) \\ \hline 0 & Q \\ 1 & Q' \end{array}$	$Q(next) = TQ' + T'Q$		
JK		$\begin{array}{c cc c} J & K & Q(next) \\ \hline 0 & 0 & Q \\ 0 & 1 & 0 \\ 1 & 0 & 1 \\ 1 & 1 & Q' \end{array}$	$Q(next) = JQ' + K'Q$		

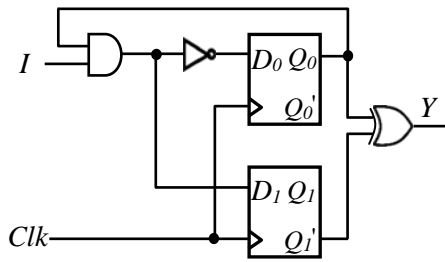


Fig. 1

$S_1$	$S_0$	Operation	Next State
0	X	No Change	$Q_3 Q_2 Q_1 Q_0$
1	0	Load Input	$I_3 I_2 I_1 I_0$
1	1	Swap	$Q_1 Q_0 Q_3 Q_2$

Table 1

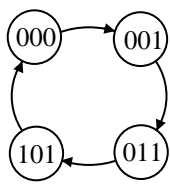


Fig. 2

Control Words	IE	Write address	Read address A	Read address B	ALU operation	Shifter operation	OE	
1	1	R1	X	X	X	X	0	
2	0	R3	R0	R0	add	pass	0	
3	0						0	
4	0						0	
5	0							0
6	0						0	
7	0	none	R3	0	add	pass	1	

Table 2

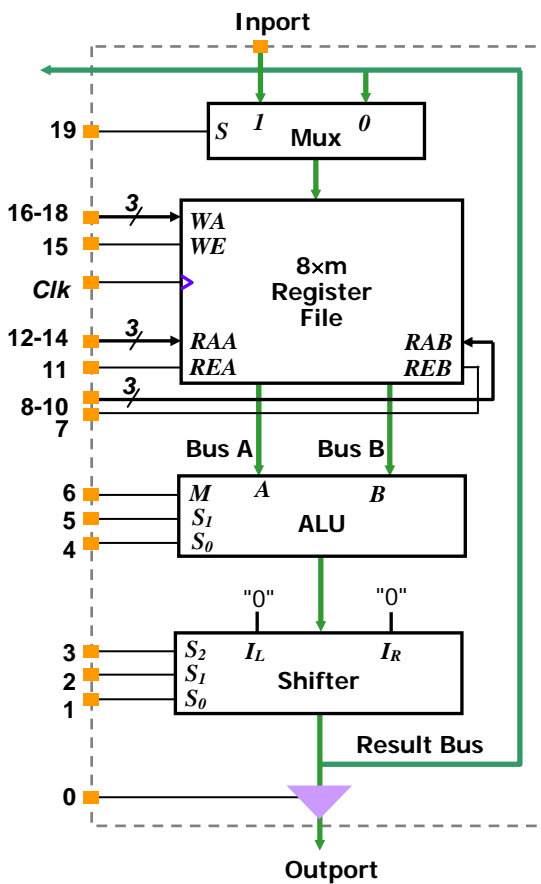


Fig. 3

1. Data := Inport
2. Ocount := 0
3. Mask := 1  
while Data ≠ 0 repeat
4. Temp := Data AND Mask
5. Ocount := Ocount + Temp
6. Data := Data >> 1
- end while
7. Output := Ocount

Data => R1  
Mask => R2  
Ocount => R3  
Temp => R4

$S_2$	$S_1$	$S_0$	Shift Operations
0	0	0	pass
0	0	1	pass
0	1	0	not used
0	1	1	not used
1	0	0	shift left
1	0	1	rotate left
1	1	0	shift right
1	1	1	rotate right

M	$S_1$	$S_0$	ALU Operations
0	0	0	complement A
0	0	1	AND
0	1	0	EX-OR
0	1	1	OR
1	0	0	decrement A
1	0	1	add
1	1	0	subtract
1	1	1	increment A