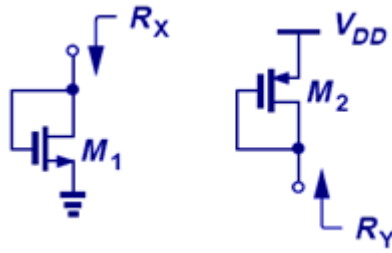



Name:

ID#

1. In the following circuit, determine the small signal resistances of  $R_X$  and  $R_Y$ . (5%)




Ans:

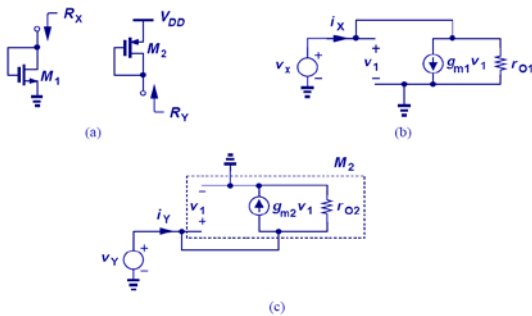

$$R_X = \frac{v_X}{i_X} = (g_{m1}v_X + \frac{v_X}{r_{O1}}) \frac{1}{i_X} = \frac{1}{g_{m1}} \parallel r_{O1}$$

$$R_Y = \frac{v_Y}{i_Y} = (g_{m2}v_Y + \frac{v_Y}{r_{O2}}) \frac{1}{i_Y} = \frac{1}{g_{m2}} \parallel r_{O2}$$

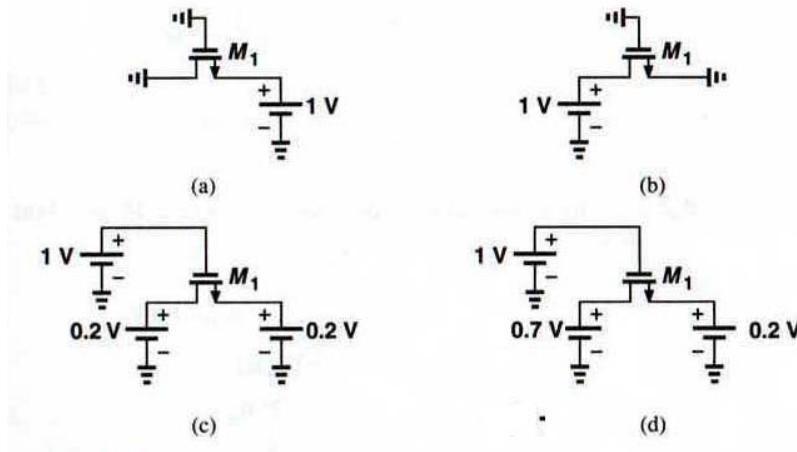2. Determine the region of operation of  $M_1$  in each of circuits shown below. (10%)  $V_{THN}=0.6V$



Ans:


20. (a) OFF  $\because V_{GS} = 0$  ( $V_{GS} < V_{TH}$ )

(b) OFF  $\because V_{GS} = 0$  ( $V_{GS} < V_{TH}$ )


(c) TRIODE (LINEAR)  $\because V_{GS} > V_{TH}$  &  
 $V_{DS} \ll 2(V_{GS} - V_{TH})$

(d) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

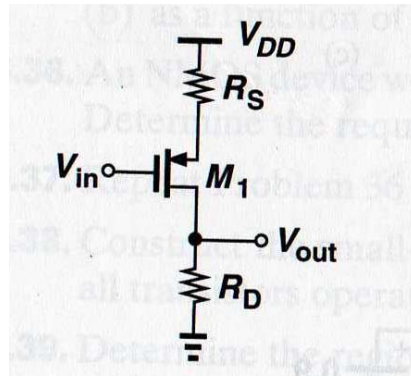3. Construct the small-signal model of the following circuit if the transistor operates in saturation and assume  $\lambda=0$  (5%).



Ans:

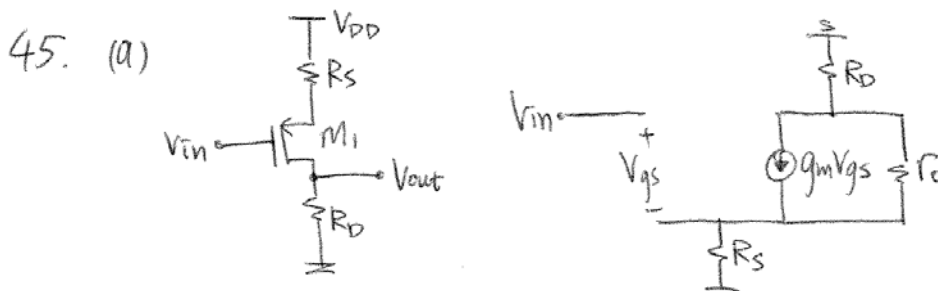

5. An NMOS device with  $\lambda=0.1V^{-1}$  must provide a  $g_m r_o$  of 20 with  $V_{DS}=1.5V$ , Determine the required value of  $W/L$  if  $I_D=0.5mA$ . (5%)

$$\mu_n C_{ox} = 200 \mu A/V^2 \quad \mu_p C_{ox} = 100 \mu A/V^2 \quad V_{THN} = 0.4V \quad V_{THP} = -0.4V$$

Ans:

3b. Given NMOS with  $\lambda = 0.1 V^{-1}$   $g_m r_o = 20$   
 $V_{DS} = 1.5V$   
 determine  $W/L$  if  $I_D = 0.5mA$ .


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 V^{-1})(0.5 mA)} = 20 k\Omega$$

$$\Rightarrow g_m = \frac{20}{20 k\Omega} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\therefore \frac{W}{L} = \left(\frac{20}{20 k\Omega}\right)^2 \frac{1}{2 \mu_n C_{ox} I_D}$$

$$= \left(\frac{1}{k\Omega}\right)^2 \frac{1}{2 \left(200 \frac{\mu A}{V^2}\right) (0.5 mA)} \approx 5.$$

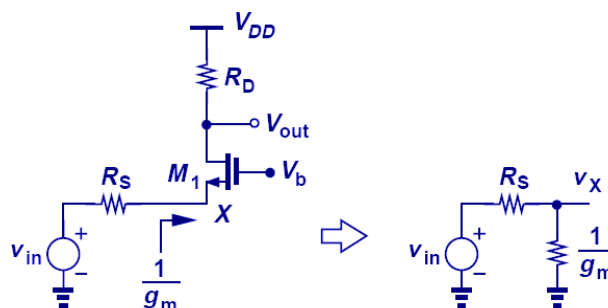6. Please find the gain of following common gate stage with signal source resistance. (5%)




Ans:

$$v_X = \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_S} v_{in} = \frac{1}{1 + g_m R_S} v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_X} \frac{v_X}{v_{in}} = \frac{g_m R_D}{1 + g_m R_S} = \frac{R_D}{\frac{1}{g_m} + R_S}$$

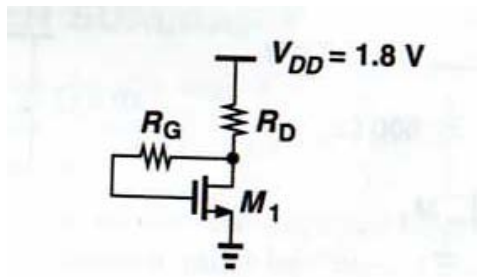7. The self-biased stage of the following figure must be designed for a drain current of 1 mA. If  $M_1$  is to provide a transconductance of  $1/(100\Omega)$ , calculate the required value of  $R_D$ . (5%)

$\mu_n C_{ox} = 200 \mu A/V^2$       $\mu_p C_{ox} = 100 \mu A/V^2$       $V_{THN} = 0.4V$     $V_{THP} = -0.4V$



Ans:

7.6

$$I_D = 1 \text{ mA}$$


$$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{1}{100}$$

$$V_{GS} = 0.6 \text{ V}$$

$$V_{GS} = V_{DD} - I_D R_D$$

$$R_D = \boxed{1.2 \text{ k}\Omega}$$

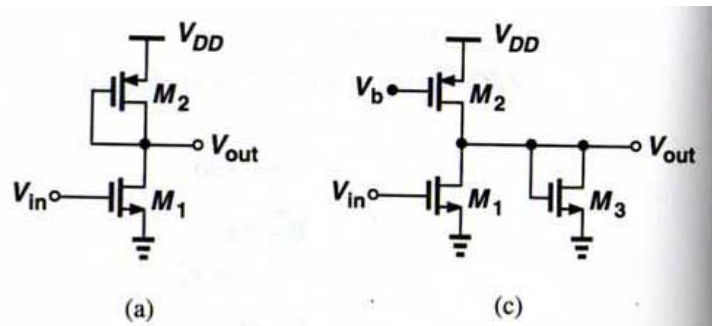8. If  $\lambda \neq 0$ , determine the voltage gain of the stages shown in the following Figure (5%)



Ans:


(a)

$$A_v = \boxed{-g_{m1} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

(c)

$$A_v = \boxed{-g_{m1} \left( r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)}$$

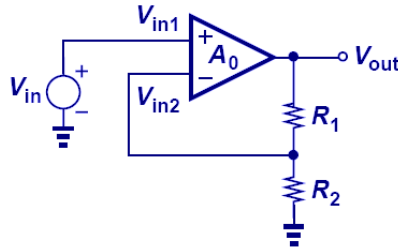9. Please find the gain of the following non-inverting amplifier (Infinite  $A_0$ ) (5%)



Ans:


$$V_{in2} = \frac{R_2}{R_1 + R_2} V_{out}$$

$$V_{in2} \approx V_{in1} \approx \frac{R_2}{R_1 + R_2} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_2}$$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

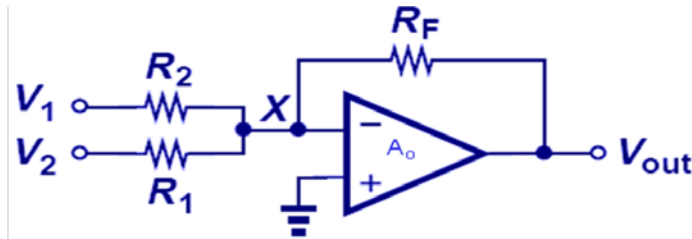9. The OP in the following figure suffers from a finite gain. Calculate  $V_{out}$  in terms of  $V_1$  and  $V_2$ . (Be aware  $V_1$  connect to  $R_2$ , Be aware  $V_2$  connect to  $R_1$ ) (10%)



Ans:

8.31

$$v_{out} = -A_0 v_X$$

$$\frac{v_1 - v_X}{R_2} + \frac{v_2 - v_X}{R_1} = \frac{v_X - v_{out}}{R_F}$$

$$\frac{v_{out}}{R_F} + \frac{v_1}{R_2} + \frac{v_2}{R_1} = \frac{v_X}{R_1 \parallel R_2 \parallel R_F}$$

$$v_{out} = -A_0 (R_1 \parallel R_2 \parallel R_F) \left( \frac{v_{out}}{R_F} + \frac{v_1}{R_2} + \frac{v_2}{R_1} \right)$$


$$v_{out} \left[ 1 + A_0 \frac{(R_1 \parallel R_2 \parallel R_F)}{R_F} \right] = -A_0 (R_1 \parallel R_2 \parallel R_F) \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right)$$

$$v_{out} = -A_0 (R_1 \parallel R_2 \parallel R_F) \frac{\frac{v_1}{R_2} + \frac{v_2}{R_1}}{1 + A_0 \frac{(R_1 \parallel R_2 \parallel R_F)}{R_F}}$$

$$= -A_0 R_F (R_1 \parallel R_2 \parallel R_F) \frac{\frac{v_1}{R_2} + \frac{v_2}{R_1}}{R_F + A_0 (R_1 \parallel R_2 \parallel R_F)}$$

$$= - \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) [R_F \parallel A_0 (R_1 \parallel R_2 \parallel R_F)]$$

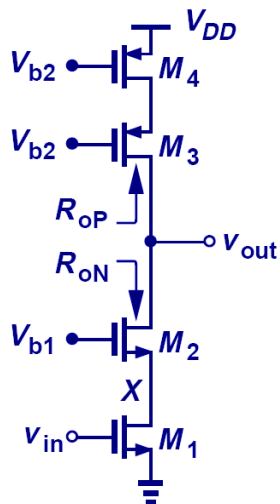10. Please find the voltage gain of the following cascode stage. (5%)



Ans:


$$R_{on} \approx g_{m2} r_{O2} r_{O1}$$

$$R_{op} \approx g_{m3} r_{O3} r_{O4}$$

$$R_{out} = R_{on} \parallel R_{op}$$

$$A_v = -g_{m1} [(g_{m2} r_{O2} r_{O1}) \parallel (g_{m3} r_{O3} r_{O4})]$$

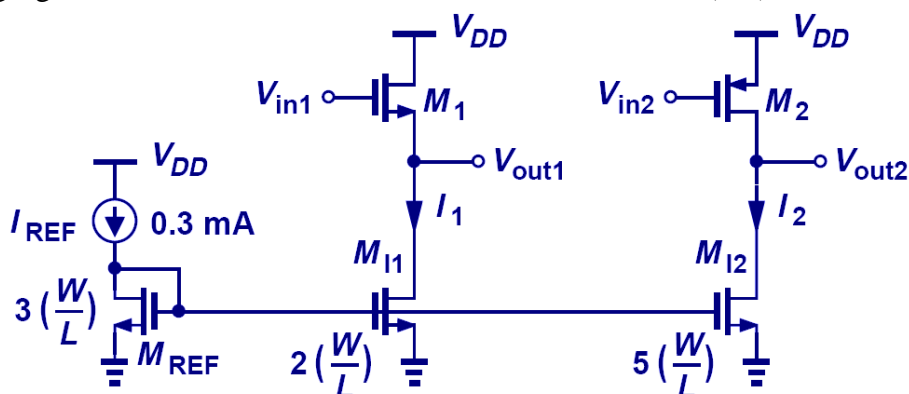11. In the following figure,  $I_{REF}$  is 0.3mA, what are the value of  $I_1$  and  $I_2$ ? (5%)




Ans:  $I_1 = (2/3) \cdot 0.3 = 0.2 \text{mA}$ ,

$I_2 = (5/3) \cdot 0.3 = 0.5 \text{mA}$


12. Please draw a CMOS logic gate which performs the following function:  $\overline{(A + D) \cdot (B + C)}$ . (5%)

Ans:

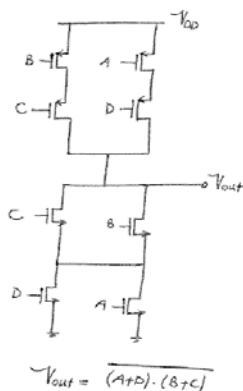

13. Please fill in A, B, C, or D by identify the correct definition in the following figure. (10%)

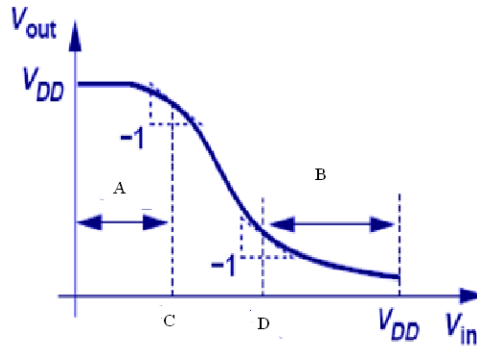- (1)  $V_{IL}$  ( ) (2)  $V_{IH}$  ( ) (3)  $NM_L$  ( ) (4)  $NM_H$  ( )





Ans:

- (1)  $V_{IL}$  ( C ) (2)  $V_{IH}$  ( D ) (3)  $NM_L$  ( A ) (4)  $NM_H$  ( B )

14. Consider the MOS current mirror shown below, and assume  $M_1$  and  $M_{REF}$  are identical, but  $\lambda \neq 0$ . (10%)

(1) How should  $V_{DS1}$  be chosen so that  $I_{copy1}$  is exactly equal to  $I_{REF}$ ?

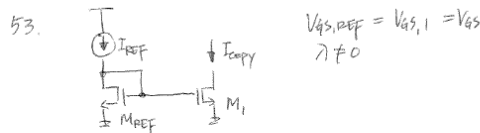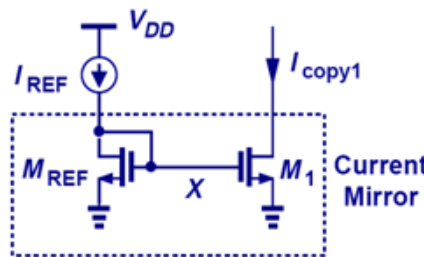(2) Determine the error be chosen in  $I_{copy1}$  with respect to  $I_{REF}$  if  $V_{DS1}$  is equal to  $V_{GS} - V_{TH}$  (so that  $M_1$  resides at the edge of saturation).



$$(a) \quad I_{REF} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS})$$


$$I_{copy} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS,1})$$

$$\text{For } I_{REF} = I_{copy} \Rightarrow V_{GS,1} = V_{GS}$$


$$(b) \quad \frac{I_{REF}}{I_{copy}} = \frac{1 + \lambda V_{GS}}{1 + \lambda (V_{GS} - V_{TH})}$$

$$\Rightarrow I_{copy} = I_{REF} \left(1 - \frac{\lambda V_{TH}}{1 + \lambda V_{GS}}\right)$$

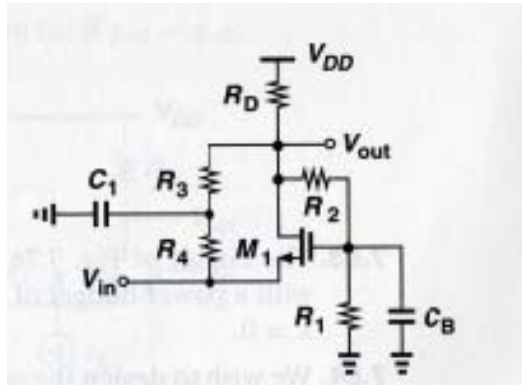15. Calculate the voltage gain of the following circuit. Assume  $\lambda=0$  and the capacitors are very large. (5%)




Ans:

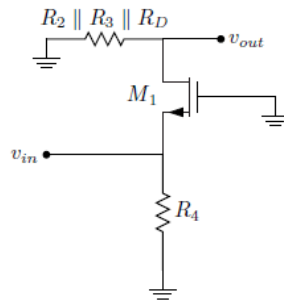

$$A_v = \boxed{g_m (R_2 \parallel R_3 \parallel R_D)}$$

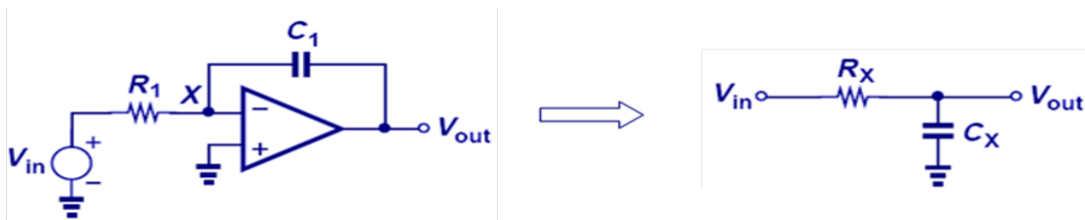16. Determine the transfer function of the following circuit. (5%)



Ans:

$$\frac{V_{in} - V_X}{R_1} = \frac{V_X - V_{out}}{\frac{1}{C_1 s}} \quad V_X = \frac{V_{out}}{-A_0}$$

$$\frac{V_{out}}{V_{in}} = \frac{-1}{\frac{1}{A_0} + \left(1 + \frac{1}{A_0}\right) R_1 C_1 s} \quad s_p = \frac{-1}{(A_0 + 1) R_1 C_1}$$