

國立中山大學九十八學年度第二學期資工系數位系統期末考試

學號：

姓名：

一、選擇與是非題 (每題 3 分, 12 分)

- () 1. 下列何者錯誤? ①latch is level triggered ②flip-flop is edge triggered ③area of latch > area of flip-flop ④For a D flip-flop, D input must be no change after the application of the positive Clk pulse. The time is called hold time.
- () 2. 下列那一種記憶元件的讀寫速度最快且所需面積最大? ①register file ②SRAM ③DRAM ④Flash memory.
- () 3. 下列何者屬於 volatile memory? ①DRAM ②ROM ③ EEPROM ④ Flash memory.
- () 4. A k -bit ring counter circulates a single bit among the flip-flops to provide k distinguishable states, and a k -bit switch-tail ring counter will go through a sequence of $2k$ distinguishable states.

二、問答題 (98 分)

1. Derive the following terms for the sequential circuit shown in Fig. 1.

- (1) Input (Excitation) equations (5%)
- (2) State equations and output equation (6%)
- (3) State table (8%)
- (4) State diagram (6%)

2. Design the synchronous sequential circuit using JK flip-flops with the state diagram as shown in Fig. 2.

- (1) Complete the state table as shown in Table 1. (8%)
- (2) Derive the simplified flip-flop input (excitation) equations. (6%)
- (3) Complete the logic diagram as shown in Fig. 3. (5%)

Table 3

A	B	C	F_1	F_2
0	0	0	0	1
0	0	1	0	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	0

3. Design a four-bit count down binary (synchronous) counter using T flip-flops as shown in Fig. 4.

- (1) Complete the state table as shown in Table 2. (7%)
- (2) Derive the simplified flip-flop input (excitation) equations. (8%)
- (3) Complete the logic diagram as shown in Fig. 4. (6%)

4. Please answer the problems about RAM.

- (1) Briefly explain the read and write operations of the 4×4 RAM and the memory cell as shown in Fig. 5(a) and 5(b), respectively. (10%)
- (2) Explain the address multiplexing for a 64K DRAM as shown in Fig. 6. (8%)

5. Using a $3 \times 4 \times 2$ PLA shown in Fig. 7, implement the truth table shown in Table 3. (15%)

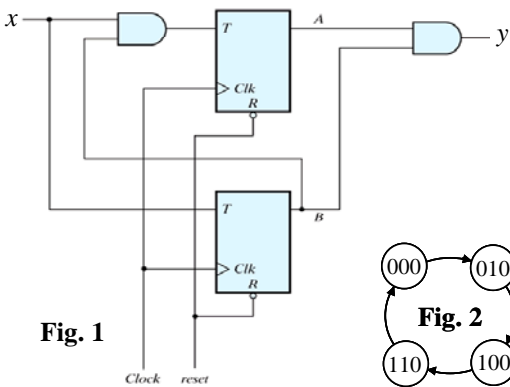


Fig. 1

 


Fig. 2

Table 1

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C

國立中山大學九十八學年度第二學期資工系數位系統期末考試

學號：

姓名：

Table 2

Present State				Next State				Flip-flop Inputs			
A_3	A_2	A_1	A_0	A_3	A_2	A_1	A_0	T_{A3}	T_{A2}	T_{A1}	T_{A0}
1	1	1	1	1	1	1	0				
1	1	1	0	1	1	0	1				
1	1	0	1	1	1	0	0				
1	1	0	0	1	0	1	1				
1	0	1	1	1	0	1	0				
1	0	1	0	1	0	0	1				
1	0	0	1	1	0	0	0				
1	0	0	0	0	1	1	1				
0	1	1	1	0	1	1	0				
0	1	1	0	0	1	0	1				
0	1	0	1	0	1	0	0				
0	1	0	0	0	0	1	1				
0	0	1	1	0	0	1	0				
0	0	1	0	0	0	0	1				
0	0	0	1	0	0	0	0				
0	0	0	0	1	1	1	1				

 


Fig. 3

 


Fig. 4

 


Fig. 5(b)

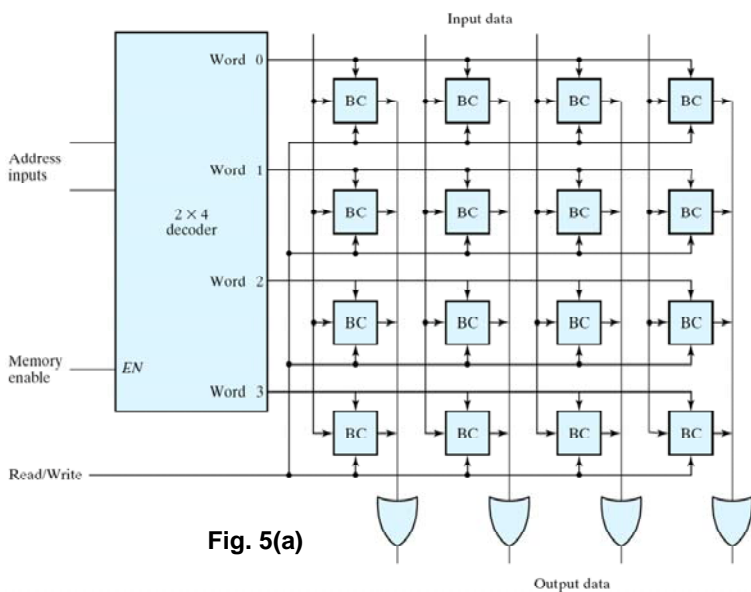


Fig. 5(a)

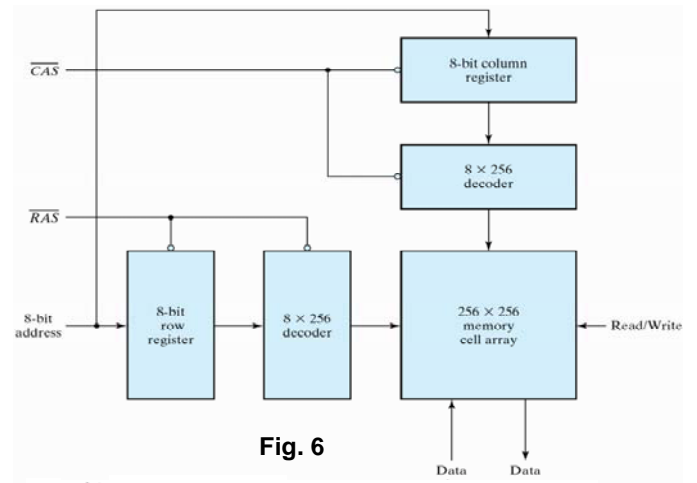


Fig. 6

 


Fig. 7