

國立中山大學九十八學年度第二學期資工系數位系統期中考試

學號：

姓名：

一、選擇與是非題 (每題 3 分, 15 分)

- () 1. 下列何者錯誤？①在 2's-complement 表示式中, 可將減數(subtrahend)取 2's complement 後與被減數相加即可以加法取代減法, 但 carry out of sign-bit position 必須捨棄 ②gray code 中任意連續兩個數碼之間的 distance 必定等於 1 ③若將 parity bit 加在左邊, 則 ASCII T=1010100 的 odd parity 為 11010100 ④sign-magnitude 表示式 1111011_2 代表 -58_{10} 。
- () 2. 下列何者錯誤？①product of maxterms is canonical form ② $F(x, y, z) = y' + zy + x'yz'$ is standard form ③ $F(w, x, y, z) = wx + y(z+w)$ is standard form ④product of sums is standard form。
- () 3. 下列何者錯誤？① $x+yz = (x+y)(x+z)$ ② $x(x'+y) = xy$ ③ $(x\oplus y)' = x'y + xy'$ ④ $x\oplus y = y\oplus x$ 。
- () 4. 對於 Boolean algebra 而言, $x+(y-z) = (x+y)(x+z)$ 成立而且的 identity element 為 0。
- () 5. 對於 three-bit message x, y, z 而言, 假如 parity bit $P = x\oplus y\oplus z$ 且 parity check $C = x\oplus y\oplus z\oplus P$, 則 $C = 1$ 代表奇數個資料位元發生錯誤。

二、問答題 (85 分)

1. (1) Find the two's complement of the following binary number: 10001111 (5%)
 (2) Use De Morgan's law to derive the complement of the following Boolean function: $F(x, y, z) = xy + y(x'+z)$, $F' = ?$ (5%)
2. (1) Derive the sum-of-minterms and the product-of-maxterms canonical forms for Boolean function $F(w, x, y, z) = (w+x+y'+z)(w'+x'+z)(y+z)$. (10%)
 (2) Using the Karnaugh map to find the simplest sum-of-products and product-of-sums of this Boolean function. (10%)
 (3) Implement the function $F(w, x, y, z)$ with NAND-NAND logic, draw the logic diagram. (10%)
3. Using the Karnaugh map to find all the simplest sum-of-products of Boolean function $F(v, w, x, y, z) = \sum m(0, 1, 3, 7, 8, 9, 11, 14, 15, 16, 17, 19, 24, 25, 27, 30)$. (12%)
4. Derive the truth table, the simplified Boolean functions, and draw the logic diagram of the following circuits.
 (1) Design the half adder (inputs: x, y and outputs: C, S) with XOR gate. (6%)
 (2) Design the full adder (inputs: x, y, z and outputs: C, S) with two half adders (with XOR gate) and an OR gate. (8%)
5. Design the carry lookahead generator of a 4-bit carry lookahead adder with inputs $A = A_3A_2A_1A_0$ and $B = B_3B_2B_1B_0$, and outputs $S = S_3S_2S_1S_0$ and C_4 .
 (1) Let carry propagate $P_i = A_i\oplus B_i$ and carry generate $G_i = A_iB_i$, then sum $S_i = P_i\oplus C_i$ and carry $C_{i+1} = G_i + P_iC_i$, where $0 \leq i \leq 3$. Please derive the Boolean functions of C_1, C_2 , and C_3 with input variables G_i, P_i and C_0 . (10%)
 (2) Draw the logic diagram of carry lookahead generator to generate C_1, C_2 , and C_3 . (8%)
6. Design a 4-bit two's complement adder-subtractor with inputs $A = A_3A_2A_1A_0, B = B_3B_2B_1B_0$, and M , and outputs $S = S_3S_2S_1S_0, C_4$, and V . If $M = 0$, the adder-subtractor performs $A+B$. Otherwise, it performs $A-B$ (i.e., $A+B'+1$).
 (1) $V = 0$ denotes that no overflow occurs and $V = 1$ denotes that an overflow occurs. Design the circuit to generate V . (5%)
 (2) Draw the logic diagram of 4-bit two's complement adder-subtractor. (6%)

	yz	00	01	11	10
wx		00	01	11	10
00		0	1	3	2
01		4	5	7	6
11		12	13	15	14
10		8	9	11	10

