 



**Dept. of Computer Science and Engineering, National Sun Yat-sen Univ.  
Second Semester of 2019 PhD Qualifying Exam**

Subject : Electronics


1. (10%) The following figure models a gate driving wires to two destinations. The gate is represented as a voltage source with effective resistance  $R$ . The two receivers are located at nodes 3 and 4. The wire to node 3 is long enough that it is represented with a pair of  $\pi$ -segments, while the wire to node 4 is represented with a single segment. We assume the parasitic capacitances in this circuits all are equal to  $C$  and the wire resistance in a single  $\pi$ -segment is  $R$ .



 - a. (5%) Please draw the effective RC circuit.
  - b. (5%) Please find the Elmore delay from input  $x$  to each receiver.
2. (65%) In the following problems, assume that the length of all MOS transistors are  $1\mu\text{m}$ . In a particular process technology, a CMOS inverter with pMOS width  $W_p=2\mu\text{m}$  and nMOS width  $W_n=1\mu\text{m}$  has equal propagation fall delay and rise delay  $T_{pHL} = T_{pLH} = T_{inv}$  of output switching from high to low and output switching from low to high respectively. The following Figure shows the circuit and the corresponding SPICE netlist.


 
```
VDD vdd gnd 1.8v
M1 y a gnd gnd NMOS W=1U L=1U
M2 y a vdd vdd PMOS W=2U L=1U
Vin a gnd pulse 0 1.8v 25ps 0ps 0 ps 35ps 80ps
* pulse v1 v2 td tr tf pw per
```




- 2.1. (5%) Draw the static CMOS circuit diagram of a three-input NAND gate (named NAND3) whose Boolean function is  $Y = \overline{ABC}$ . Hint: CMOS NAND3 consists of a pull-up pMOS network with three pMOS transistors and a pull-down nMOS network with three nMOS transistors.
- 2.2. (15%) Write down the SPICE netlist that describes the CMOS NAND3 circuits. Hint: the SPICE list contains 6 SPICE statements starting with M... indicating MOS transistors, and 1 statement starting with V... indicating the power supply.

- 2.3. (10%) Draw the waveforms of the three inputs so that they can be used to measure the “worse-case” propagation delay from the input A to the output Y. Hint: worse-case delay happens when only one MOS is ON in case of MOS transistors connected in parallel.
- 2.4. (5%) Write down the SPICE netlist that generates the above input waveforms. Hint: the SPICE list contains 3 SPICE statements starting with V
- 2.5. (5%) Design the static CMOS circuit for three-input AND gate (named AND3)  $Y = ABC$ . How many transistors are required? Note that in static CMOS design, the output should be either strong (good) logic “1” or strong (good) logic “0”. How many transistors are required?
- 2.6. (5%) Design a circuit for AND3 with fewer transistors than static CMOS AND3. Compare it with the static CMOS AND3 in the previous problem. Hint: AND3 circuit with weak logic “1” or logic “0” might have fewer transistors.
- 2.7. (10%) A two-to-one multiplexer (named MUX2) can be represented by Boolean function  $SD_0 + \bar{S}D_1$ . Use CMOS NAND2, NOR2, and inverters to construct MUX2. How many transistors are required in this circuit?
- 2.8. (10%) Draw the circuit diagram for following circuit layout with inputs A, B, and output Y. What is the logic function of the layout?

3. (25%) Answer the following questions about

 - 3.1. (10%) The simplest D-latch circuit design is a single nMOS shown below. It has many drawbacks such as 1) threshold voltage drop, 2) non-restoring, 3) backdriving, 4) dynamic, 5) diffusion input



Explain the meaning for each of the above five drawbacks. Why are they not good for circuit design and How can you avoid the drawbacks?

- 3.2. (5%) Comment on conventional CMOS logic circuit with pull-down nMOS network and pull-up pMOS network. Does CMOS logic circuit violate the above circuit design criteria?
- 3.3. (10%) Design a robust D-latch circuit that does not have any drawback mentioned above.